


# Electronics Kirchhoff's Laws

Terry Sturtevant


Wilfrid Laurier University

February 16, 2010


# Kirchhoff's Current Law

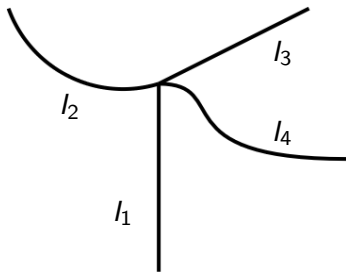


# Kirchhoff's Current Law

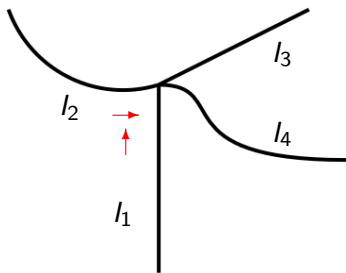


# Kirchhoff's Current Law

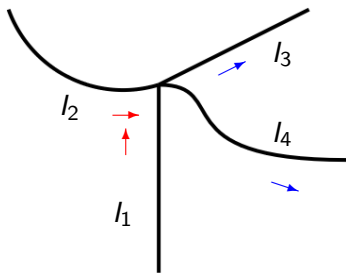

# Kirchhoff's Current Law

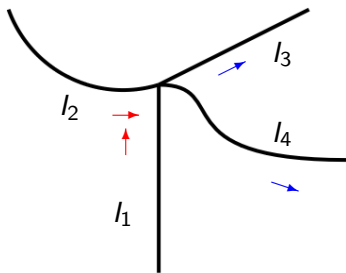


# Kirchhoff's Current Law

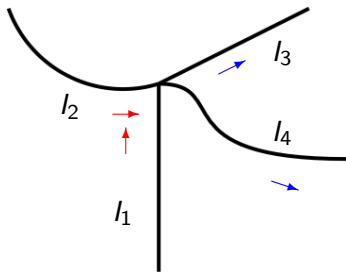

Sum of the currents at a node is zero


# Kirchhoff's Current Law

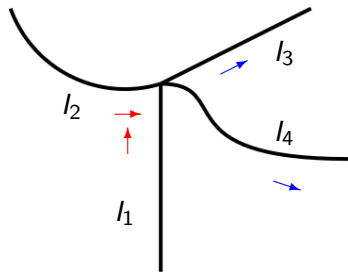

Sum of the currents at a node is zero


→ Sum of the currents *into* a node equals the sum of the currents *out of* the node.

# Kirchhoff's Voltage Law

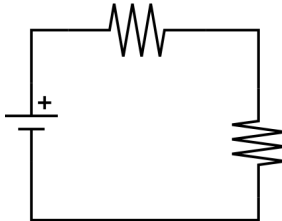





# Kirchhoff's Voltage Law

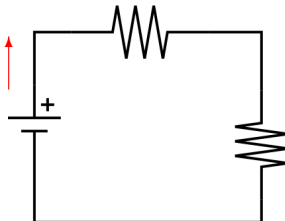

# Kirchhoff's Voltage Law

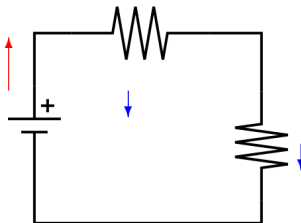


# Kirchhoff's Voltage Law

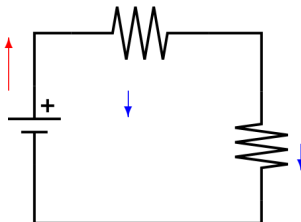

Sum of the voltage drops around a loop is zero

# Kirchhoff's Voltage Law

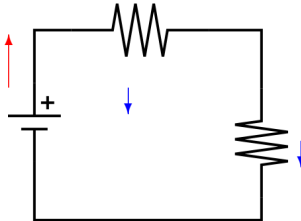

Sum of the voltage drops around a loop is zero


→ Sum of the voltage *increases* in a loop equals the sum of the voltage *drops* in the loop

# Applications of Kirchhoff's Current Law


# Applications of Kirchhoff's Current Law

## Series Circuits

# Series Circuits

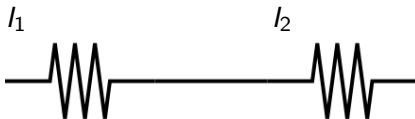


# Series Circuits

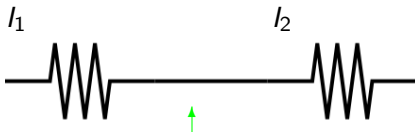

A "virtual" node can be created between the two resistors



## Series Circuits

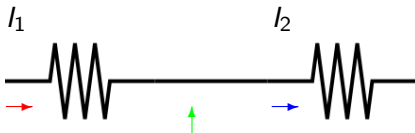



Since there is nowhere else for current to go,  $I_1 \equiv I_2$


# Applications of Kirchhoff's Current Law


# Applications of Kirchhoff's Current Law

## Parallel Circuits

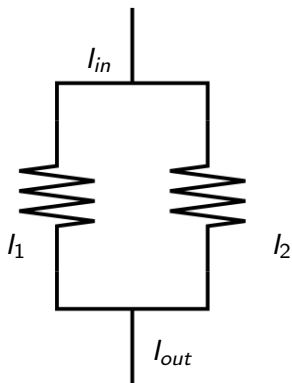


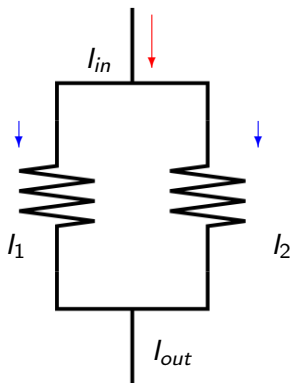

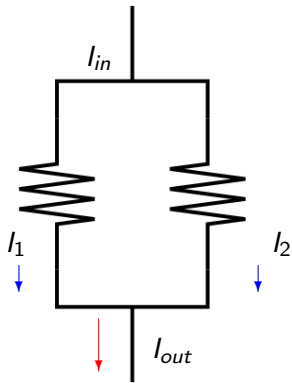

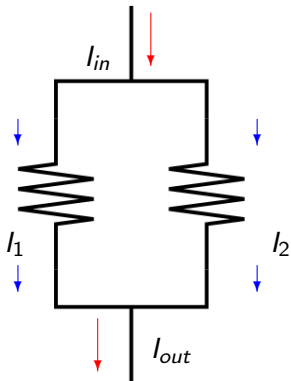

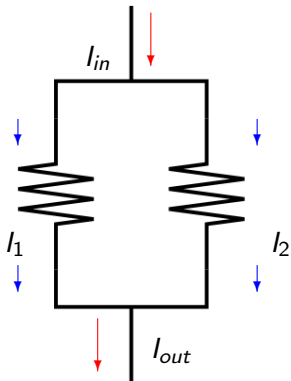The current exiting at the bottom has to equal the current entering at the top




$$I_{in} = I_1 + I_2 = I_{out}$$




# Applications of Kirchhoff's Voltage Law


# Applications of Kirchhoff's Voltage Law

## Voltage dividers

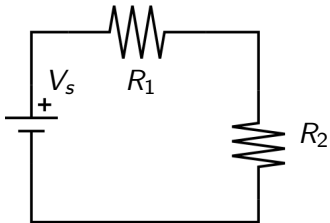


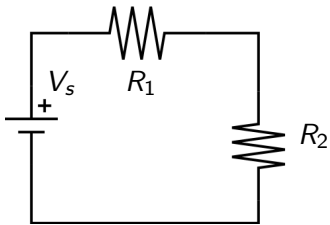


$$V_s = V_{R_1} + V_{R_2}$$

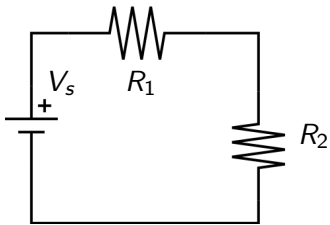

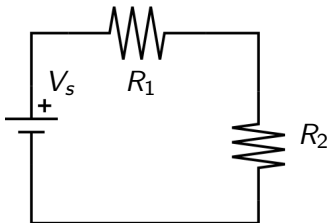
- A **voltage divider** “divides” the supply voltage



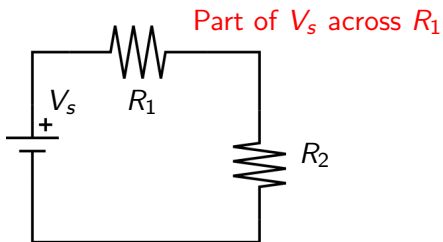- A **voltage divider** “divides” the supply voltage
- It's useful when you need a different voltage than the supply



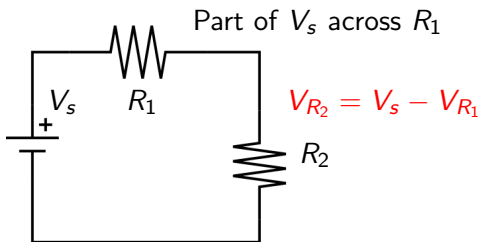- A **voltage divider** “divides” the supply voltage
- It's useful when you need a different voltage than the supply



- A **voltage divider** “divides” the supply voltage
- It's useful when you need a different voltage than the supply




Since the current is the same in both resistors, the voltage is *divided* between the two; thus it is a **voltage divider**.


Since the current is the same in both resistors, the voltage is *divided* between the two; thus it is a **voltage divider**.

*Voltage divider circuits are very common, even when one or both circuit elements aren't resistors.*


Since the current is the same in both resistors, the voltage is *divided* between the two; thus it is a **voltage divider**.

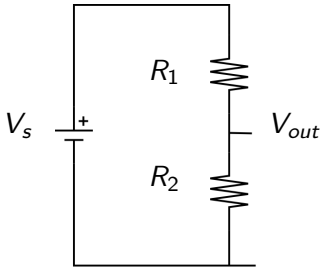*Voltage divider circuits are very common, even when one or both circuit elements aren't resistors.*



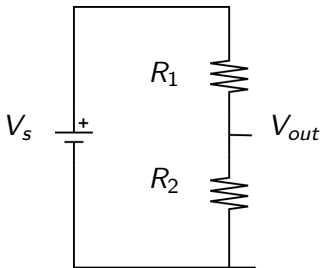


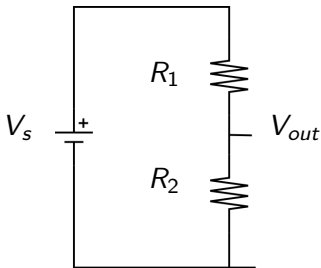Usually a voltage divider is drawn like this so it looks like a ladder.




Usually a voltage divider is drawn like this so it looks like a ladder.

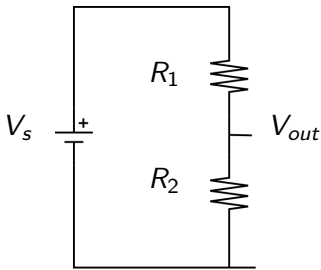As you climb the ladder, the voltage increases.




Since  $I_1 = I_2$ ,

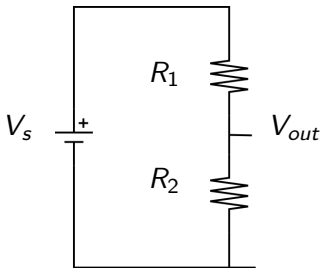


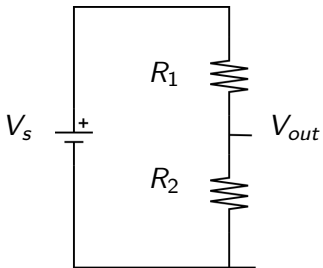Since  $I_1 = I_2$ , (by Kirchhoff's current law,)






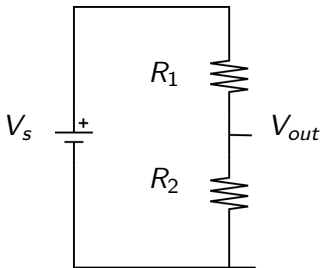
Since  $I_1 = I_2$ , (by Kirchhoff's current law),  
and  $V_s = V_{R_1} + V_{R_2}$ ,



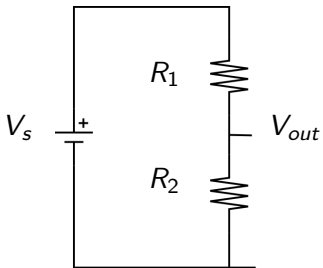
Since  $I_1 = I_2$ , (by Kirchhoff's current law),  
and  $V_s = V_{R_1} + V_{R_2}$ , (by Kirchhoff's voltage law),



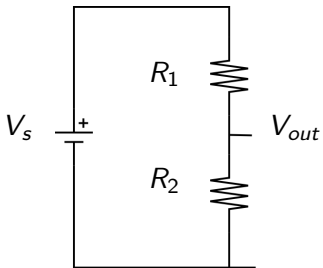
Since  $I_1 = I_2$ , (by Kirchhoff's current law),  
and  $V_s = V_{R_1} + V_{R_2}$ , (by Kirchhoff's voltage law),  
so  $V_s = I_1 R_1 + I_1 R_2$



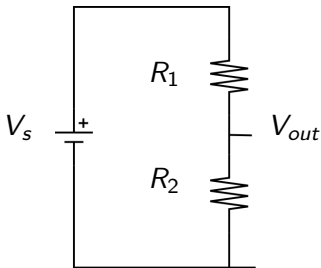
Since  $I_1 = I_2$ , (by Kirchhoff's current law),  
and  $V_s = V_{R_1} + V_{R_2}$ , (by Kirchhoff's voltage law),  
so  $V_s = I_1 R_1 + I_1 R_2 = I (R_1 + R_2)$



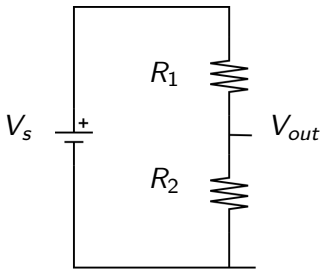
Since  $I_1 = I_2$ , (by Kirchhoff's current law),  
and  $V_s = V_{R_1} + V_{R_2}$ , (by Kirchhoff's voltage law),  
so  $V_s = I_1 R_1 + I_1 R_2 = I (R_1 + R_2)$   
$$I = \frac{V_s}{R_1 + R_2}$$



$$\text{So } V_{out} = V_2 = IR_2$$

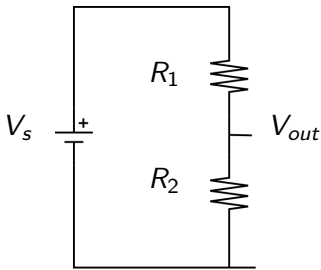
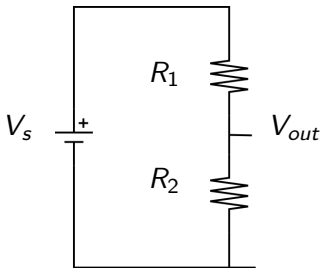
$$\text{So } V_{out} = V_2 = IR_2 = \frac{V_s}{R_1 + R_2} R_2$$



$$\begin{aligned} \text{So } V_{out} &= V_2 = IR_2 = \frac{V_s}{R_1 + R_2} R_2 \\ &= V_s \left( \frac{R_2}{R_1 + R_2} \right) \end{aligned}$$



# Voltage divider (no load)

## Voltage divider (no load)

If  $R_1 = 5\Omega$  ,  $R_2 = 10\Omega$ ,  $V_s = 5V$

## Voltage divider (no load)

If  $R_1 = 5\Omega$  ,  $R_2 = 10\Omega$ ,  $V_s = 5V$

$V_{out}$

## Voltage divider (no load)

If  $R_1 = 5\Omega$  ,  $R_2 = 10\Omega$ ,  $V_s = 5V$


$$\begin{aligned} V_{out} \\ = V_s \left( \frac{R_2}{R_1 + R_2} \right) = 5 \left( \frac{10}{5 + 10} \right) \end{aligned}$$

## Voltage divider (no load)

If  $R_1 = 5\Omega$  ,  $R_2 = 10\Omega$ ,  $V_s = 5V$


$$\begin{aligned}V_{out} &= V_s \left( \frac{R_2}{R_1 + R_2} \right) = 5 \left( \frac{10}{5 + 10} \right) \\ &= 3.3V\end{aligned}$$

## Voltage divider (with load $R_L$ )

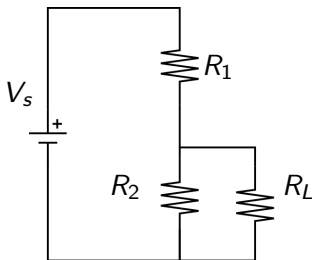


Load will reduce the output voltage

# Voltage divider (with load $R_L$ )

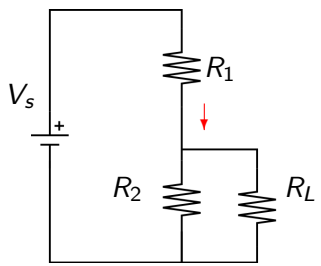

## Voltage divider (with load $R_L$ )

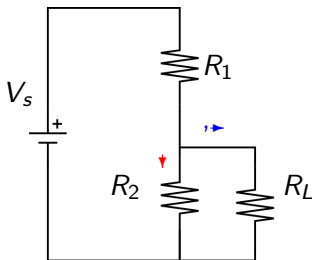

Some current goes through  $R_2$ , but some goes through  $R_L$  so the *effective* value of  $R_2$  is reduced.



If  $R_1 = 5\Omega$  ,  $R_2 = 10\Omega$ ,  $V_s = 5V$  and  $R_L = 10\Omega$

If  $R_1 = 5\Omega$  ,  $R_2 = 10\Omega$ ,  $V_s = 5V$  and  $R_L = 10\Omega$

Parallel resistance of  $R_2$  and  $R_L = \frac{R_2 R_L}{R_2 + R_L}$

If  $R_1 = 5\Omega$ ,  $R_2 = 10\Omega$ ,  $V_s = 5V$  and  $R_L = 10\Omega$

Parallel resistance of  $R_2$  and  $R_L = \frac{R_2 R_L}{R_2 + R_L}$

$$= \frac{10 \times 10}{10 + 10} = 5\Omega$$

If  $R_1 = 5\Omega$  ,  $R_2 = 10\Omega$ ,  $V_s = 5V$  and  $R_L = 10\Omega$

Parallel resistance of  $R_2$  and  $R_L = \frac{R_2 R_L}{R_2 + R_L}$

$$= \frac{10 \times 10}{10 + 10} = 5\Omega$$

Thus  $V_{out}$

If  $R_1 = 5\Omega$  ,  $R_2 = 10\Omega$ ,  $V_s = 5V$  and  $R_L = 10\Omega$

Parallel resistance of  $R_2$  and  $R_L = \frac{R_2 R_L}{R_2 + R_L}$

$$= \frac{10 \times 10}{10 + 10} = 5\Omega$$

Thus  $V_{out}$

$$= V_s \frac{R_p}{R_1 + R_p} = 5 \left( \frac{5}{5 + 5} \right)$$

If  $R_1 = 5\Omega$  ,  $R_2 = 10\Omega$ ,  $V_s = 5V$  and  $R_L = 10\Omega$

Parallel resistance of  $R_2$  and  $R_L = \frac{R_2 R_L}{R_2 + R_L}$

$$= \frac{10 \times 10}{10 + 10} = 5\Omega$$

Thus  $V_{out}$

$$= V_s \frac{R_p}{R_1 + R_p} = 5 \left( \frac{5}{5 + 5} \right)$$

$$= 2.5V$$