

# Electronics

## Resistive Sensors and Bridge Circuits

Terry Sturtevant

Wilfrid Laurier University

September 27, 2012

# Switches in voltage dividers

## Switches in voltage dividers


- One of the simplest forms of voltage divider is where one of the elements is a *switch*.


## Switches in voltage dividers


- One of the simplest forms of voltage divider is where one of the elements is a *switch*.
- A switch can be thought of as a resistor which can have a value of either zero or infinity.
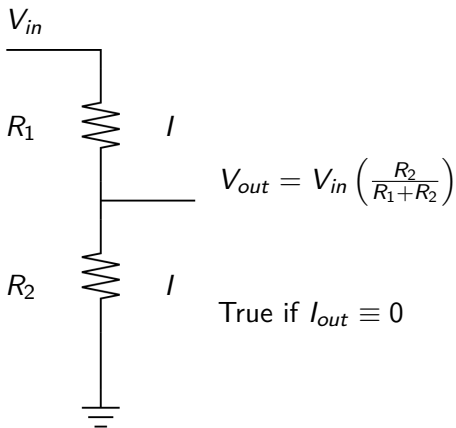
## Switches in voltage dividers


- One of the simplest forms of voltage divider is where one of the elements is a *switch*.
- A switch can be thought of as a resistor which can have a value of either zero or infinity.
- Following is an illustration of a voltage divider where one element is a switch.




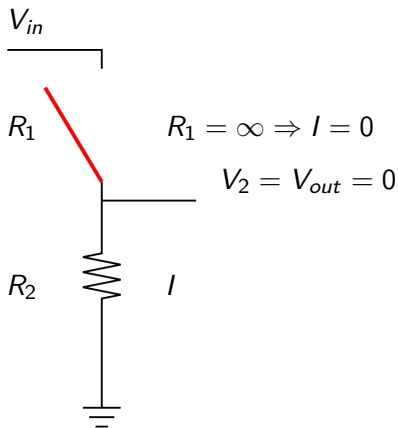

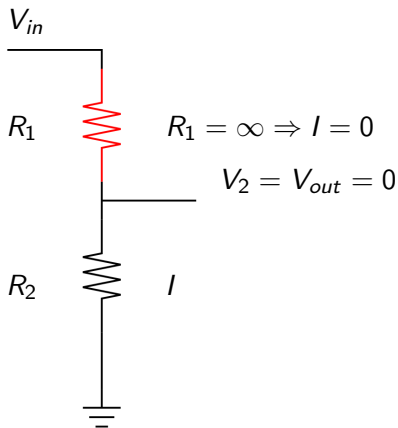




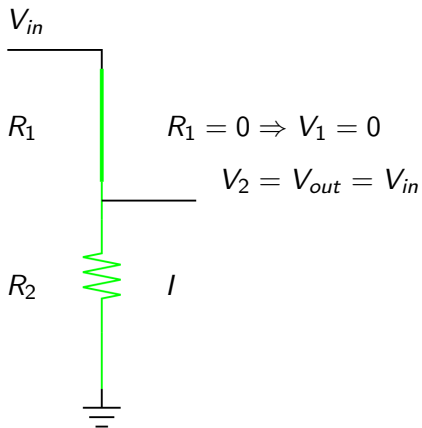

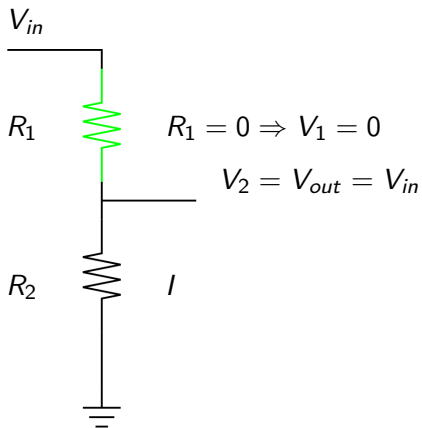

- So if one of the elements is a *switch*, the output varies between 0 and  $V_{in}$ .

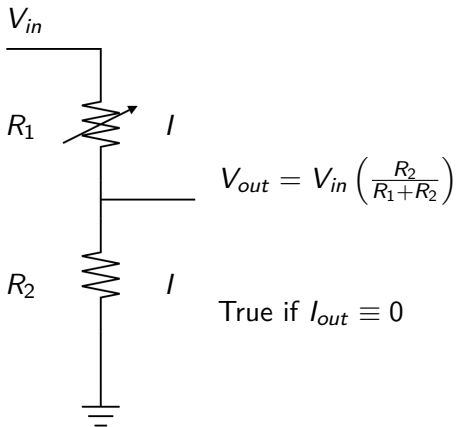- So if one of the elements is a *switch*, the output varies between 0 and  $V_{in}$ .
- If either resistor in a voltage divider is *variable*, then a range of output voltages is possible.



# Resistive sensors

# Resistive sensors

A **resistive sensor** is a resistor which changes according to some physical change in its environment.

# Resistive sensors

A **resistive sensor** is a resistor which changes according to some physical change in its environment. Some examples would be:



# Resistive sensors

A **resistive sensor** is a resistor which changes according to some physical change in its environment. Some examples would be:

- Potentiometer;

# Resistive sensors

A **resistive sensor** is a resistor which changes according to some physical change in its environment. Some examples would be:

- Potentiometer; the resistance varies with *physical movement*

# Resistive sensors

A **resistive sensor** is a resistor which changes according to some physical change in its environment. Some examples would be:

- Potentiometer; the resistance varies with *physical movement*
- Photoresistor;

# Resistive sensors

A **resistive sensor** is a resistor which changes according to some physical change in its environment. Some examples would be:

- Potentiometer; the resistance varies with *physical movement*
- Photoresistor; the resistance varies with *light*

# Resistive sensors

A **resistive sensor** is a resistor which changes according to some physical change in its environment. Some examples would be:

- Potentiometer; the resistance varies with *physical movement*
- Photoresistor; the resistance varies with *light*
- Thermistor;

# Resistive sensors

A **resistive sensor** is a resistor which changes according to some physical change in its environment. Some examples would be:

- Potentiometer; the resistance varies with *physical movement*
- Photoresistor; the resistance varies with *light*
- Thermistor; the resistance varies with *heat*

# Resistive sensors

A **resistive sensor** is a resistor which changes according to some physical change in its environment. Some examples would be:

- Potentiometer; the resistance varies with *physical movement*
- Photoresistor; the resistance varies with *light*
- Thermistor; the resistance varies with *heat*
- Strain gauge (or gage);

# Resistive sensors

A **resistive sensor** is a resistor which changes according to some physical change in its environment. Some examples would be:

- Potentiometer; the resistance varies with *physical movement*
- Photoresistor; the resistance varies with *light*
- Thermistor; the resistance varies with *heat*
- Strain gauge (or gage); the resistance varies with *stress* or *compression*



# Resistive sensors

A **resistive sensor** is a resistor which changes according to some physical change in its environment. Some examples would be:


- Potentiometer; the resistance varies with *physical movement*
- Photoresistor; the resistance varies with *light*
- Thermistor; the resistance varies with *heat*
- Strain gauge (or gage); the resistance varies with *stress* or *compression*
- Force-dependent resistor;

# Resistive sensors


A **resistive sensor** is a resistor which changes according to some physical change in its environment. Some examples would be:


- Potentiometer; the resistance varies with *physical movement*
- Photoresistor; the resistance varies with *light*
- Thermistor; the resistance varies with *heat*
- Strain gauge (or gage); the resistance varies with *stress* or *compression*
- Force-dependent resistor; the resistance varies with *applied pressure*

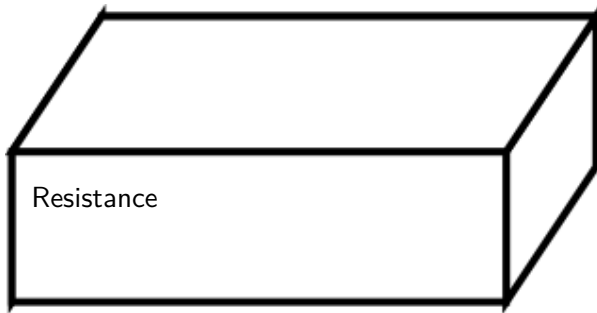Here's an example of how a strain gauge works.




$$R = \rho \frac{L}{A}$$

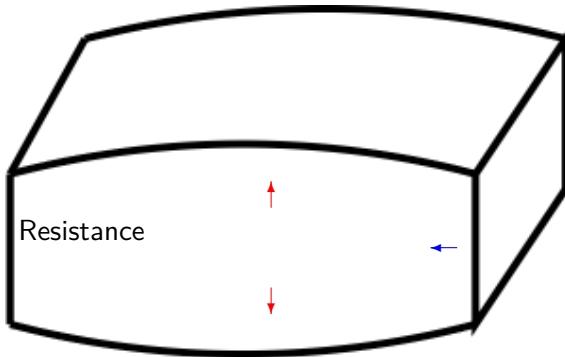


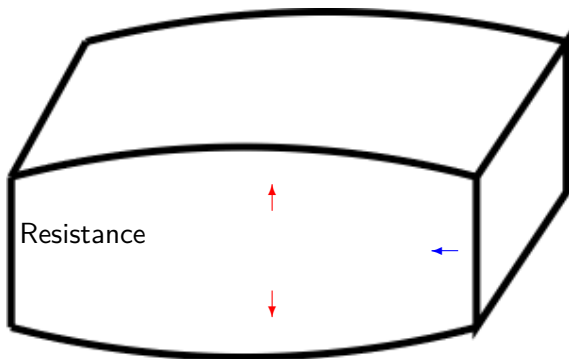

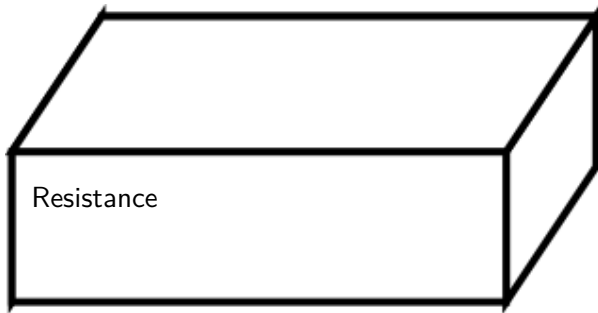
$$R' = \rho \frac{(L - \Delta L)}{(A + \Delta A)} < R$$




$$R = \rho \frac{L}{A}$$

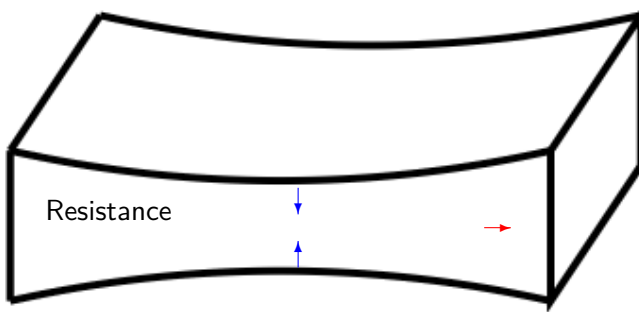




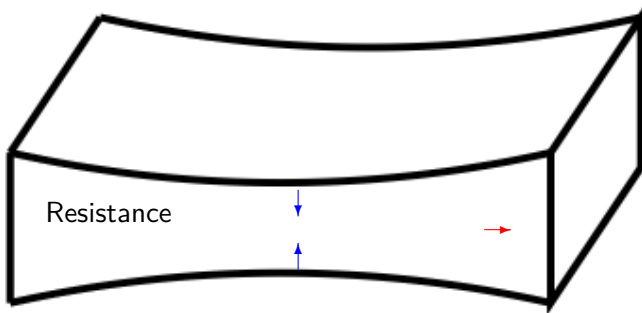

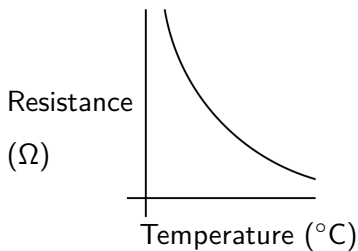
$$R' = \rho \frac{(L + \Delta L)}{(A - \Delta A)} > R$$



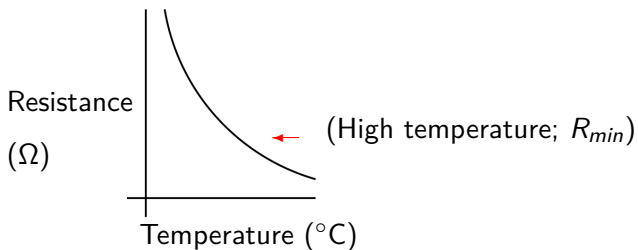This is the resistance/temperature curve for a thermistor.



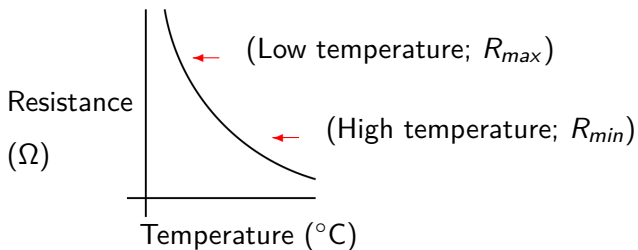This is the resistance/temperature curve for a thermistor.



This is the resistance/temperature curve for a thermistor.

- If we want to put this variable resistor in a voltage divider, then we need to *choose* the other resistor.

- If we want to put this variable resistor in a voltage divider, then we need to *choose* the other resistor.
- To make the output *vary over as large a range as possible* as the variable resistor goes from  $R_{min}$  to  $R_{max}$ , it turns out we want to choose the other resistor,  $R$  so that

- If we want to put this variable resistor in a voltage divider, then we need to *choose* the other resistor.
- To make the output *vary over as large a range as possible* as the variable resistor goes from  $R_{min}$  to  $R_{max}$ , it turns out we want to choose the other resistor,  $R$  so that

$$R = \sqrt{R_{min} \times R_{max}}$$

# Wheatstone bridges



# Wheatstone bridges


- A common type of circuit is a **Wheatstone bridge**.


# Wheatstone bridges


- A common type of circuit is a **Wheatstone bridge**.
- It is really a pair of voltage dividers using a common voltage source.

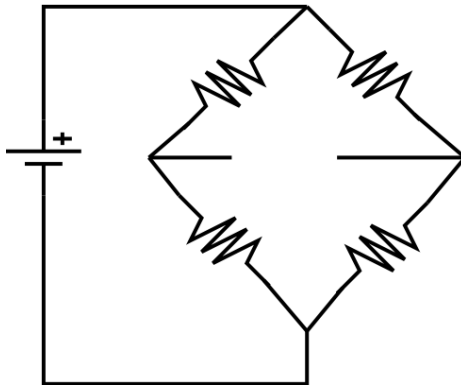
# Wheatstone bridges


- A common type of circuit is a **Wheatstone bridge**.
- It is really a pair of voltage dividers using a common voltage source.
- It's usually operated with the output voltage at or close to zero.



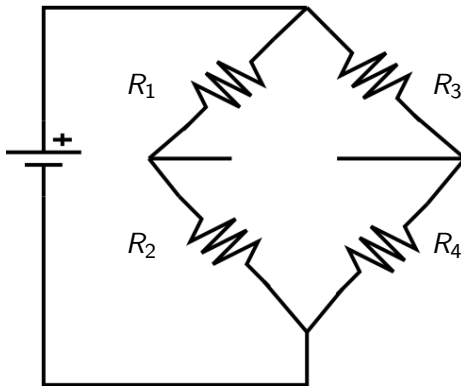

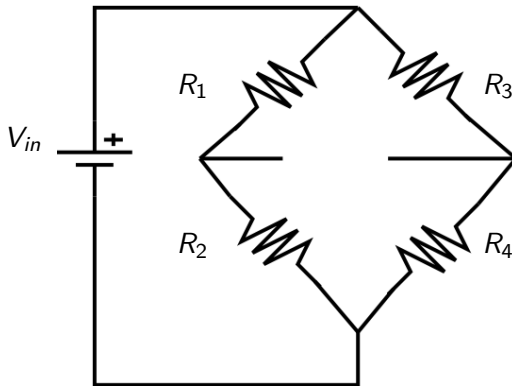


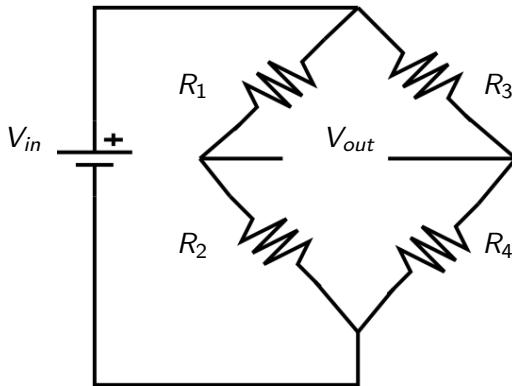

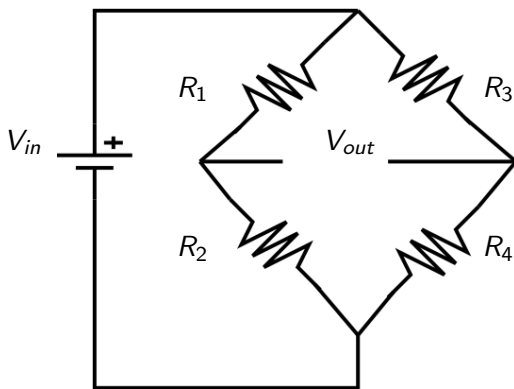


This is a Wheatstone bridge.




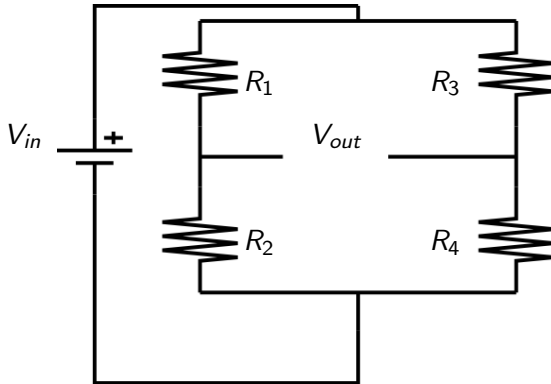

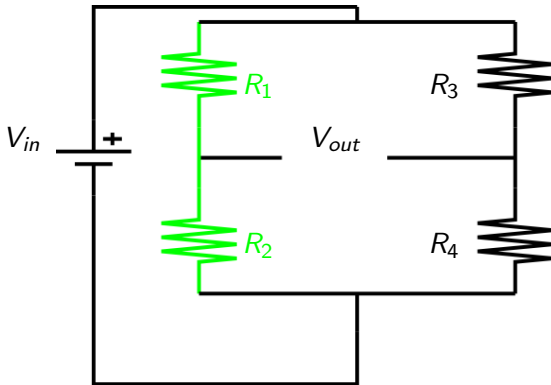Here it's redrawn to show the two voltage dividers.



Here's one voltage divider.

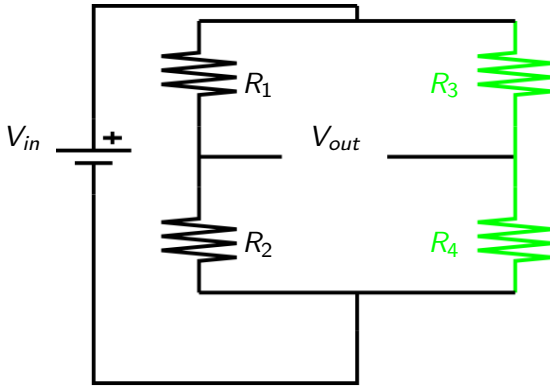


Here's the other voltage divider.

- Often a Wheatstone bridge is used with one resistor variable, such as a resistive sensor.

- Often a Wheatstone bridge is used with one resistor variable, such as a resistive sensor.
- Knowing the other resistors allows the variable one to be easily determined.

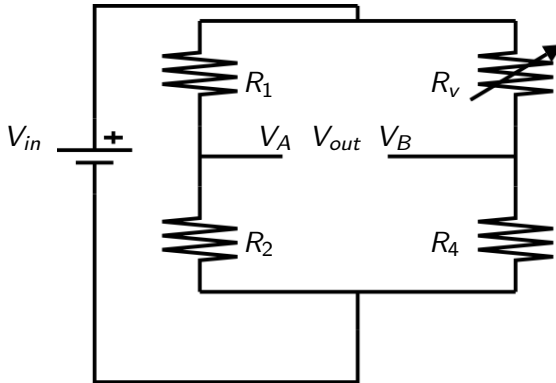- Often a Wheatstone bridge is used with one resistor variable, such as a resistive sensor.
- Knowing the other resistors allows the variable one to be easily determined.
- The circuit is very sensitive to small changes in the variable resistor.



The variable resistor could be in any of the four positions; this is one example.

# Balancing a Wheatstone Bridge



# Balancing a Wheatstone Bridge

- When the bridge is “balanced”,  $V_o = 0$  or  $V_A = V_B$ .

# Balancing a Wheatstone Bridge

- When the bridge is “balanced”,  $V_o = 0$  or  $V_A = V_B$ .
- (This will happen when  $\frac{R_1}{R_2} = \frac{R_3}{R_4}$ .)

# Balancing a Wheatstone Bridge

- When the bridge is “balanced”,  $V_o = 0$  or  $V_A = V_B$ .
- (This will happen when  $\frac{R_1}{R_2} = \frac{R_V}{R_4}$ .)
- For our diagram  $R_1 \rightarrow R_2$  is the *reference* branch, and  $R_V \rightarrow R_4$  is the *evaluation* branch.

## Balancing a Wheatstone Bridge


- When the bridge is “balanced”,  $V_o = 0$  or  $V_A = V_B$ .
- (This will happen when  $\frac{R_1}{R_2} = \frac{R_V}{R_4}$ .)
- For our diagram  $R_1 \rightarrow R_2$  is the *reference* branch, and  $R_V \rightarrow R_4$  is the *evaluation* branch.
- If  $R_V$  increases,  $V_B$  will decrease, and vice versa.

# Balancing a Wheatstone Bridge

- When the bridge is “balanced”,  $V_o = 0$  or  $V_A = V_B$ .
- (This will happen when  $\frac{R_1}{R_2} = \frac{R_V}{R_4}$ .)
- For our diagram  $R_1 \rightarrow R_2$  is the *reference* branch, and  $R_V \rightarrow R_4$  is the *evaluation* branch.
- If  $R_V$  increases,  $V_B$  will decrease, and vice versa.
- For optimum performance, all resistors should be of the same order of magnitude.
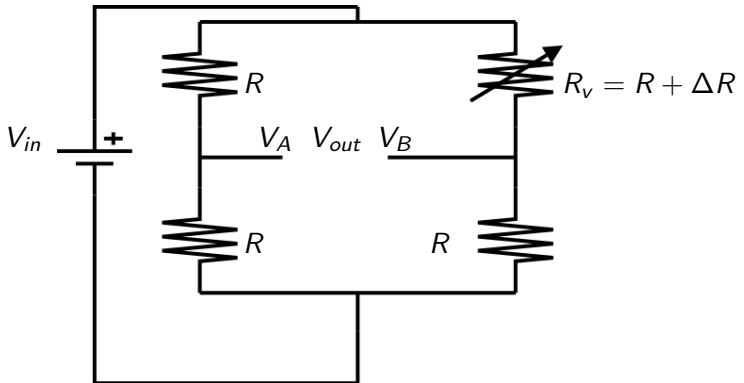
# Balancing a Wheatstone Bridge

- When the bridge is “balanced”,  $V_o = 0$  or  $V_A = V_B$ .
- (This will happen when  $\frac{R_1}{R_2} = \frac{R_V}{R_4}$ .)
- For our diagram  $R_1 \rightarrow R_2$  is the *reference* branch, and  $R_V \rightarrow R_4$  is the *evaluation* branch.
- If  $R_V$  increases,  $V_B$  will decrease, and vice versa.
- For optimum performance, all resistors should be of the same order of magnitude.
- If using a resistive sensor, use a meter to measure resistance of sensor to get a correct order of magnitude.



If resistors are chosen to be equal, except for  $R_v$ , then the output voltage will vary with changes in  $R_v$ .

Specifically,



Specifically,

$$V_A = V \frac{R}{2R} = V/2$$

Specifically,

$$V_A = V \frac{R}{2R} = V/2$$

$$V_B = V \frac{R}{2R + \Delta R} = V \frac{R + \Delta R/2 - \Delta R/2}{2R + \Delta R} = V/2 - V \frac{\Delta R/2}{2R + \Delta R} \approx$$

$$V/2 - V \frac{\Delta R/2}{2R}$$

Specifically,

$$V_A = V \frac{R}{2R} = V/2$$

$$V_B = V \frac{R}{2R + \Delta R} = V \frac{R + \Delta R/2 - \Delta R/2}{2R + \Delta R} = V/2 - V \frac{\Delta R/2}{2R + \Delta R} \approx$$

$$V/2 - V \frac{\Delta R/2}{2R}$$

If no current flows between  $A$  and  $B$  then

Specifically,

$$V_A = V \frac{R}{2R} = V/2$$

$$V_B = V \frac{R}{2R + \Delta R} = V \frac{R + \Delta R/2 - \Delta R/2}{2R + \Delta R} = V/2 - V \frac{\Delta R/2}{2R + \Delta R} \approx$$

$$V/2 - V \frac{\Delta R/2}{2R}$$

If no current flows between  $A$  and  $B$  then

$$V_A - V_B \approx V \frac{\Delta R}{4R}$$

Specifically,

$$V_A = V \frac{R}{2R} = V/2$$

$$V_B = V \frac{R}{2R + \Delta R} = V \frac{R + \Delta R/2 - \Delta R/2}{2R + \Delta R} = V/2 - V \frac{\Delta R/2}{2R + \Delta R} \approx$$
$$V/2 - V \frac{\Delta R/2}{2R}$$

If no current flows between  $A$  and  $B$  then

$$V_A - V_B \approx V \frac{\Delta R}{4R}$$

which can be rearranged to give

Specifically,

$$V_A = V \frac{R}{2R} = V/2$$

$$V_B = V \frac{R}{2R+\Delta R} = V \frac{R+\Delta R/2-\Delta R/2}{2R+\Delta R} = V/2 - V \frac{\Delta R/2}{2R+\Delta R} \approx$$
$$V/2 - V \frac{\Delta R/2}{2R}$$

If no current flows between  $A$  and  $B$  then

$$V_A - V_B \approx V \frac{\Delta R}{4R}$$

which can be rearranged to give

$$\Delta R \approx \frac{(V_A - V_B)}{V} 4R$$

Specifically,

$$V_A = V \frac{R}{2R} = V/2$$

$$V_B = V \frac{R}{2R+\Delta R} = V \frac{R+\Delta R/2-\Delta R/2}{2R+\Delta R} = V/2 - V \frac{\Delta R/2}{2R+\Delta R} \approx$$
$$V/2 - V \frac{\Delta R/2}{2R}$$

If no current flows between  $A$  and  $B$  then

$$V_A - V_B \approx V \frac{\Delta R}{4R}$$

which can be rearranged to give

$$\Delta R \approx \frac{(V_A - V_B)}{V} 4R$$

So we can determine  $\Delta R$ .

Specifically,

$$V_A = V \frac{R}{2R} = V/2$$

$$V_B = V \frac{R}{2R+\Delta R} = V \frac{R+\Delta R/2-\Delta R/2}{2R+\Delta R} = V/2 - V \frac{\Delta R/2}{2R+\Delta R} \approx$$
$$V/2 - V \frac{\Delta R/2}{2R}$$

If no current flows between  $A$  and  $B$  then

$$V_A - V_B \approx V \frac{\Delta R}{4R}$$

which can be rearranged to give

$$\Delta R \approx \frac{(V_A - V_B)}{V} 4R$$

So we can determine  $\Delta R$ .

*(This approximation is true as long as  $\Delta R \ll R$ )*