

# Electronics

## Logic Gate Characteristics: Current

Terry Sturtevant

Wilfrid Laurier University

September 4, 2013

# Current convention

# Current convention

By convention, current into a chip is positive, so current out of a chip is negative.

# Operating current limits

# Operating current limits

Gates have current limits as well as voltage limits.

# Operating current limits

Gates have current limits as well as voltage limits.

There are limits to the input and output currents of each individual gate.

# Operating current limits


Gates have current limits as well as voltage limits.

There are limits to the input and output currents of each individual gate.


In addition, there is some current required by the chip itself, as long as power is applied.

# Output current limits; example


# Output current limits; example

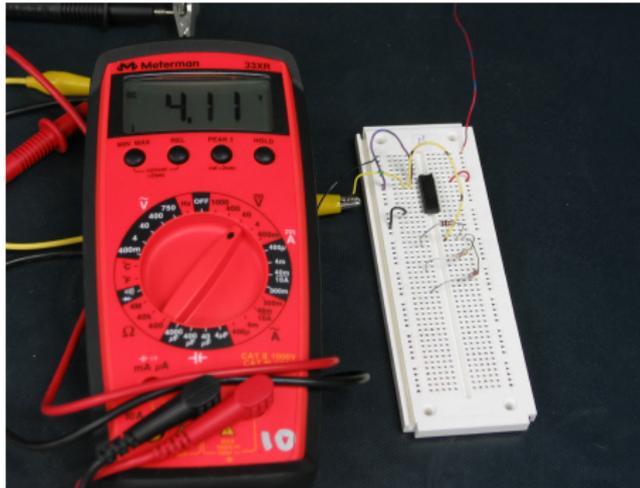


# Output current limits; example

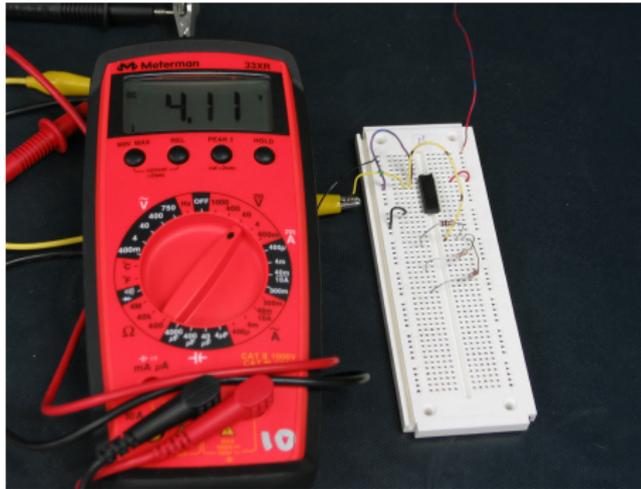

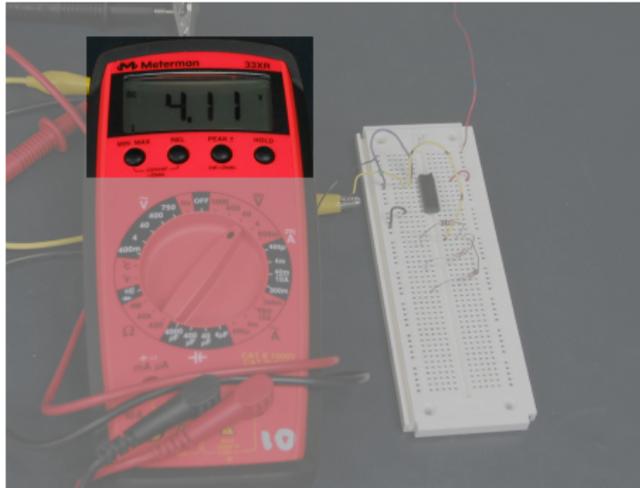
Here's a TTL gate (LS04) producing a HIGH output with no load.



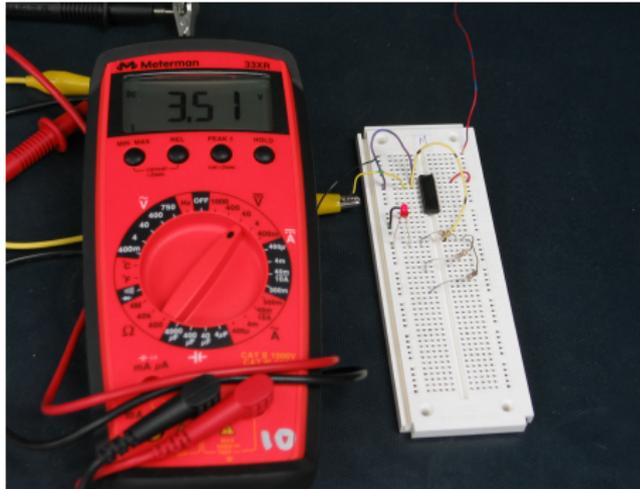
The output voltage with no load is 4.11 Volts.



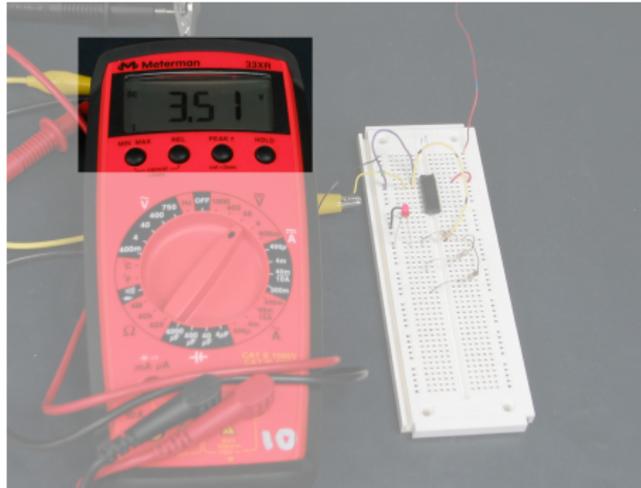
With an LED with a  $5.1k\Omega$  resistor, the output voltage has dropped.



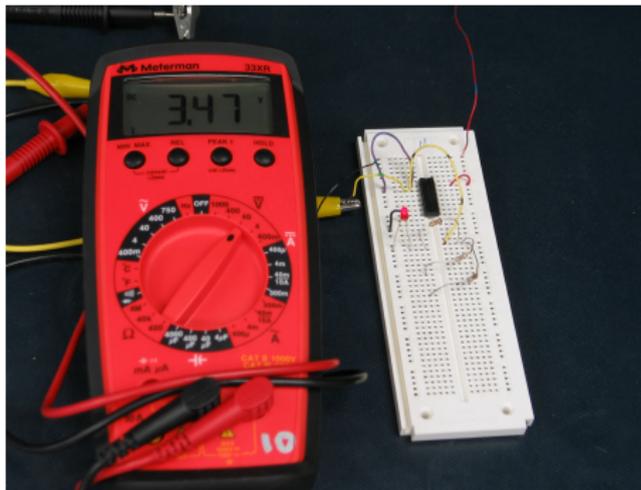
Note that the current being drawn is less than 1 mA.



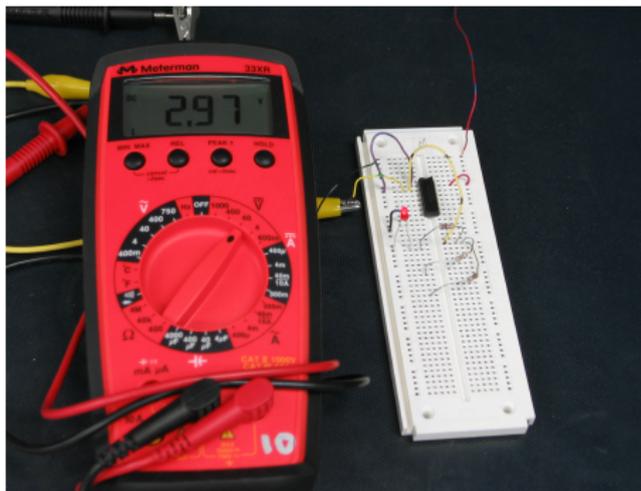
With an LED with a  $1k\Omega$  resistor, the output voltage has dropped further.



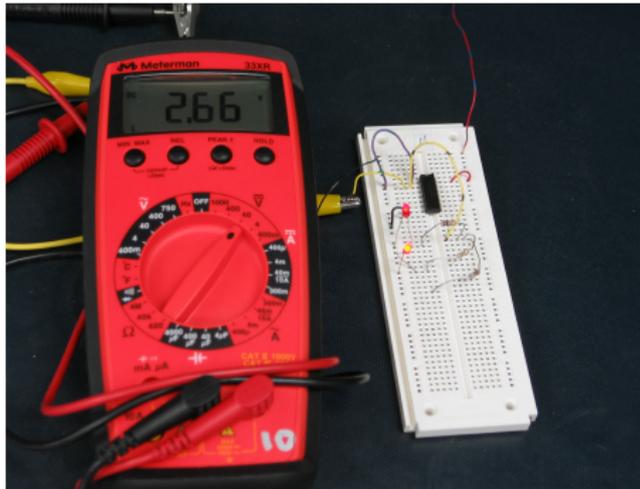
With an LED with a  $100\Omega$  resistor, the output voltage has dropped further.



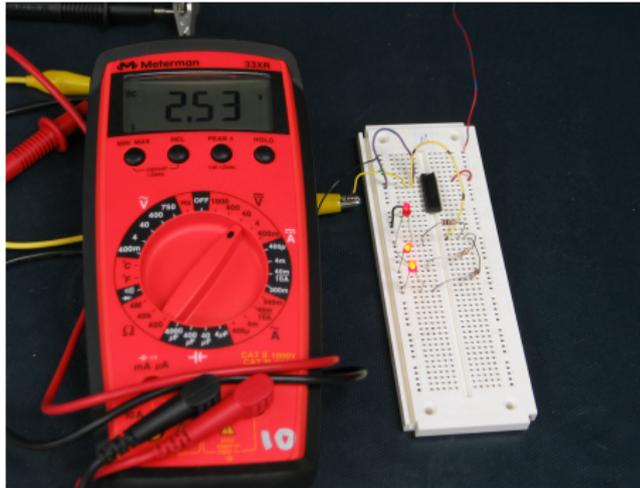
With two LEDs with  $100\Omega$  resistors, the output voltage has dropped further.



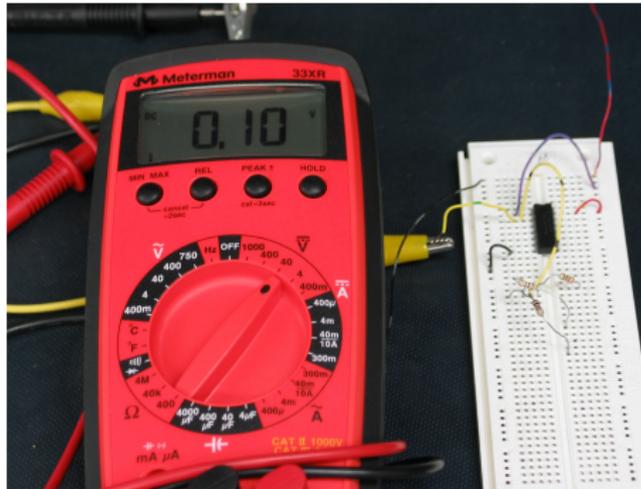
With three LEDs with  $100\Omega$  resistors, the output voltage has dropped further.



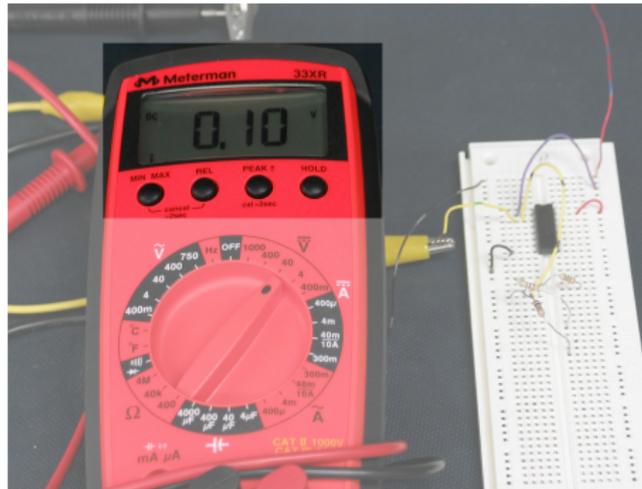
Here's the same TTL gate (LS04) producing a LOW output with no load.



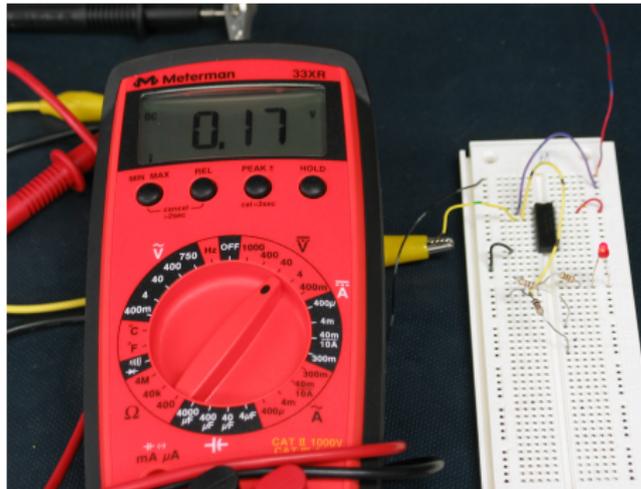
The output voltage with no load is 0.10 Volts.



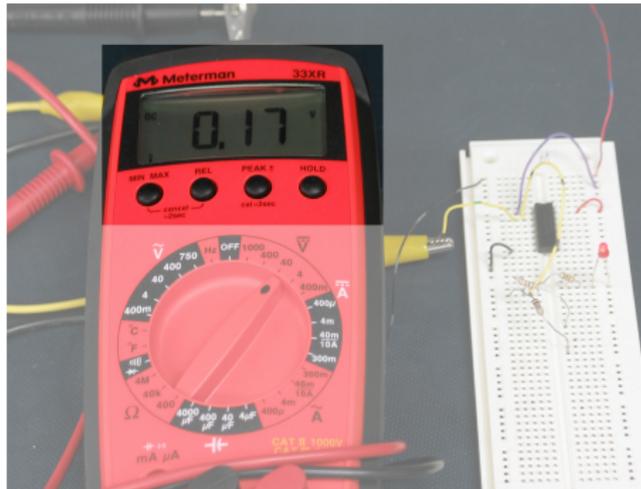
With an LED with a  $5.1k\Omega$  pull-up resistor, the output voltage has risen.



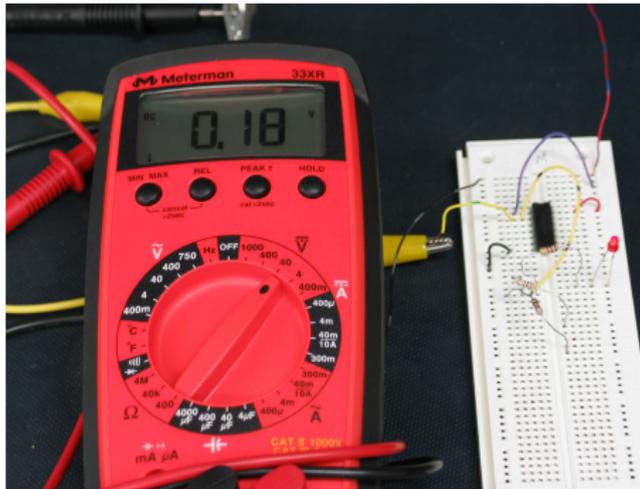
The output voltage with less than 1mA load is 0.17 Volts.



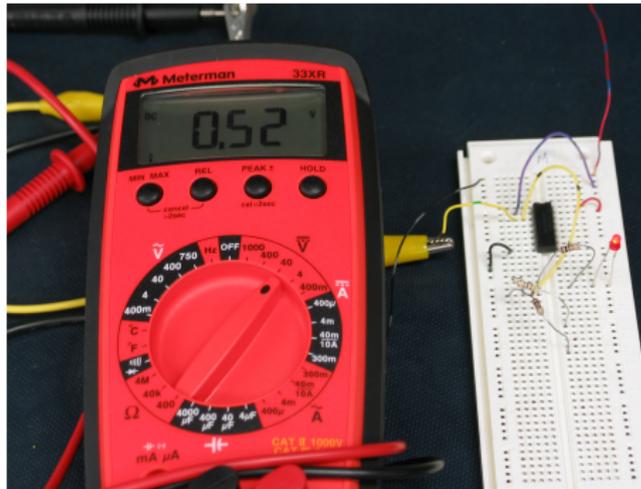
With an LED with a  $1k\Omega$  resistor, the output voltage has risen further.



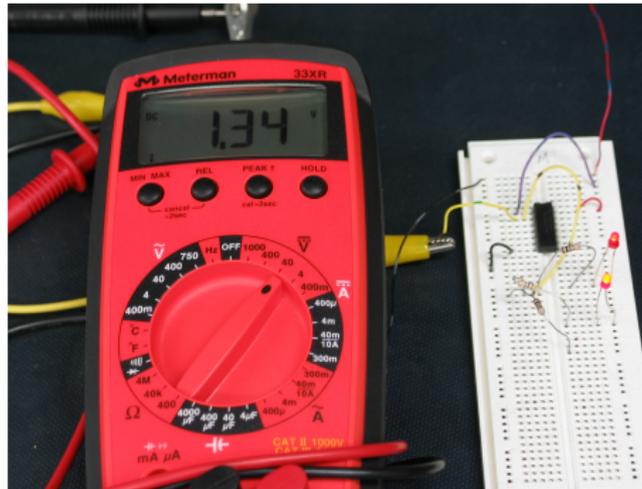With an LED with a  $100\Omega$  resistor, the output voltage has risen further.



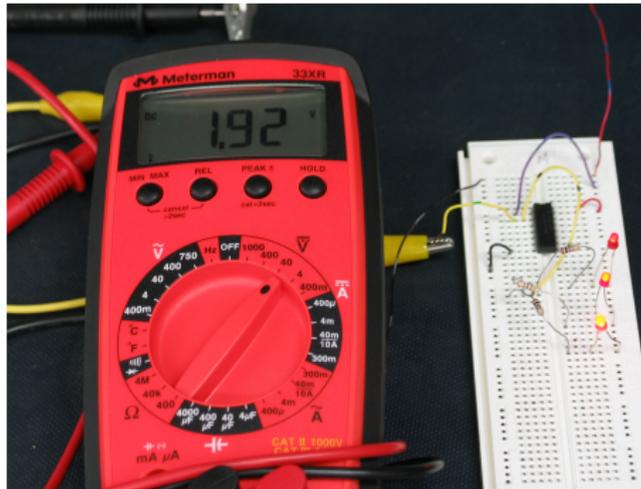With two LEDs with  $100\Omega$  resistors, the output voltage has risen further.



With three LEDs with  $100\Omega$  resistors, the output voltage has risen further.

# Input current requirements

# Input current requirements

When the inputs of a gate are unconnected, they are neither HIGH nor LOW.


# Input current requirements

When the inputs of a gate are unconnected, they are neither HIGH nor LOW.


They are said to be **floating**.

# Input current limits; example


# Input current limits; example

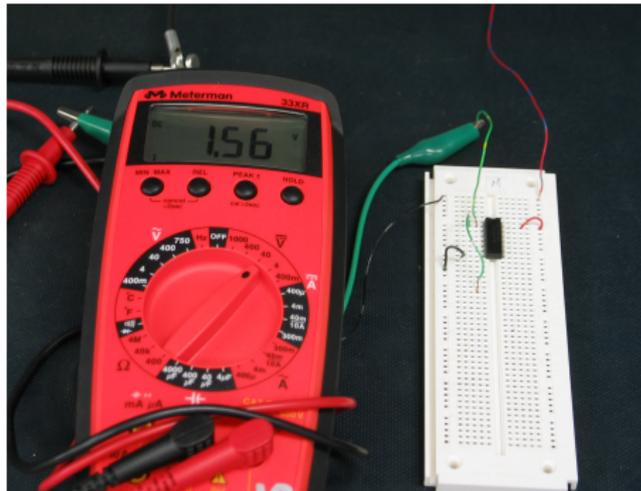


# Input current limits; example

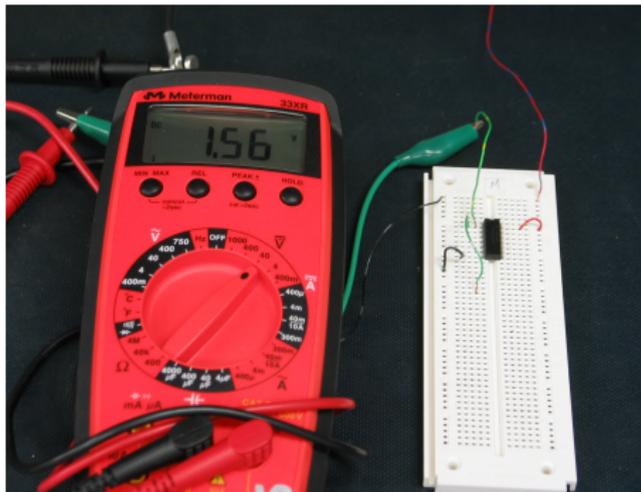

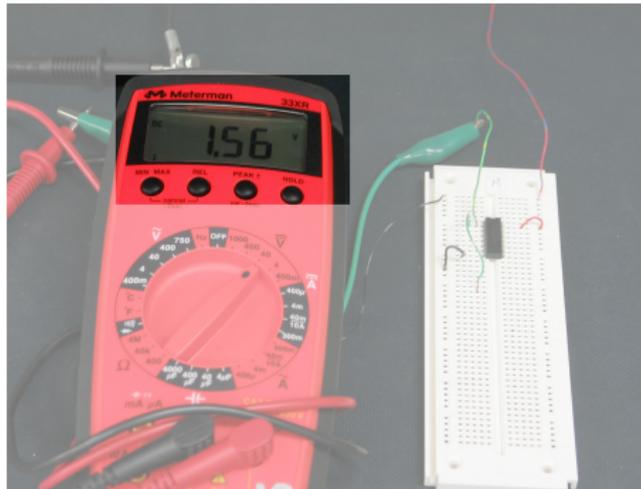
Here's the voltage on the input of a TTL gate (LS04) when left floating.



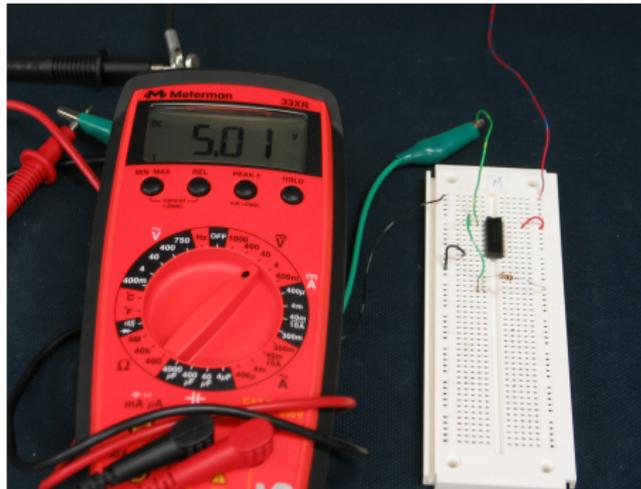
Notice that the input voltage is not valid for either **HIGH** or **LOW**.



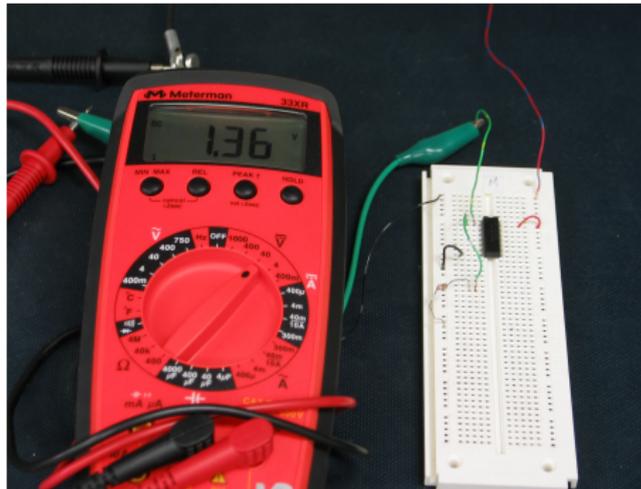
With a  $10k\Omega$  resistor to  $V_{CC}$ , the input is now a valid HIGH.



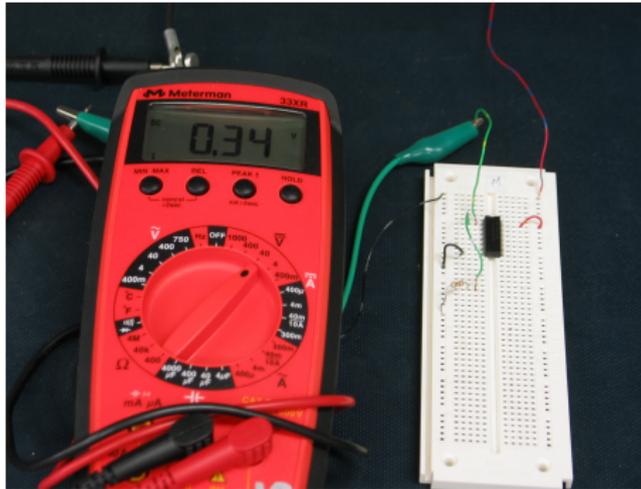
With a  $10k\Omega$  resistor to GROUND, though, the input is **not** a valid LOW.



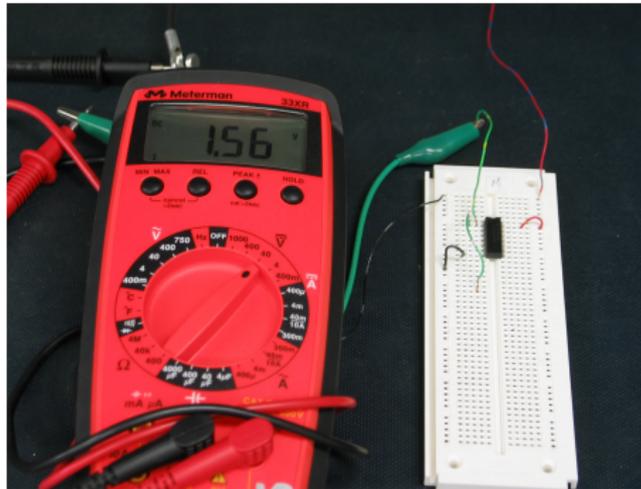With a  $5.1k\Omega$  resistor to GROUND the input **is** a valid LOW.



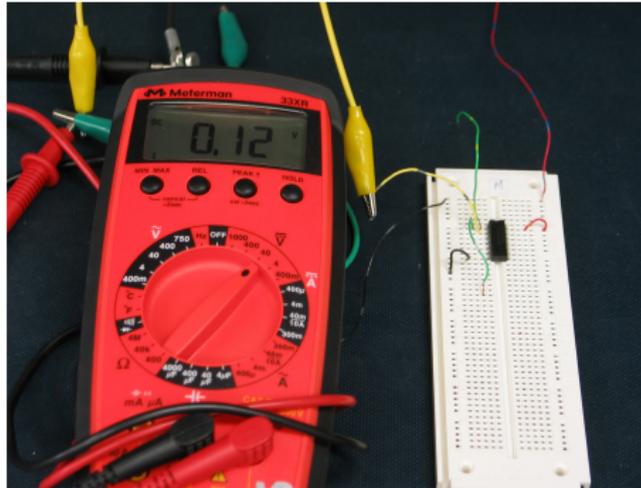What's the output when the inputs are floating?



The output (in this case) is a valid LOW, *as though* the input were a valid HIGH.

# Output current limits; Connecting gates

# Output current limits; Connecting gates

When the output of one gate is used as the input of another gate, the *output* section of the first gate must source (or sink) enough current so that the *input* voltage of the second gate is within the proper range.


## Output current limits; Connecting gates

When the output of one gate is used as the input of another gate, the *output* section of the first gate must source (or sink) enough current so that the *input* voltage of the second gate is within the proper range.


The output of different types of gates is more similar than the inputs functionally, and an equivalent circuit is given in the following figure.

# TTL input current limits

# TTL input current limits

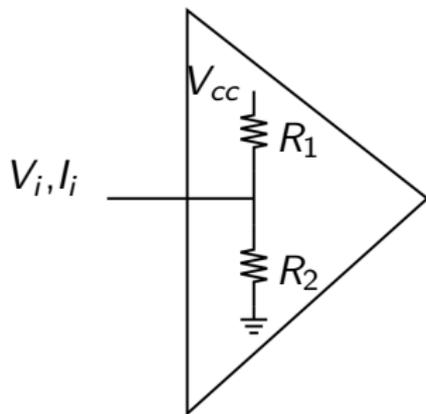

# TTL input current limits

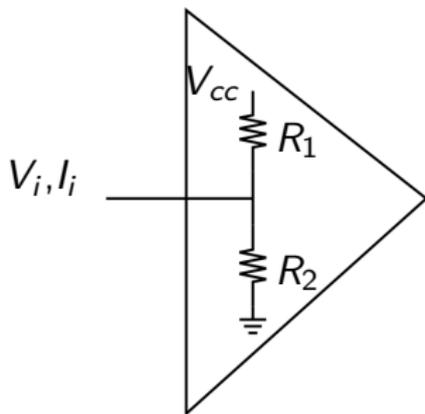

This is an equivalent circuit for a TTL gate *input*.

Logic gate operating currents

Total power consumption

Interfacing families; CMOS to TTL and TTL to CMOS


Operating current limits

**TTL connections**


CMOS connections

# TTL connections

# TTL connections

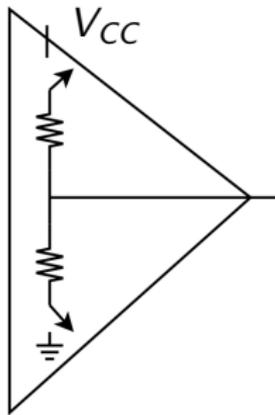


# TTL connections

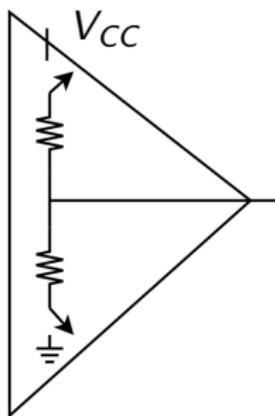


This is an equivalent circuit for a gate *output*.

Here's what happens when a TTL HIGH output feeds into another TTL input.

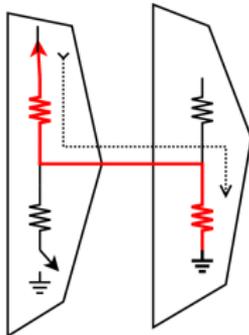Here's what happens when a TTL HIGH output feeds into another TTL input.




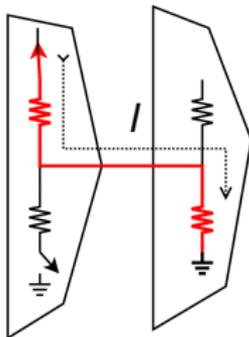Here's what happens when a TTL HIGH output feeds into another TTL input.



Current flows *out of* gate

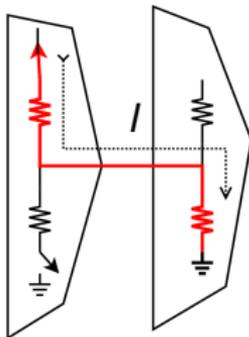Here's what happens when a TTL HIGH output feeds into another TTL input.




Current flows *out of* gate


Voltage must stay above  $V_{IH_{min}}$

Here's what happens when a TTL LOW output feeds into another TTL input.

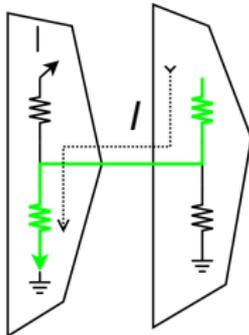Here's what happens when a TTL LOW output feeds into another TTL input.




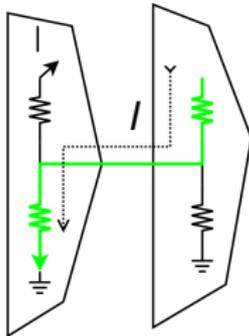Here's what happens when a TTL LOW output feeds into another TTL input.



Current flows *into* gate

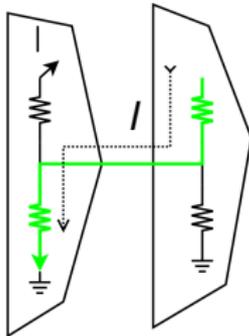Here's what happens when a TTL LOW output feeds into another TTL input.



Current flows *into* gate


Voltage must stay below  $V_{IL_{max}}$

The input to a logic gate is not like an ideal voltmeter.


The input to a logic gate is not like an ideal voltmeter.  
Consider the equivalent circuit shown in the following figure.

# TTL input analysis

# TTL input analysis

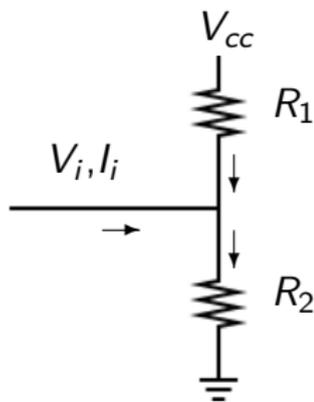

# TTL input analysis

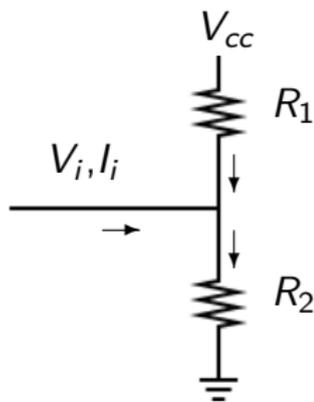

This is an equivalent circuit for a TTL gate *input*.

The actual voltage going into the gate,  $V_i$ , depends on the current input like this:

The actual voltage going into the gate,  $V_i$ , depends on the current input like this:

$$V_i = \left( \frac{V_{cc} - V_i}{R_1} + I_i \right) R_2$$

The actual voltage going into the gate,  $V_i$ , depends on the current input like this:

$$V_i = \left( \frac{V_{cc} - V_i}{R_1} + I_i \right) R_2$$

and thus

$$V_i = \left( V_{cc} \frac{R_2}{R_1} + I_i R_2 \right) \frac{R_1}{R_1 + R_2}$$

The actual voltage going into the gate,  $V_i$ , depends on the current input like this:

$$V_i = \left( \frac{V_{cc} - V_i}{R_1} + I_i \right) R_2$$

and thus

$$V_i = \left( V_{cc} \frac{R_2}{R_1} + I_i R_2 \right) \frac{R_1}{R_1 + R_2}$$

(Note that in order to make  $V_i$  low,  $I_i$  will have to be negative.)

Logic gate operating currents

Total power consumption

Interfacing families; CMOS to TTL and TTL to CMOS

Operating current limits

**TTL connections**

CMOS connections

# TTL

# TTL

For TTL, the amount of current drawn by producing a high output is not the same as the amount drawn by a low output.

# TTL

For TTL, the amount of current drawn by producing a high output is not the same as the amount drawn by a low output. Thus there are two quantities,

# TTL

For TTL, the amount of current drawn by producing a high output is not the same as the amount drawn by a low output.

Thus there are two quantities,  $I_{CCH}$

# TTL

For TTL, the amount of current drawn by producing a high output is not the same as the amount drawn by a low output. Thus there are two quantities,  $I_{CCH}$  and  $I_{CCL}$ .


Since CMOS is based on FETs rather than BJTs, the input current required is very small, but the input capacitance of the gate must be considered.

Since CMOS is based on FETs rather than BJTs, the input current required is very small, but the input capacitance of the gate must be considered.


The following figure shows the equivalent circuit for a CMOS input.

# CMOS input current limits

# CMOS input current limits

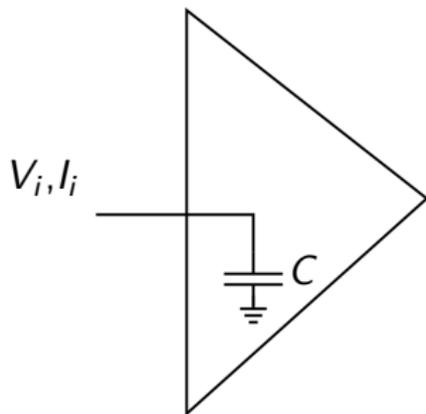

# CMOS input current limits

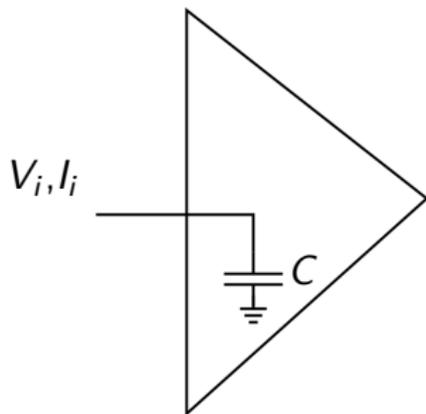

This is an equivalent circuit for a CMOS gate *input*.

Logic gate operating currents

Total power consumption

Interfacing families; CMOS to TTL and TTL to CMOS


Operating current limits

TTL connections


CMOS connections

# CMOS connections

# CMOS connections

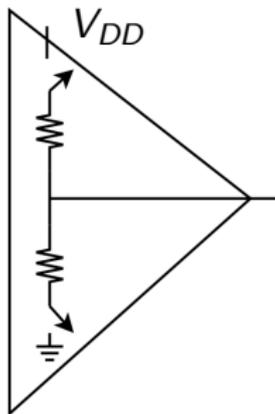


# CMOS connections

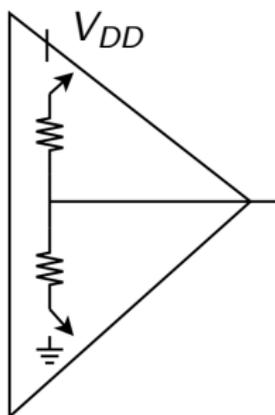


The equivalent circuit for a CMOS *output* is similar to TTL.

Here's what happens when a CMOS HIGH output feeds into another CMOS input.

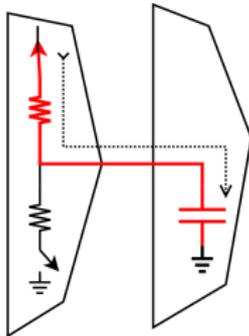Here's what happens when a CMOS HIGH output feeds into another CMOS input.




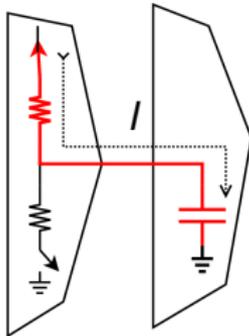Here's what happens when a CMOS HIGH output feeds into another CMOS input.



Current flows *out of* gate

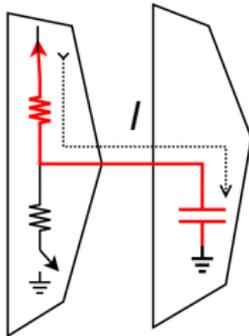Here's what happens when a CMOS HIGH output feeds into another CMOS input.




Current flows *out of* gate


Voltage must rise above  $V_{IH_{min}}$

Here's what happens when a CMOS LOW output feeds into another CMOS input.

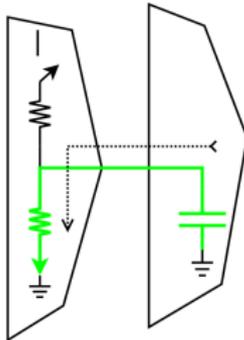Here's what happens when a CMOS LOW output feeds into another CMOS input.




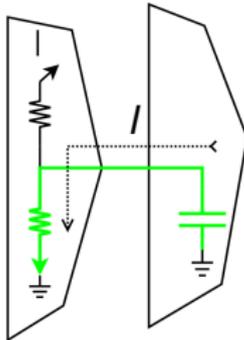Here's what happens when a CMOS LOW output feeds into another CMOS input.



Current flows *into* gate

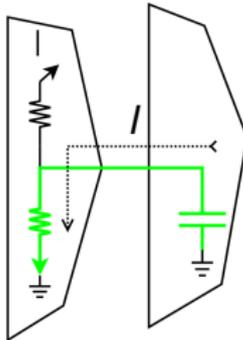Here's what happens when a CMOS LOW output feeds into another CMOS input.



Current flows *into* gate

Voltage must fall below  $V_{IL_{max}}$

For CMOS, even though the output equivalent circuit is similar to that of a TTL gate, when one gate is connected to another there is a limit to the *speed* at which the second gate will change due to the time it takes for the input capacitor to charge or discharge.

For CMOS, even though the output equivalent circuit is similar to that of a TTL gate, when one gate is connected to another there is a limit to the *speed* at which the second gate will change due to the time it takes for the input capacitor to charge or discharge.

Since the gate input is capacitive, then the current drawn from the previous gate will start big and get smaller as the capacitor reaches its intended voltage.

Logic gate operating currents

Total power consumption

Interfacing families; CMOS to TTL and TTL to CMOS

Operating current limits

TTL connections

CMOS connections

# CMOS

# CMOS

For CMOS, the symmetry of the internals means that the current needed to produce a high output is the same as the amount drawn by a low output.

# CMOS

For CMOS, the symmetry of the internals means that the current needed to produce a high output is the same as the amount drawn by a low output.

Thus there is only one quantity,

# CMOS

For CMOS, the symmetry of the internals means that the current needed to produce a high output is the same as the amount drawn by a low output.

Thus there is only one quantity,  $I_{DD_{max}}$

# Total power consumption

# Total power consumption

The power consumption of the device is given by

# Total power consumption

The power consumption of the device is given by

$$P = V_{supply} \times I_{total}$$

# Total power consumption

The power consumption of the device is given by

$$P = V_{supply} \times I_{total}$$

where  $I_{total}$  is the sum of the currents drawn by each of the gates on the device.

The power drawn by a circuit is the sum of the power drawn by each device in the circuit.

The power drawn by a circuit is the sum of the power drawn by each device in the circuit.

The supply must be able to provide as much as needed by the whole circuit.

# Quiescent current

# Quiescent current

As long as power is applied to a chip, it will be drawing a small amount of current.

Definition of terms can sometimes become tricky.

Definition of terms can sometimes become tricky.

An output limit, for instance, can be seen as either how much is guaranteed to be *supplied*, or as how much can be safely *demanded*.

Definition of terms can sometimes become tricky.

An output limit, for instance, can be seen as either how much is guaranteed to be *supplied*, or as how much can be safely *demanded*.

In other words, the limit can be seen as either belonging to the *device* or the the *surrounding* circuit.

Definition of terms can sometimes become tricky.

An output limit, for instance, can be seen as either how much is guaranteed to be *supplied*, or as how much can be safely *demanded*.

In other words, the limit can be seen as either belonging to the *device* or the the *surrounding* circuit.

While they are functionally equivalent, the first view will give a *minimum* for a quantity while the second will give a *maximum*.

Definition of terms can sometimes become tricky.

An output limit, for instance, can be seen as either how much is guaranteed to be *supplied*, or as how much can be safely *demanded*.

In other words, the limit can be seen as either belonging to the *device* or the the *surrounding* circuit.

While they are functionally equivalent, the first view will give a *minimum* for a quantity while the second will give a *maximum*.

Different manufacturers may take either view, and so it is important to understand this so that you can make sense of whichever you are given.

Four particular quantities are of interest in specifying the tolerance:

$$① I_{IL_{max}}$$

## 1 $I_{IL_{max}}$

the *maximum* input current which must be drawn from a gate's input to ground to guarantee the input will be low.

1  $I_{IL_{max}}$

the *maximum* input current which must be drawn from a gate's input to ground to guarantee the input will be low.

2  $I_{IH_{max}}$

1  $I_{IL_{max}}$

the *maximum* input current which must be drawn from a gate's input to ground to guarantee the input will be low.

2  $I_{IH_{max}}$

the *maximum* input current which must be supplied to a gate's input to guarantee the input will be high.

①  $I_{IL_{max}}$

the *maximum* input current which must be drawn from a gate's input to ground to guarantee the input will be low.

②  $I_{IH_{max}}$

the *maximum* input current which must be supplied to a gate's input to guarantee the input will be high.

③  $I_{OH_{max}}$

1  $I_{IL_{max}}$

the *maximum* input current which must be drawn from a gate's input to ground to guarantee the input will be low.

2  $I_{IH_{max}}$

the *maximum* input current which must be supplied to a gate's input to guarantee the input will be high.

3  $I_{OH_{max}}$

the *maximum* current which the gate can source through its output and still keep the output high.

1  $I_{IL_{max}}$

the *maximum* input current which must be drawn from a gate's input to ground to guarantee the input will be low.

2  $I_{IH_{max}}$

the *maximum* input current which must be supplied to a gate's input to guarantee the input will be high.

3  $I_{OH_{max}}$

the *maximum* current which the gate can source through its output and still keep the output high.

4  $I_{OL_{max}}$

1  $I_{IL_{max}}$

the *maximum* input current which must be drawn from a gate's input to ground to guarantee the input will be low.

2  $I_{IH_{max}}$

the *maximum* input current which must be supplied to a gate's input to guarantee the input will be high.

3  $I_{OH_{max}}$

the *maximum* current which the gate can source through its output and still keep the output high.

4  $I_{OL_{max}}$

the *maximum* current which the gate can sink through its output and still keep the output low.

$I_{IL_{max}}$  and  $I_{IH_{max}}$  may require some explanation.

$I_{IL_{max}}$  and  $I_{IH_{max}}$  may require some explanation.

Most people assume that if the inputs of a gate are not attached to anything they will be treated as logic low.

$I_{IL_{max}}$  and  $I_{IH_{max}}$  may require some explanation.

Most people assume that if the inputs of a gate are not attached to anything they will be treated as logic low.

This is a bad assumption.

$I_{IL_{max}}$  and  $I_{IH_{max}}$  may require some explanation.

Most people assume that if the inputs of a gate are not attached to anything they will be treated as logic low.

This is a bad assumption.

An important piece of information about various logic families is what happens when inputs are left to **float**; i.e. remain unconnected.

$I_{IL_{max}}$  and  $I_{IH_{max}}$  may require some explanation.

Most people assume that if the inputs of a gate are not attached to anything they will be treated as logic low.

This is a bad assumption.

An important piece of information about various logic families is what happens when inputs are left to **float**; i.e. remain unconnected.

They may float high, low or anywhere in between.

$I_{IL_{max}}$  and  $I_{IH_{max}}$  may require some explanation.

Most people assume that if the inputs of a gate are not attached to anything they will be treated as logic low.

This is a bad assumption.

An important piece of information about various logic families is what happens when inputs are left to **float**; i.e. remain unconnected.

They may float high, low or anywhere in between.

To have an input recognized as something other than its “floating” state will require that a finite amount of current be either supplied to the input (to make it high) or drawn from the input to ground (to make it low.)

$I_{IL_{max}}$  and  $I_{IH_{max}}$  may require some explanation.

Most people assume that if the inputs of a gate are not attached to anything they will be treated as logic low.

This is a bad assumption.

An important piece of information about various logic families is what happens when inputs are left to **float**; i.e. remain unconnected.

They may float high, low or anywhere in between.

To have an input recognized as something other than its “floating” state will require that a finite amount of current be either supplied to the input (to make it high) or drawn from the input to ground (to make it low.)

*Never assume anything about unconnected inputs.*

$I_{IL_{max}}$  and  $I_{IH_{max}}$  may require some explanation.

Most people assume that if the inputs of a gate are not attached to anything they will be treated as logic low.

This is a bad assumption.

An important piece of information about various logic families is what happens when inputs are left to **float**; i.e. remain unconnected.

They may float high, low or anywhere in between.

To have an input recognized as something other than its “floating” state will require that a finite amount of current be either supplied to the input (to make it high) or drawn from the input to ground (to make it low.)

*Never assume anything about unconnected inputs.*

*If you want them to be in a particular state, tie them that way.*

These current limits are referred to as the *fan-in* and *fan-out* characteristics of digital circuits.

These current limits are referred to as the *fan-in* and *fan-out* characteristics of digital circuits.

*Note that a given gate will occasionally have zero for either  $I_{IL_{max}}$  or  $I_{IH_{max}}$ .*

# Interfacing families; CMOS to TTL and TTL to CMOS

# Interfacing families; CMOS to TTL and TTL to CMOS

Because different families have different current and voltage requirements, they can't simply be mixed as though they were all the same.

# Interfacing families; CMOS to TTL and TTL to CMOS

Because different families have different current and voltage requirements, they can't simply be mixed as though they were all the same.

Each gate must stay within its required operating parameters.