

Electronics

Logic Gate Characteristics: Voltage

Terry Sturtevant

Wilfrid Laurier University

February 5, 2014

Ideal logic gates

Real logic gates

Logic families

Determining device limits

Noise Immunity

Ideal logic gates

Ideal logic gates

- In PC/CP120, logic gates are treated as “ideal” devices.

Ideal logic gates

- In PC/CP120, logic gates are treated as “ideal” devices.
As well, only one or perhaps two logic families were discussed.

Ideal logic gates

- In PC/CP120, logic gates are treated as “ideal” devices.
As well, only one or perhaps two logic families were discussed.
- Now the real (i.e. non-ideal) operating characteristics of different logic families will be studied.

Ideal logic gates

- In PC/CP120, logic gates are treated as “ideal” devices.
As well, only one or perhaps two logic families were discussed.
- Now the real (i.e. non-ideal) operating characteristics of different logic families will be studied.
- The operation of an *ideal* logic gate can be summarized by the following rules:

- Input and output voltages will be at either the *high* or the *low* value specified for that family; (eg. 5 and 0 volts, respectively for TTL)

- Input and output voltages will be at either the *high* or the *low* value specified for that family; (eg. 5 and 0 volts, respectively for TTL)
- Inputs will draw no current from whatever drives them, and outputs can supply as much current as necessary for whatever follows.

- Input and output voltages will be at either the *high* or the *low* value specified for that family; (eg. 5 and 0 volts, respectively for TTL)
- Inputs will draw no current from whatever drives them, and outputs can supply as much current as necessary for whatever follows.
- Any change of an input will immediately be reflected on the output.

Ideal logic gates

Real logic gates

Logic families

Determining device limits

Noise Immunity

Reading Data sheets

Real logic gates

Real logic gates

In practice, these rules do not hold.

Real logic gates

In practice, these rules do not hold.

A *real* logic gate operates under the following restrictions:

- Input voltages will not always be at ideal values

- Input voltages will not always be at ideal values
a *range* of input values must be considered *high*

- Input voltages will not always be at ideal values
a *range* of input values must be considered *high*
another range of input values must be considered *low*.

- Input voltages will not always be at ideal values
a *range* of input values must be considered *high*
another range of input values must be considered *low*.
- Similarly output voltages will not always be at ideal values

- Input voltages will not always be at ideal values
a *range* of input values must be considered *high*
another range of input values must be considered *low*.
- Similarly output voltages will not always be at ideal values
a *range* of output voltages should be considered as *high*

- Input voltages will not always be at ideal values
a *range* of input values must be considered *high*
another range of input values must be considered *low*.
- Similarly output voltages will not always be at ideal values
a *range* of output voltages should be considered as *high*
another *range* of output voltages should be considered *low*.

- Input voltages will not always be at ideal values
a *range* of input values must be considered *high*
another range of input values must be considered *low*.
- Similarly output voltages will not always be at ideal values
a *range* of output voltages should be considered as *high*
another *range* of output voltages should be considered *low*.
- Changes made at the inputs will take a finite amount of time
to be reflected on the outputs.

- Input voltages will not always be at ideal values
a *range* of input values must be considered *high*
another range of input values must be considered *low*.
- Similarly output voltages will not always be at ideal values
a *range* of output voltages should be considered as *high*
another *range* of output voltages should be considered *low*.
- Changes made at the inputs will take a finite amount of time
to be reflected on the outputs.
- Inputs must draw a small but finite amount of current from
whatever is driving them in order that they will be recognized.

- Input voltages will not always be at ideal values
a *range* of input values must be considered *high*
another range of input values must be considered *low*.
- Similarly output voltages will not always be at ideal values
a *range* of output voltages should be considered as *high*
another *range* of output voltages should be considered *low*.
- Changes made at the inputs will take a finite amount of time
to be reflected on the outputs.
- Inputs must draw a small but finite amount of current from
whatever is driving them in order that they will be recognized.
- Outputs have a limited current capacity for maintaining the
output voltage at the desired level.

Ideal logic gates

Real logic gates

Logic families

Determining device limits

Noise Immunity


Reading Data sheets

Real logic gates

Ideal logic gates
Real logic gates
Logic families
Determining device limits
Noise Immunity

Reading Data sheets


Real logic gates

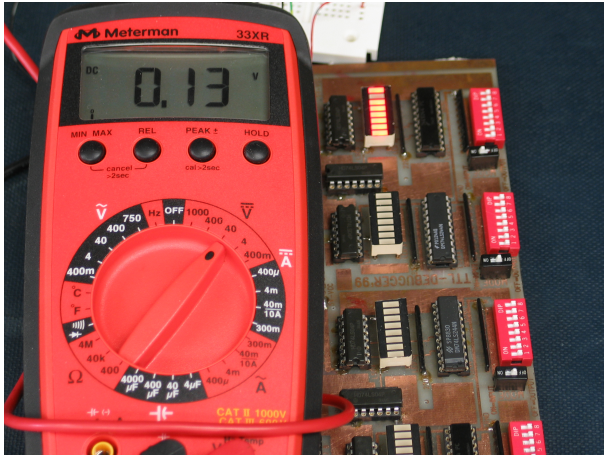

Ideal logic gates
Real logic gates
Logic families
Determining device limits
Noise Immunity

Reading Data sheets


Real logic gates

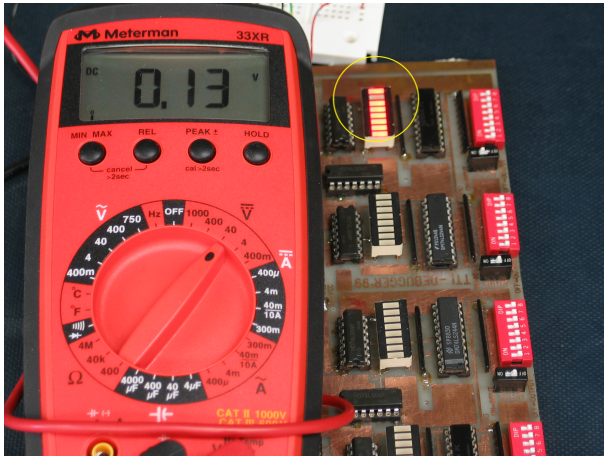

Ideal logic gates
Real logic gates
Logic families
Determining device limits
Noise Immunity

Reading Data sheets


Real logic gates

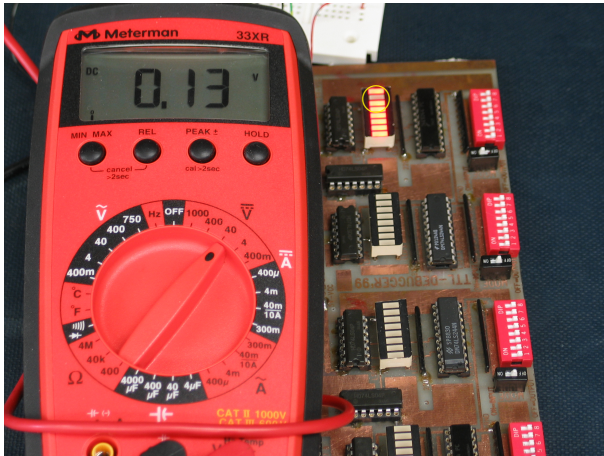

Ideal logic gates
Real logic gates
Logic families
Determining device limits
Noise Immunity

Reading Data sheets


Real logic gates

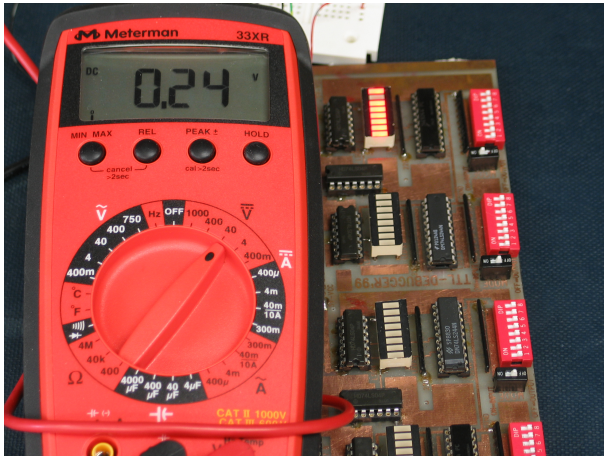

Ideal logic gates
Real logic gates
Logic families
Determining device limits
Noise Immunity

Reading Data sheets


Real logic gates

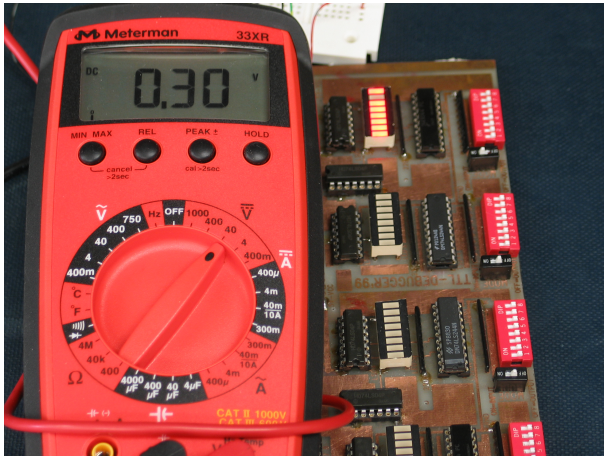

Ideal logic gates
Real logic gates
Logic families
Determining device limits
Noise Immunity

Reading Data sheets


Real logic gates

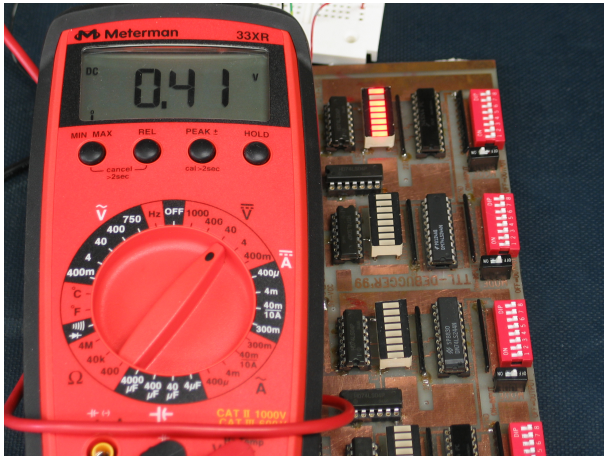

Ideal logic gates
Real logic gates
Logic families
Determining device limits
Noise Immunity

Reading Data sheets


Real logic gates

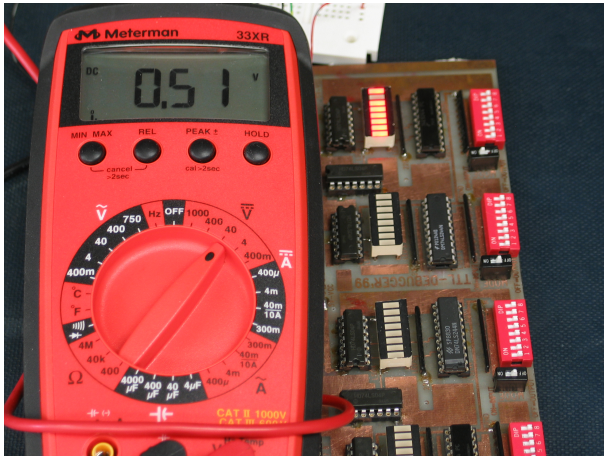

Ideal logic gates
Real logic gates
Logic families
Determining device limits
Noise Immunity

Reading Data sheets


Real logic gates

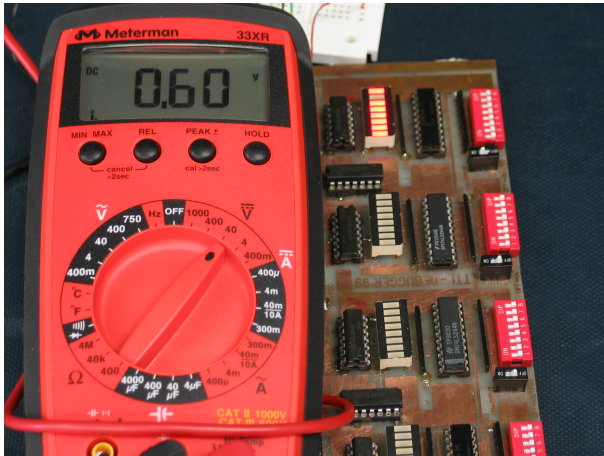

Ideal logic gates
Real logic gates
Logic families
Determining device limits
Noise Immunity

Reading Data sheets


Real logic gates

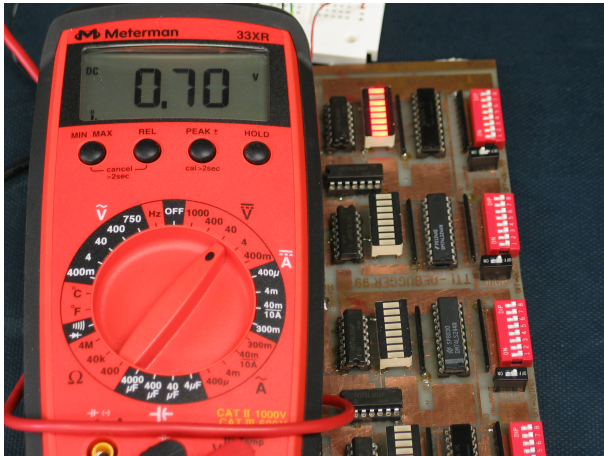

Ideal logic gates
Real logic gates
Logic families
Determining device limits
Noise Immunity

Reading Data sheets


Real logic gates

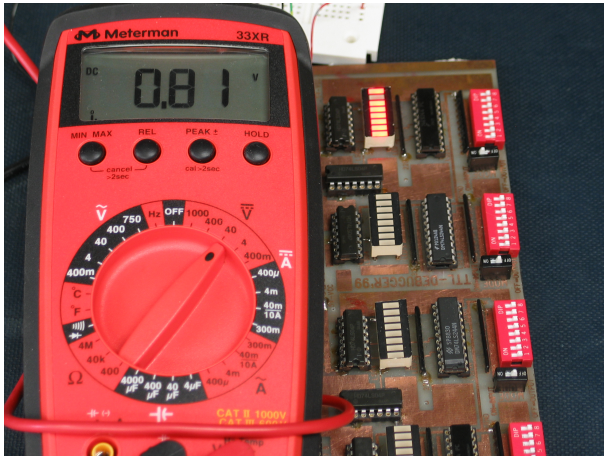

Ideal logic gates
Real logic gates
Logic families
Determining device limits
Noise Immunity

Reading Data sheets


Real logic gates

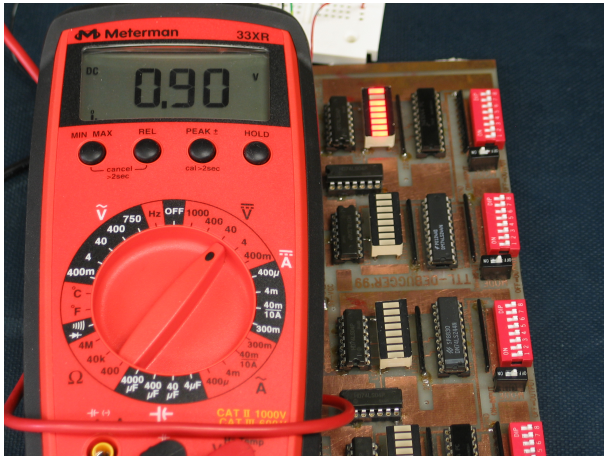

Ideal logic gates
Real logic gates
Logic families
Determining device limits
Noise Immunity

Reading Data sheets


Real logic gates

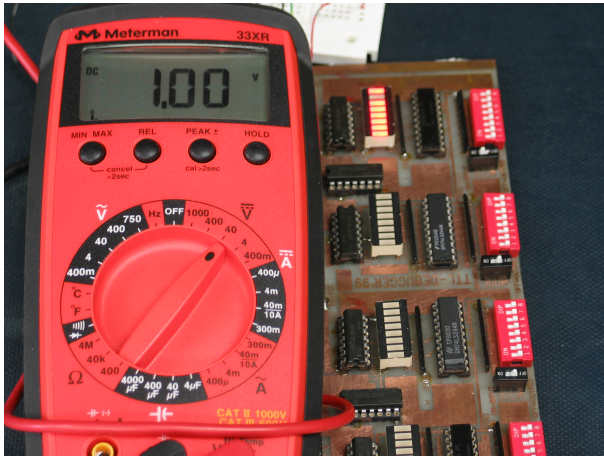

Ideal logic gates
Real logic gates
Logic families
Determining device limits
Noise Immunity

Reading Data sheets


Real logic gates

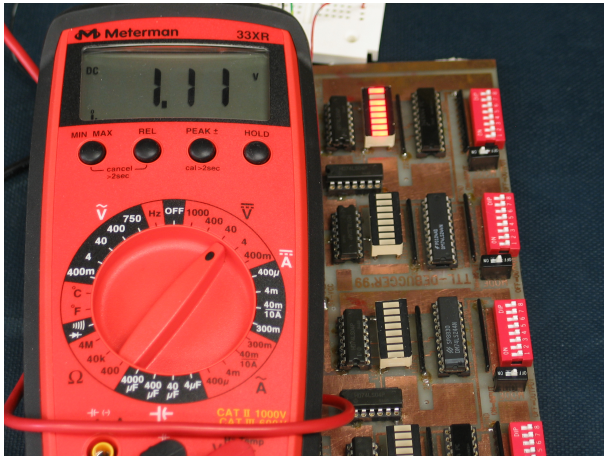

Ideal logic gates
Real logic gates
Logic families
Determining device limits
Noise Immunity

Reading Data sheets


Real logic gates

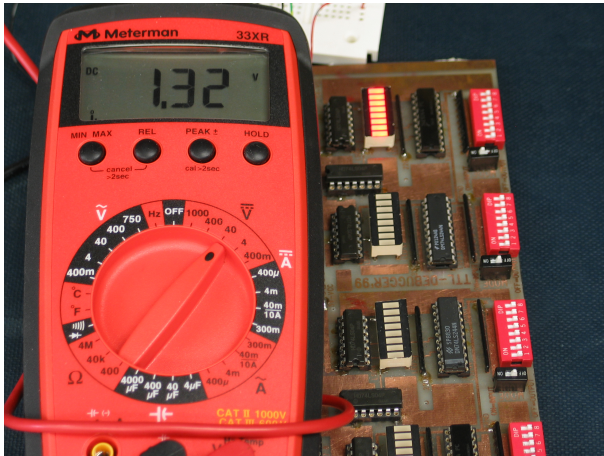

Ideal logic gates
Real logic gates
Logic families
Determining device limits
Noise Immunity

Reading Data sheets


Real logic gates

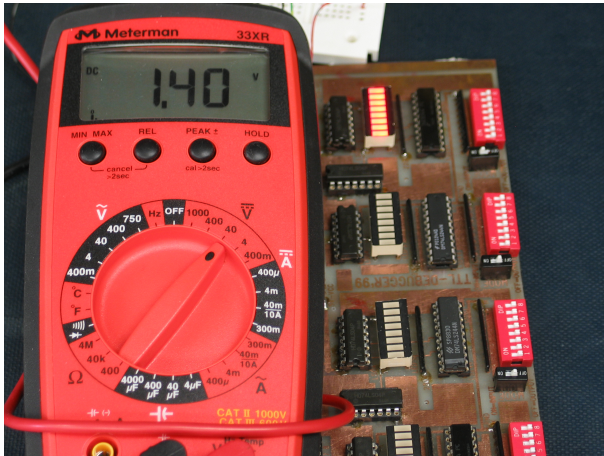

Ideal logic gates
Real logic gates
Logic families
Determining device limits
Noise Immunity

Reading Data sheets

Real logic gates

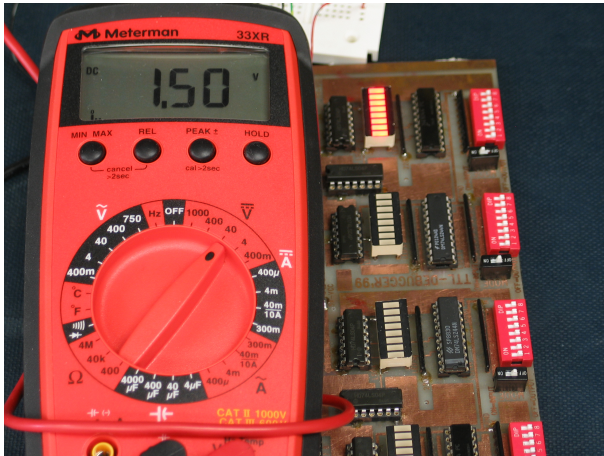

Ideal logic gates

Real logic gates

Logic families

Determining device limits

Noise Immunity


Reading Data sheets

More detail

Ideal logic gates
Real logic gates
Logic families
Determining device limits
Noise Immunity

Reading Data sheets


More detail

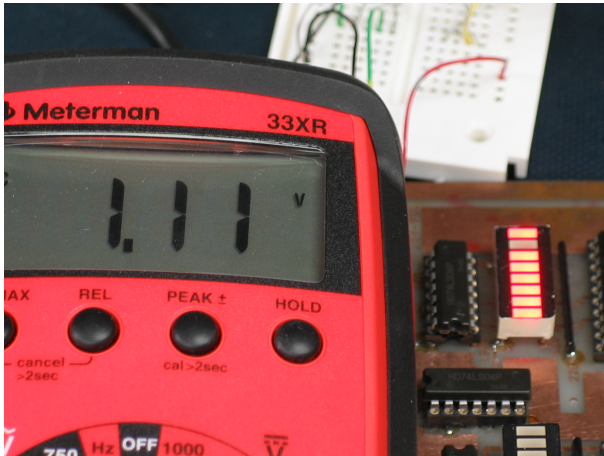

Ideal logic gates
Real logic gates
Logic families
Determining device limits
Noise Immunity

Reading Data sheets


More detail

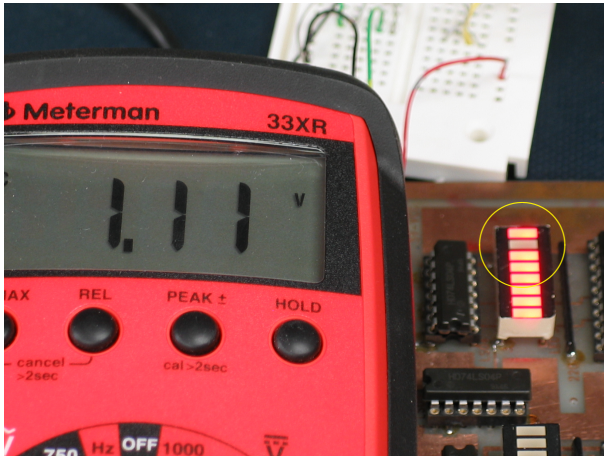

Ideal logic gates
Real logic gates
Logic families
Determining device limits
Noise Immunity

Reading Data sheets


More detail

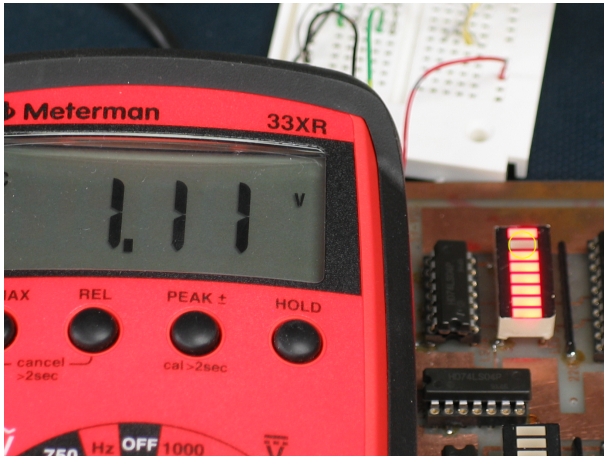

Ideal logic gates
Real logic gates
Logic families
Determining device limits
Noise Immunity

Reading Data sheets


More detail

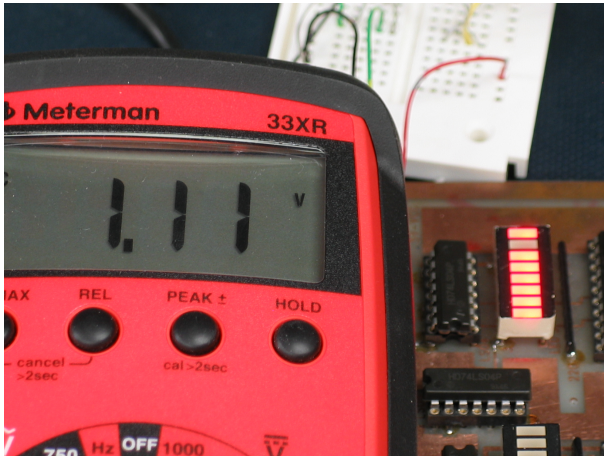

Ideal logic gates
Real logic gates
Logic families
Determining device limits
Noise Immunity

Reading Data sheets

More detail

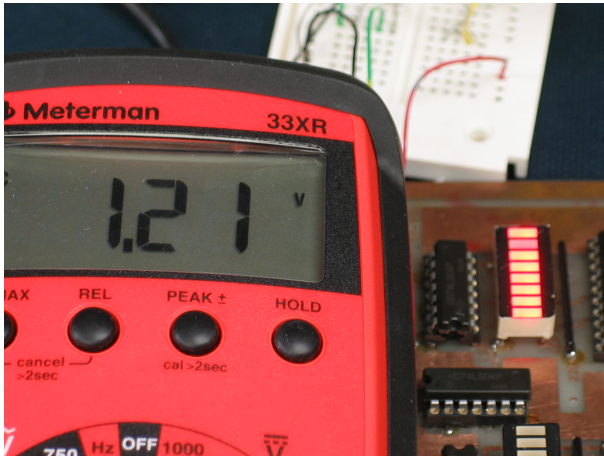

Ideal logic gates
Real logic gates
Logic families
Determining device limits
Noise Immunity

Reading Data sheets

More detail



Ideal logic gates

Real logic gates

Logic families

Determining device limits

Noise Immunity

Reading Data sheets

Reading Data sheets

Reading Data sheets

The actual limits on voltage, current, timing, etc. will be given in manufacturer's **data sheets**.

Reading Data sheets

The actual limits on voltage, current, timing, etc. will be given in manufacturer's **data sheets**.

Different manufacturers arrange their data sheets differently, and use different names.

Logic families

Logic families

- The real limitations on *voltages*, *timing*, and *currents* depend on the *logic family* involved.

Logic families

- The real limitations on *voltages*, *timing*, and *currents* depend on the *logic family* involved.

Note that usually comparing “real” to “ideal” values involves seeing how close one number, (the “real” value) is to another (the “ideal” value).

Logic families

- The real limitations on *voltages*, *timing*, and *currents* depend on the *logic family* involved.

Note that usually comparing “real” to “ideal” values involves seeing how close one number, (the “real” value) is to another (the “ideal” value).

- *With digital logic chips, however, rather than having a single “ideal” value for a parameter, the manufacturers give **bounds** for it instead.*

Logic families

- The real limitations on *voltages*, *timing*, and *currents* depend on the *logic family* involved.

Note that usually comparing “real” to “ideal” values involves seeing how close one number, (the “real” value) is to another (the “ideal” value).

- *With digital logic chips, however, rather than having a single “ideal” value for a parameter, the manufacturers give **bounds** for it instead.*

*This is because these **specifications** are not values that should be matched, but rather they are values that should be considered as limits that one should achieve even in the “worst case” during real operation.*

- *For instance, if a family has a nominal input “high” voltage of 5 volts, then any voltage above some voltage will be considered “high”.*

- *For instance, if a family has a nominal input “high” voltage of 5 volts, then any voltage above some voltage will be considered “high”.*

If an actual gate accepts a slightly lower voltage as a high, then that is not surprising and in fact is desirable.

Note that for some parameters the specifications will give an *upper* bound while for some they will give a *lower* bound.

Note that for some parameters the specifications will give an *upper* bound while for some they will give a *lower* bound. Which one is given will make sense if you understand what each parameter means.

Supply voltage Designations

Supply voltage Designations

- The supply voltages for various families have names which are based on the type of transistors used in their construction.

Supply voltage Designations

- The supply voltages for various families have names which are based on the type of transistors used in their construction. For instance, TTL gates are made with **bipolar** transistors, which have a **collector** and an **emitter**, the supply voltages are V_{CC} and GROUND is occasionally given as V_{EE} .

Supply voltage Designations

- The supply voltages for various families have names which are based on the type of transistors used in their construction. For instance, TTL gates are made with **bipolar** transistors, which have a **collector** and an **emitter**, the supply voltages are V_{CC} and GROUND is occasionally given as V_{EE} .
- On the other hand, CMOS gates are built with **field-effect** transistors which have a **drain** and a **source**, the supply voltages are V_{DD} and V_{SS} .

TTL Voltage Limits

TTL Voltage Limits

While the *ideal* voltage in TTL circuits are 0 (logic 0) and +5 volts (logic 1), the typical, or observed, voltages are different in practice.

TTL Voltage Limits

While the *ideal* voltage in TTL circuits are 0 (logic 0) and +5 volts (logic 1), the typical, or observed, voltages are different in practice. It is important to know what **tolerances** must be observed in order to guarantee the correct operation of a digital circuit.

TTL Voltage Limits

While the *ideal* voltage in TTL circuits are 0 (logic 0) and +5 volts (logic 1), the typical, or observed, voltages are different in practice. It is important to know what **tolerances** must be observed in order to guarantee the correct operation of a digital circuit. Four particular quantities are of interest in specifying the tolerance:

- $V_{IH_{min}}$

- $V_{IH_{min}}$
the *minimum* input voltage which will be accepted as a logic 1.

- $V_{IH_{min}}$
the *minimum* input voltage which will be accepted as a logic 1.
- $V_{IL_{max}}$

- $V_{IH_{min}}$
the *minimum* input voltage which will be accepted as a logic 1.
- $V_{IL_{max}}$
the *maximum* input voltage which will be accepted as a logic 0.

- $V_{IH_{min}}$
the *minimum* input voltage which will be accepted as a logic 1.
- $V_{IL_{max}}$
the *maximum* input voltage which will be accepted as a logic 0.
- $V_{OH_{min}}$

- $V_{IH_{min}}$
the *minimum* input voltage which will be accepted as a logic 1.
- $V_{IL_{max}}$
the *maximum* input voltage which will be accepted as a logic 0.
- $V_{OH_{min}}$
the *minimum* output voltage representing a logic 1 state.

- $V_{IH_{min}}$
the *minimum* input voltage which will be accepted as a logic 1.
- $V_{IL_{max}}$
the *maximum* input voltage which will be accepted as a logic 0.
- $V_{OH_{min}}$
the *minimum* output voltage representing a logic 1 state.
- $V_{OL_{max}}$

- $V_{IH_{min}}$
the *minimum* input voltage which will be accepted as a logic 1.
- $V_{IL_{max}}$
the *maximum* input voltage which will be accepted as a logic 0.
- $V_{OH_{min}}$
the *minimum* output voltage representing a logic 1 state.
- $V_{OL_{max}}$
the *maximum* output voltage representing a logic 0 state.


For the 3 logic families to be studied, the *specified* values of these parameters are given in the following table.

For the 3 logic families to be studied, the *specified* values of these parameters are given in the following table. In other words, real gates should perform *at least as well* as the values listed.

Family	$V_{IH_{min}}$	$V_{IL_{max}}$	$V_{OH_{min}}$	$V_{OL_{max}}$
TTL	2.0	0.8	2.4	0.4
LSTTL	2.0	0.8	2.7	0.5
CMOS	$0.7V_{DD}$	$0.3V_{DD}$	$0.99V_{DD}$	$0.01V_{DD}$
$V_{DD}=5V$	3.5	1.5	4.95	0.05

What the above information means is that, (for instance), if both *inputs* to a 7400 TTL NAND gate are at greater than or equal to 2.4 volts, they will be considered “high”, and so the *output* should be “low”,

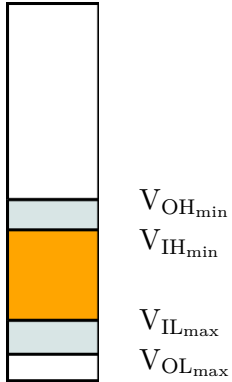What the above information means is that, (for instance), if both *inputs* to a 7400 TTL NAND gate are at greater than or equal to 2.4 volts, they will be considered “high”, and so the *output* should be “low”, i.e. at a voltage less than or equal to 0.4 volts.



TTL



$V_{OL_{max}}$



Anything below here is a valid LOW *output*

TTL



$V_{IL_{max}}$



Anything below here is a valid LOW *input*

TTL



$V_{IH_{min}}$

Anything above here is a valid HIGH *input*

TTL



$V_{OH_{min}}$



Anything above here is a valid HIGH *output*

TTL



$V_{OH_{min}}$



Anything above here is a valid HIGH *output*

$V_{OL_{max}}$



Anything below here is a valid LOW *output*

TTL



$V_{IH_{min}}$


$V_{IL_{max}}$



Anything above here is a valid HIGH *input*

Anything below here is a valid LOW *input*

TTL

 

$V_{OH_{min}}$

$V_{IH_{min}}$

$V_{IL_{max}}$

$V_{OL_{max}}$

CMOS

CMOS logic

CMOS logic

Note: For CMOS logic V_{DD} can be as low as 3.5V and as high as 15V.

Noise immunity

Noise immunity

- For each logic family, you should notice that the *output* voltage limits are more stringent than the *input* voltage limits.

Noise immunity


- For each logic family, you should notice that the *output* voltage limits are more stringent than the *input* voltage limits. This is to provide **noise immunity** to the devices.

Noise immunity

- For each logic family, you should notice that the *output* voltage limits are more stringent than the *input* voltage limits. This is to provide **noise immunity** to the devices. In other words, if a bit of noise (i.e. voltage fluctuation) were added to the output of one gate, it should not affect a gate which follows this one.

Noise immunity

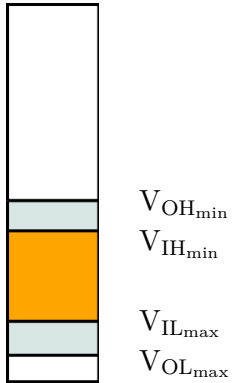- For each logic family, you should notice that the *output* voltage limits are more stringent than the *input* voltage limits. This is to provide **noise immunity** to the devices. In other words, if a bit of noise (i.e. voltage fluctuation) were added to the output of one gate, it should not affect a gate which follows this one.
- Imagine what would happen if the limits were the same.



TTL



$V_{OH_{min}}$

$V_{IH_{min}}$

$V_{IL_{max}}$

$V_{OL_{max}}$

Output here will still be seen as HIGH

TTL



$V_{OH_{min}}$


$V_{IH_{min}}$

$V_{IL_{max}}$


$V_{OL_{max}}$

Output here will still be seen as LOW

TTL

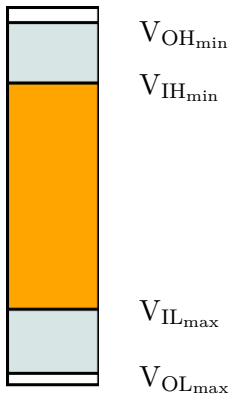

CMOS

 

$V_{OH_{min}}$


$V_{IH_{min}}$

$V_{IL_{max}}$

$V_{OL_{max}}$


Output here will still be seen as HIGH

CMOS

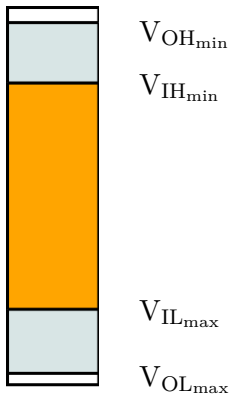


CMOS


Output here will still be seen as LOW

 


Consider one gate feeding into another.

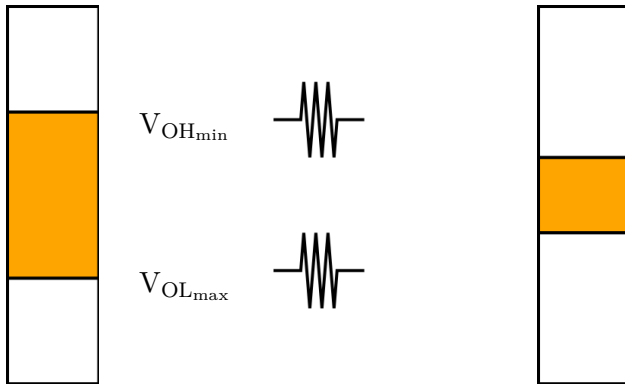

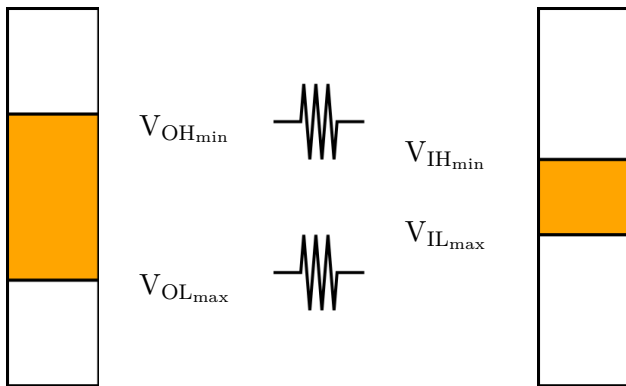If a signal gets *noise* added to it, the voltage will fluctuate up and down.



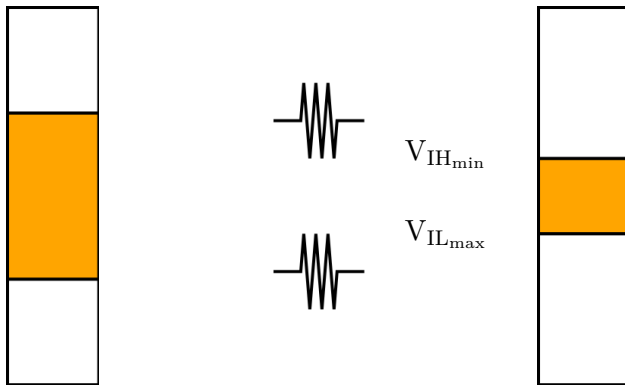A certain amount of noise will still leave the resulting signal within the *input* limits of the second gate.



The difference between the output and input limits is the **noise immunity**.