

Transient Process for RLC Circuit

Purpose

1. Observe the transient process for RLC circuit
2. Study the transient characteristics for RLC circuit

Theory

For a circuit contained a resistor R, a capacitor C and an inductor L, when the voltage of source changes suddenly from 0 to E volts the voltage or current of the circuit can't respond it immediately. It performs a transient process.

1. A simple RC circuit

As shown in Figure 1, a simple RC circuit is supplied by a source voltage $u(t)$ which is a square signal jumped from 0 to E or vice versa. The circuit equation is described as:

$$iR + u_c = E \quad (1)$$

where u_c is the voltage across the capacitor, and i is the AC current passing through the capacitor and equals to

$$i = c \frac{du_c}{dt} \quad (2)$$

The solution of Equation (1) is:

$$u_c = E(1 - e^{-\frac{t}{RC}}) \quad (3)$$

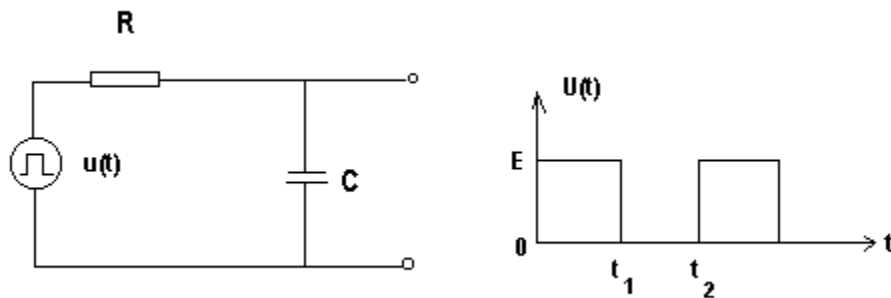


Figure 1 A simple RC circuit and its source voltage

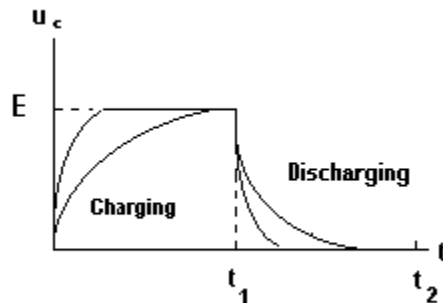


Figure 2 The voltage changed on the capacitor

It tells us that u_c increases exponentially when charging and decreases exponentially when discharging as shown in Figure 2.

2. A series RLC circuit

Figure 3 is a RLC circuit described by the following equation:

$$L \frac{d^2 u_c}{dt^2} + R \frac{du_c}{dt} + \frac{1}{C} u_c = 0 \quad (3)$$

The solution of Equation (3) is:

$$u_c = E e^{-\frac{t}{\tau}} \cos \omega t \quad (4)$$

where τ is a time constant determined by

$$\tau = \frac{2L}{R} \quad (5)$$

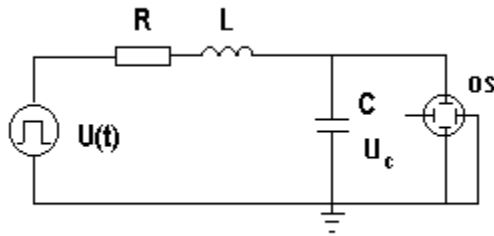


Figure 3 A RLC circuit

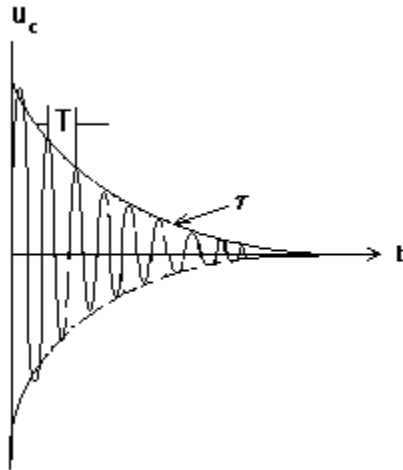


Figure 4 The transient voltage u_c across capacitor for a RLC circuit

In Equation (4), ω is the natural resonant frequency determined by:

$$\omega = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} \quad (5)$$

Figure 4 shows the transient respond of the series RLC circuit on the capacitor. Figure 5 is a typical waveform observed from the oscilloscope. We can determine τ and ω based on the waveform using the following method. As shown in Figure 5, when $t=t_n$ the amplitude of oscillation u_n can be expressed as:

$$u_n = Ee^{-\frac{t_n}{\tau}} \cos \omega t_n \quad (6)$$

Assuming that the period of oscillation is T, when $t=t_n+NT$ the amplitude of oscillation u_{n+NT} then becomes:

$$u_{n+NT} = Ee^{-\frac{t_n+NT}{\tau}} \cos \omega(t_n + NT) \quad (7)$$

where

$$\omega(t_n + NT) = \omega t_n + 2\pi N \quad (8)$$

Therefore, Equation (7) becomes then

$$u_{n+NT} = Ee^{-\frac{t_n+NT}{\tau}} \cos \omega t_n \quad (9)$$

Taking the ratio of Equation (9) and (6), we find that:

$$\frac{u_{n+NT}}{u_n} = e^{-\frac{NT}{\tau}} \quad (10)$$

Then the time constant τ can be easily determined as:

$$\tau = \frac{-NT}{\ln\left(\frac{u_{n+NT}}{u_n}\right)} \quad (11)$$

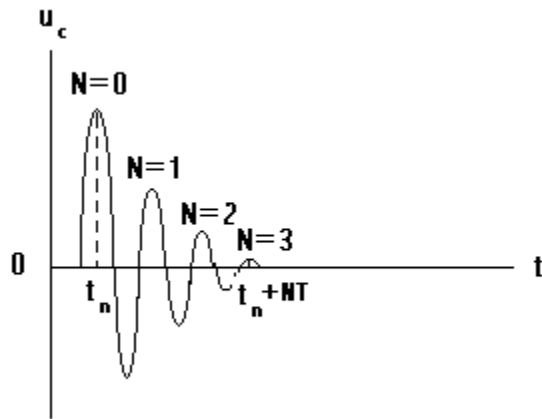


Figure 5 Determining τ and ω from the a waveform

Apparatus

1. Oscilloscope with two channels
2. Square signal generator
3. Inductor
4. Capacitor
5. Resistor box

Procedure

1. A simple RC circuit
 - a. Observe charging and discharging for a RC circuit
 - Construct the apparatus according to Figure 1
 - Use square signal generator with $f=100\text{Hz}$ as $u(t)$ (If f is too high, what will happen?)
 - Take $C=0.1\mu\text{F}$, and $R=300\Omega$, $1\text{K}\Omega$ and $3\text{K}\Omega$ respectively
 - Set input as DC for oscilloscope
 - Use oscilloscope to observe both u_c and u_R by two channels shown in Figure 6
 - Sketch $u_c \sim t$ and $u_R \sim t$ for three different resistances
 - b. Determine the time constants τ , and compare the experiment values with theoretical ones

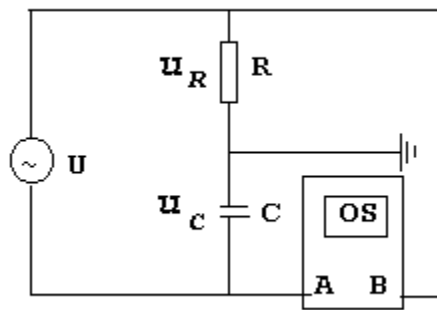


Figure 6 Measuring u_c and u_R

2. A series RLC circuit
 - a. Study the transient process for the RLC circuit
 - Construct the apparatus according to Figure 3
 - Use square signal generator with $f=100\text{Hz}$ as $u(t)$ (If f is too high or too low, what will happen?)
 - Take $C=4700\text{pF}$, $L=0.6$ or 0.3 H and $R=R_0+R_L+R_M$. R_M -the internal resistance of generator (usually 50Ω), R_L -the impedance of the inductor, R_0 -the resistance of the box. Make sure $R^2 < 4L/C$, otherwise, see what will happen
 - Sketch the oscillation waveform
 - Calculate τ and ω by using Equation (11) when setting $R_0=0$
 - Calculate R_L if $R_0=0$ and $R_M=50\Omega$ by using Equation (5)
 - b. Increase the resistance until no oscillation can be seen

