

PC221 Analog Electronics AC Circuits Lab Checklist (2.1)

1. Schematic  
(from LTspice or CircuitLab) \_\_\_\_\_
2. DC Voltages and currents  
(analysis, meter, scope, simulation) \_\_\_\_\_
3. AC Voltages and currents  
(analysis, meter, scope, simulation) \_\_\_\_\_
4. Transient analysis trace / waveform sketch  
(from LTspice or CircuitLab and scope) \_\_\_\_\_
5. Comments on results  
(i.e. similarities and differences) \_\_\_\_\_