

PC221 Analog Electronics Diode Lab Checklist (2.1)

1. Schematic
(from simulation) _____
2. IV graph and sketch
(from measurements) _____
3. IV graph and transient trace
(from simulation) _____
4. Comments on results
(i.e. similarities and differences) _____
5. Question
(Diode operation as expected?) _____