

# Electronics

## Operational Amplifier Dynamic Characteristics

Terry Sturtevant

Wilfrid Laurier University

September 4, 2014

# Op amp frequency response

# Op amp frequency response

- The gain of an op amp is not the same at all frequencies.

# Op amp frequency response

- The gain of an op amp is not the same at all frequencies.
- The **open loop gain** is the gain without feedback.

# Op amp frequency response

- The gain of an op amp is not the same at all frequencies.
- The **open loop gain** is the gain without feedback.
- Open loop gain is constant at low frequencies,

## Op amp frequency response


- The gain of an op amp is not the same at all frequencies.
- The **open loop gain** is the gain without feedback.
- Open loop gain is constant at low frequencies, but then starts to decrease at higher frequencies.

6V

4V

6V

4V

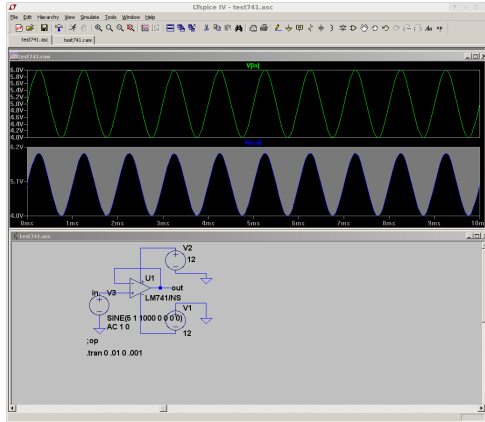


Here's a voltage follower with a 1 kHz input.

6V

4V

6V

4V

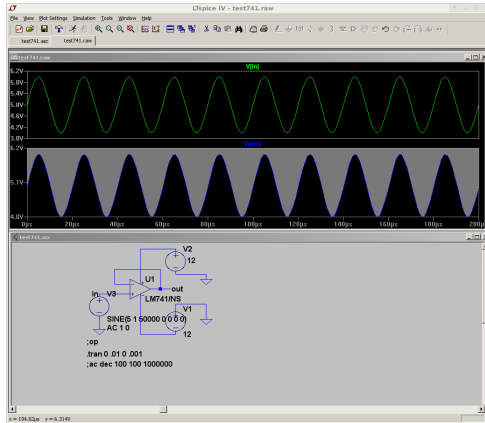

With a 50 kHz input, the output still matches pretty closely.




6V

4V


6V

4V

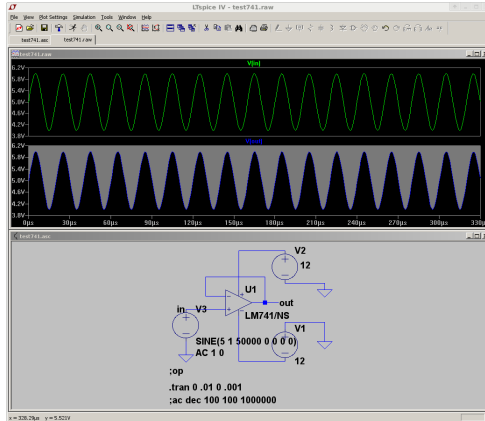

Here it is on the same scale.

6V  
4V  
5.8V  
4.2V

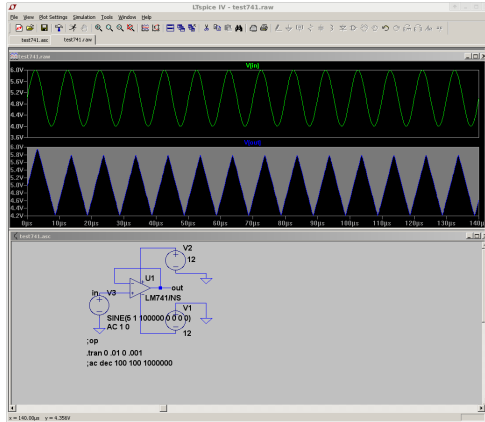


By 100kHz, the output is starting to diverge from the input.

6V

4V


6V

4V

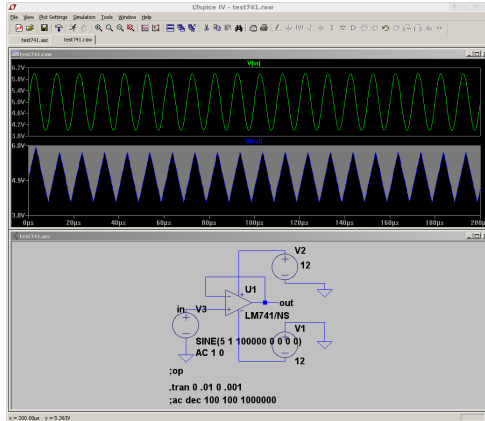

It's more obvious if the scales are the same.

6V  
4V  
5.4V  
4.8V

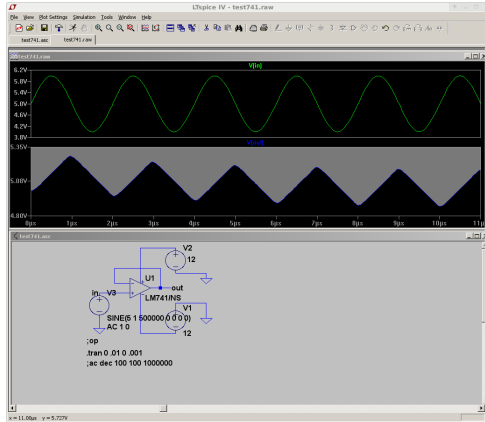


With a 500kHz input, the output change is very clear.

6V

4V

6V


4V

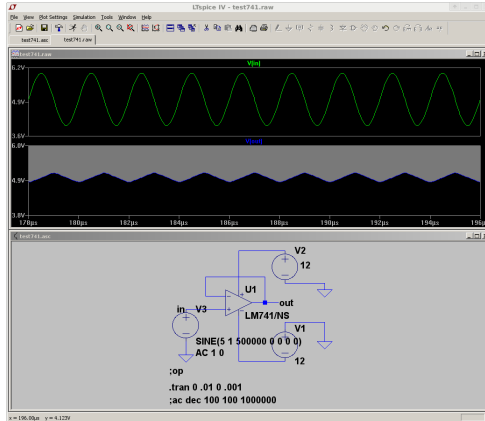


On the same scale, it's obvious.

The **rolloff** can be seen in the next figures.

100mV  
1V

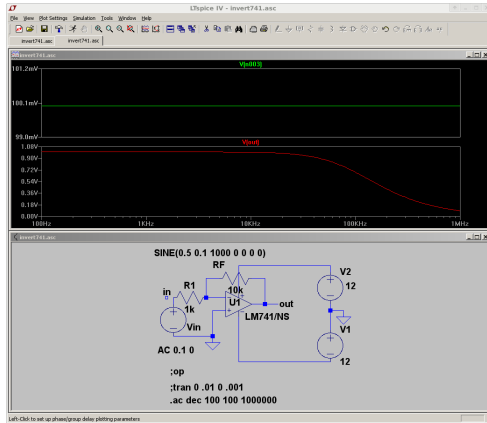

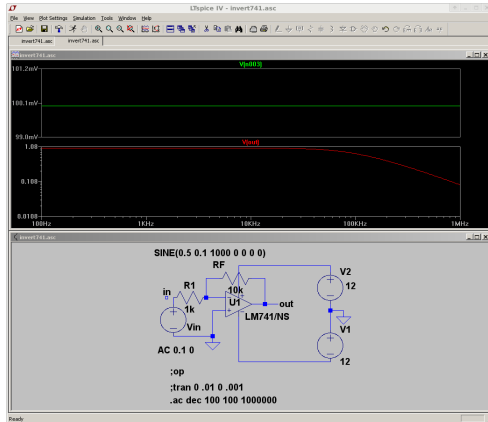
Here's what an AC analysis shows for a gain of 10.





A logarithmic scale is helpful sometimes.




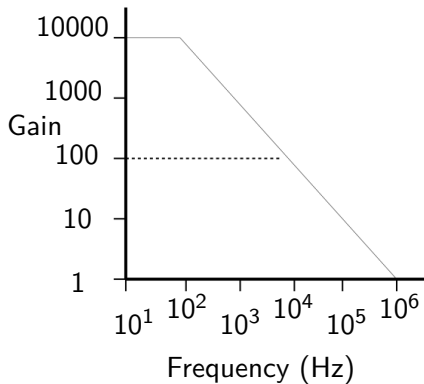
The **rolloff** affects both open-loop and closed-loop gain.




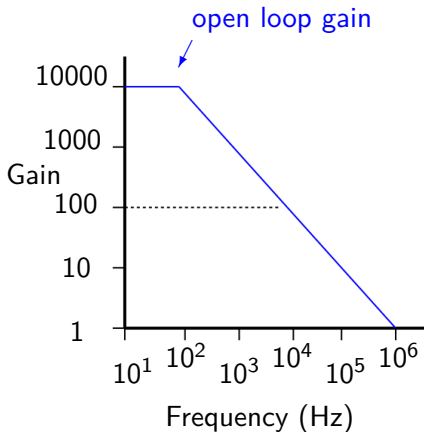

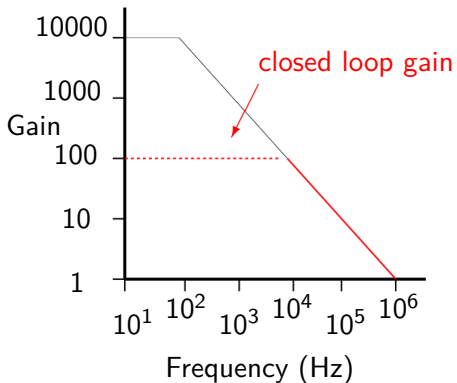

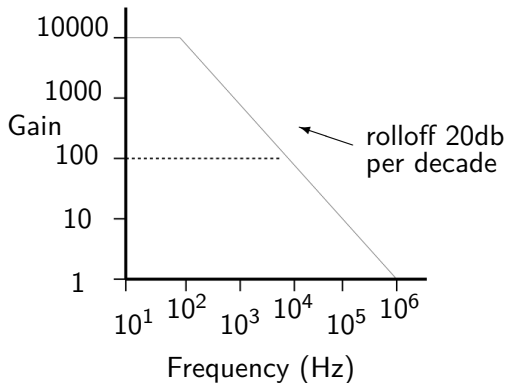

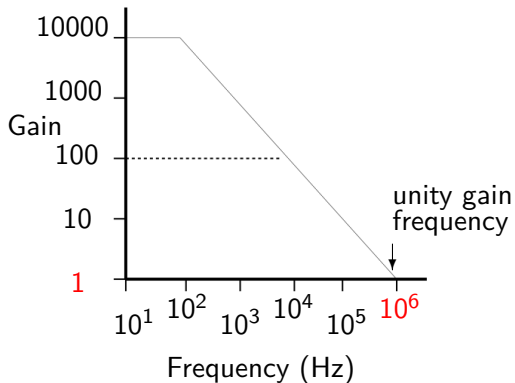

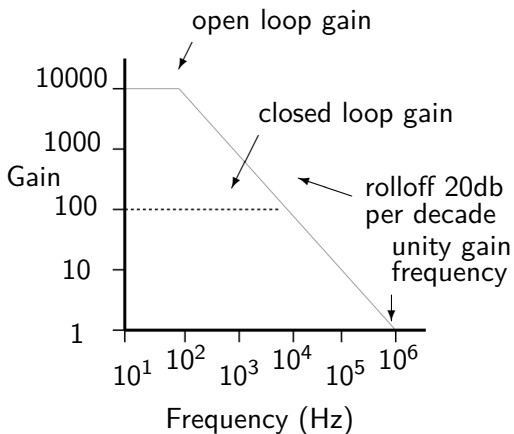

# Illustrating frequency response



## Illustrating frequency response

- The **Bode plot** is logarithmic in both frequency and gain.

## Illustrating frequency response

- The **Bode plot** is logarithmic in both frequency and gain.
- The straight line indicates that gain is inversely proportional to frequency

## Illustrating frequency response

- The **Bode plot** is logarithmic in both frequency and gain.
- The straight line indicates that gain is inversely proportional to frequency

$$A \propto \frac{1}{f}$$

## Illustrating frequency response

- The **Bode plot** is logarithmic in both frequency and gain.
- The straight line indicates that gain is inversely proportional to frequency

$$A \propto \frac{1}{f}$$

- Gain is often expressed in **decibels**, rather than simply as a ratio of output to input

## Illustrating frequency response

- The **Bode plot** is logarithmic in both frequency and gain.
- The straight line indicates that gain is inversely proportional to frequency

$$A \propto \frac{1}{f}$$

- Gain is often expressed in **decibels**, rather than simply as a ratio of output to input
- So

$$G_{db} = 20 \log \left( \frac{V_o}{V_i} \right)$$

$$G_{db} = 20 \log \left( \frac{V_o}{V_i} \right)$$

$$G_{db} = 20 \log \left( \frac{V_o}{V_i} \right)$$

- A change by a factor of 10 in  $\left( \frac{V_o}{V_i} \right)$  is a change of 20 db.

$$G_{db} = 20 \log \left( \frac{V_o}{V_i} \right)$$

- A change by a factor of 10 in  $\left( \frac{V_o}{V_i} \right)$  is a change of 20 db.
- A **decade** is a factor of 10, so rolloff of 20 db/decade represents a *decrease* in  $\left( \frac{V_o}{V_i} \right)$  of a factor of 10 as the frequency *increases* by a factor of 10.



- This inverse relationship between frequency and gain is expressed in various ways

- This inverse relationship between frequency and gain is expressed in various ways
- The **gain-bandwidth product** (GBW) is

- This inverse relationship between frequency and gain is expressed in various ways
- The **gain-bandwidth product** (GBW) is

$$GBW = Af$$

- This inverse relationship between frequency and gain is expressed in various ways
- The **gain-bandwidth product** (GBW) is

$$GBW = Af$$

- The **unity-gain frequency**  $\rightarrow$  frequency at which  $\left(\frac{V_o}{V_i}\right) = 1$ .

- This inverse relationship between frequency and gain is expressed in various ways
- The **gain-bandwidth product** (GBW) is

$$GBW = Af$$

- The **unity-gain frequency**  $\rightarrow$  frequency at which  $\left(\frac{V_o}{V_i}\right) = 1$ .
- (I will use the term  $A$  to refer to  $\left(\frac{V_o}{V_i}\right)$  and  $G$  to denote the gain in decibels, as described above. This convention is common, but not universal, so when consulting information on the subject be sure to pay attention to how gain is expressed.)

## Relationship between open loop and closed loop gain

- When negative feedback is employed in an op amp circuit, the **closed-loop gain** is decreased.

## Relationship between open loop and closed loop gain

- When negative feedback is employed in an op amp circuit, the **closed-loop gain** is decreased.
- As frequency increases, and the open-loop gain decreases due to rolloff, the values of open-loop and closed-loop gain eventually coincide.

## Relationship between open loop and closed loop gain

- When negative feedback is employed in an op amp circuit, the **closed-loop gain** is decreased.
- As frequency increases, and the open-loop gain decreases due to rolloff, the values of open-loop and closed-loop gain eventually coincide.
- From this point on, the closed loop gain also begins to experience rolloff at the same rate.



## Relationship between open loop and closed loop gain

- When negative feedback is employed in an op amp circuit, the **closed-loop gain** is decreased.
- As frequency increases, and the open-loop gain decreases due to rolloff, the values of open-loop and closed-loop gain eventually coincide.
- From this point on, the closed loop gain also begins to experience rolloff at the same rate.
- *Thus the unity-gain frequency for an op amp circuit is the same, regardless of the mid-band gain.*


# Slew Rate

# Slew Rate

When the inputs to an op amp change, it takes time for the output to change.

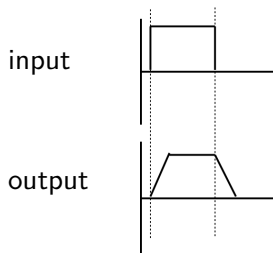
# Slew Rate

When the inputs to an op amp change, it takes time for the output to change.


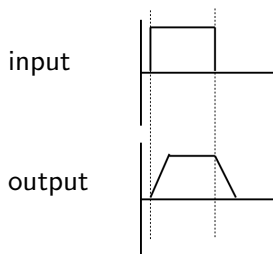
# Slew Rate


When the inputs to an op amp change, it takes time for the output to change.




The *rate* of possible change of the output voltage is referred to as the **slew rate**.

This is the output of a voltage follower at 100kHz, for a sine wave input.

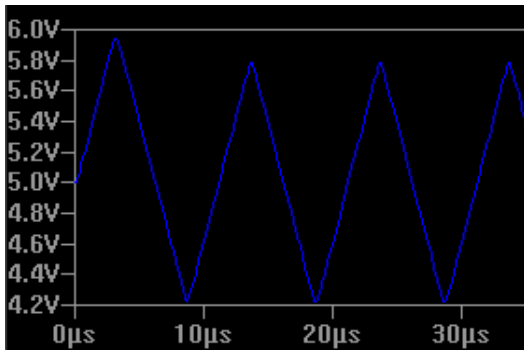This is the output of a voltage follower at 100kHz, for a sine wave input.



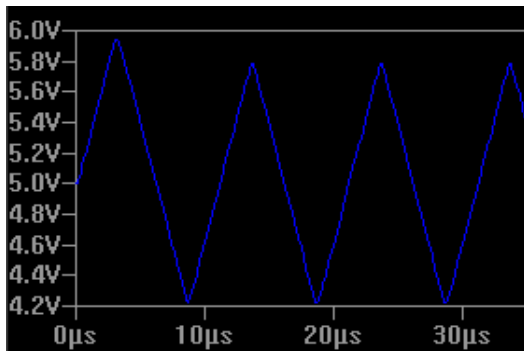This is the output of a voltage follower at 100kHz, for a sine wave input.



The rise (or fall) is about 1.6 volts in 5  $\mu\text{s}$ , or about 0.3 V/ $\mu\text{s}$ .



- The **slew rate** of an operational amplifier is defined as *the maximum rate of change of voltage output*.

- The **slew rate** of an operational amplifier is defined as *the maximum rate of change of voltage output*.
- Slew rate is usually given in  $V/\mu S$ .

- The **slew rate** of an operational amplifier is defined as *the maximum rate of change of voltage output*.
- Slew rate is usually given in  $V/\mu S$ .

$$\text{slew rate} = \left. \frac{dV}{dt} \right|_{max}$$

# Interaction of amplitude and slew rate

# Interaction of amplitude and slew rate

$$\text{slew rate} = \left. \frac{dV}{dt} \right|_{\text{max}}$$

# Interaction of amplitude and slew rate

$$\text{slew rate} = \left. \frac{dV}{dt} \right|_{max}$$

- Thus if we have a sinusoidal signal

# Interaction of amplitude and slew rate

$$\text{slew rate} = \left. \frac{dV}{dt} \right|_{\text{max}}$$

- Thus if we have a sinusoidal signal

$$V = A \sin(\omega t)$$

# Interaction of amplitude and slew rate

$$\text{slew rate} = \left. \frac{dV}{dt} \right|_{max}$$

- Thus if we have a sinusoidal signal

$$V = A \sin(\omega t)$$

$$\frac{dV}{dt} = \omega A \cos(\omega t)$$



# Interaction of amplitude and slew rate

$$\text{slew rate} = \left. \frac{dV}{dt} \right|_{\max}$$

- Thus if we have a sinusoidal signal

$$V = A \sin(\omega t)$$

$$\frac{dV}{dt} = \omega A \cos(\omega t)$$

$$\left. \frac{dV}{dt} \right|_{\max} = \omega A = 2\pi f A$$

$$\textit{slew rate} = \left. \frac{dV}{dt} \right|_{\textit{max}}$$

$$\text{slew rate} = \left. \frac{dV}{dt} \right|_{\max}$$

$$(\text{sine wave}) \left. \frac{dV}{dt} \right|_{\max} = \omega A = 2\pi fA$$

$$\text{slew rate} = \left. \frac{dV}{dt} \right|_{\max}$$

$$(\text{sine wave}) \left. \frac{dV}{dt} \right|_{\max} = \omega A = 2\pi f A$$

$$f_{\max} = \frac{\text{slew rate}}{2\pi A}$$

$$\text{slew rate} = \left. \frac{dV}{dt} \right|_{\max}$$

$$(\text{sine wave}) \left. \frac{dV}{dt} \right|_{\max} = \omega A = 2\pi f A$$

$$f_{\max} = \frac{\text{slew rate}}{2\pi A}$$

- Thus the higher the amplitude, the lower the maximum frequency without distortion.

$$\text{slew rate} = \left. \frac{dV}{dt} \right|_{max}$$

$$(\text{sine wave}) \left. \frac{dV}{dt} \right|_{max} = \omega A = 2\pi fA$$

$$f_{max} = \frac{\text{slew rate}}{2\pi A}$$

- Thus the higher the amplitude, the lower the maximum frequency without distortion.


Sine waves will be the *least* distorted of any waveform.

6V

4V

6V

4V

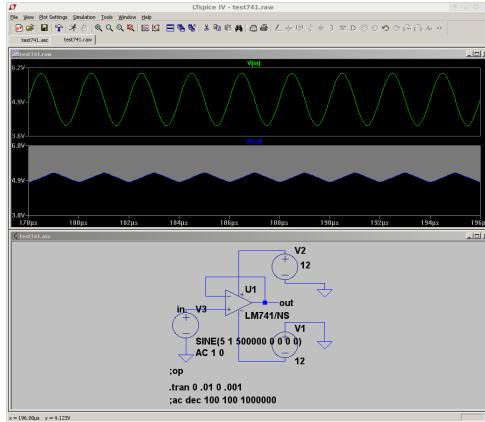


Here's a previous circuit; 1V, 500kHz into a voltage follower.

5.1V

4.9V

5.1V

4.9V

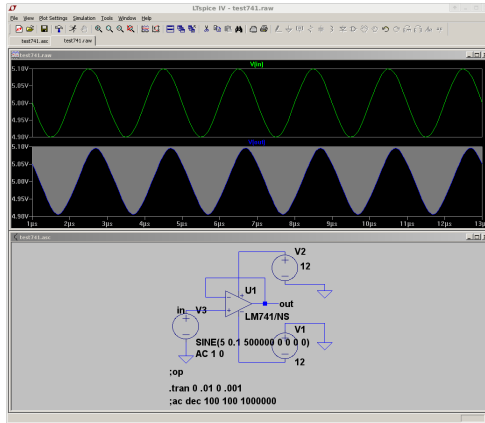

Reducing the input to 0.1V makes the output much closer.



## Active filters

- One of the uses of op amps is to produce circuits which are used to amplify or attenuate a certain range of frequencies.

## Active filters

- One of the uses of op amps is to produce circuits which are used to amplify or attenuate a certain range of frequencies.
- These are called **active filters**.

## Low Pass Filters

- A **low pass filter** allows frequencies below a certain **corner frequency**  $f_c$  to pass, and attenuates those above.

## Low Pass Filters

- A **low pass filter** allows frequencies below a certain **corner frequency**  $f_c$  to pass, and attenuates those above.
- Note that the corner frequency is not an absolute limit; it is the point at which attenuation begins.

## Low Pass Filters

- A **low pass filter** allows frequencies below a certain **corner frequency**  $f_c$  to pass, and attenuates those above.
- Note that the corner frequency is not an absolute limit; it is the point at which attenuation begins.

Actually it's the “3 db point” at which the gain differs from the mid-band gain by 3db.

## Low Pass Filters

- A **low pass filter** allows frequencies below a certain **corner frequency**  $f_c$  to pass, and attenuates those above.
- Note that the corner frequency is not an absolute limit; it is the point at which attenuation begins.

Actually it's the “3 db point” at which the gain differs from the mid-band gain by 3db.

Expressing gain without using decibels, it's the point at which the gain is the mid-band gain divided by  $\sqrt{2}$ .

## Low Pass Filters

- A **low pass filter** allows frequencies below a certain **corner frequency**  $f_c$  to pass, and attenuates those above.
- Note that the corner frequency is not an absolute limit; it is the point at which attenuation begins.

Actually it's the "3 db point" at which the gain differs from the mid-band gain by 3db.

Expressing gain without using decibels, it's the point at which the gain is the mid-band gain divided by  $\sqrt{2}$ .

- A low pass filter and its Bode plot are shown in the following figures.

## Low Pass Filters

- A **low pass filter** allows frequencies below a certain **corner frequency**  $f_c$  to pass, and attenuates those above.
- Note that the corner frequency is not an absolute limit; it is the point at which attenuation begins.


Actually it's the "3 db point" at which the gain differs from the mid-band gain by 3db.

Expressing gain without using decibels, it's the point at which the gain is the mid-band gain divided by  $\sqrt{2}$ .


- A low pass filter and its Bode plot are shown in the following figures.
- (Note: there are numerous designs for filters; the ones shown here are simple to analyze.)




## Low pass filter

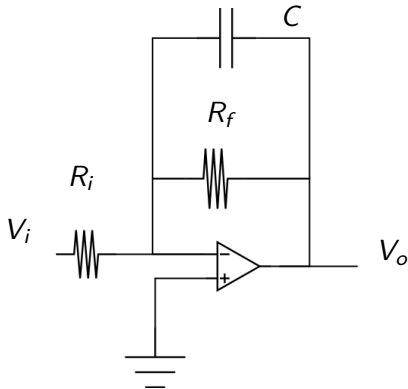


## Low pass filter at *low* frequencies

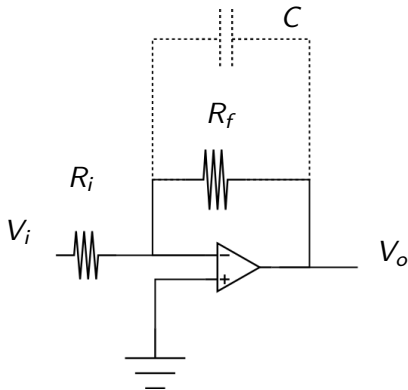


## Low pass filter at *high* frequencies

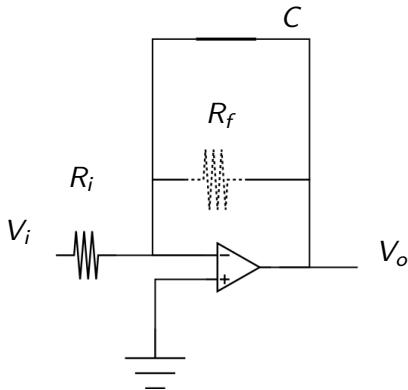

## Low pass filter Bode plot

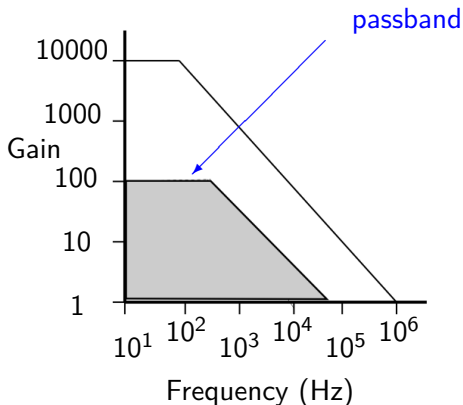

## Low pass filter Bode plot

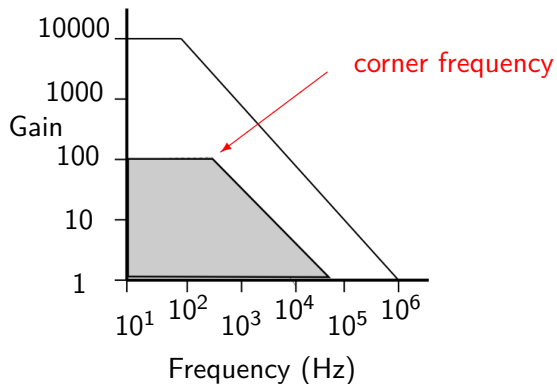

## Low pass filter

- In the feedback part of the circuit, at low frequencies  $X_c \approx \infty$  and so the gain is that of a normal inverting amplifier.

## Low pass filter

- In the feedback part of the circuit, at low frequencies  $X_c \approx \infty$  and so the gain is that of a normal inverting amplifier.
- As the frequency increases, at a **corner frequency**  $X_c = R_f$ .

## Low pass filter

- In the feedback part of the circuit, at low frequencies  $X_c \approx \infty$  and so the gain is that of a normal inverting amplifier.
- As the frequency increases, at a **corner frequency**  $X_c = R_f$ .
- Above this frequency,



## Low pass filter

- In the feedback part of the circuit, at low frequencies  $X_c \approx \infty$  and so the gain is that of a normal inverting amplifier.
- As the frequency increases, at a **corner frequency**  $X_c = R_f$ .
- Above this frequency,

$$Z \propto \frac{1}{f}$$

since  $X_c < R_f$ .

## High Pass Filters

- A **high pass filter** allows frequencies *above* a certain corner frequency,  $f_c$  to pass, and attenuates those *below*.

## High Pass Filters

- A **high pass filter** allows frequencies *above* a certain corner frequency,  $f_c$  to pass, and attenuates those *below*.
- As for the low pass filter, the corner frequency is not an absolute limit; it is the point at which amplification begins.

## High Pass Filters

- A **high pass filter** allows frequencies *above* a certain corner frequency,  $f_c$  to pass, and attenuates those *below*.
- As for the low pass filter, the corner frequency is not an absolute limit; it is the point at which amplification begins.
- The high pass filter has a limitation due to the rolloff of the op amp.


## High Pass Filters


- A **high pass filter** allows frequencies *above* a certain corner frequency,  $f_c$  to pass, and attenuates those *below*.
- As for the low pass filter, the corner frequency is not an absolute limit; it is the point at which amplification begins.
- The high pass filter has a limitation due to the rolloff of the op amp.
- As with any amplifier circuit, it is never possible to have gain above the open loop gain of the op amp, so any high pass filter is actually a **band pass filter**, which will be discussed below.

## High Pass Filters


- A **high pass filter** allows frequencies *above* a certain corner frequency,  $f_c$  to pass, and attenuates those *below*.
- As for the low pass filter, the corner frequency is not an absolute limit; it is the point at which amplification begins.
- The high pass filter has a limitation due to the rolloff of the op amp.
- As with any amplifier circuit, it is never possible to have gain above the open loop gain of the op amp, so any high pass filter is actually a **band pass filter**, which will be discussed below.
- A high pass filter and its Bode plot are shown in the following figures.

## High pass filter

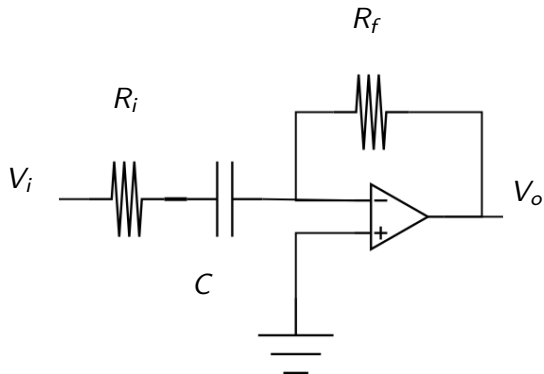


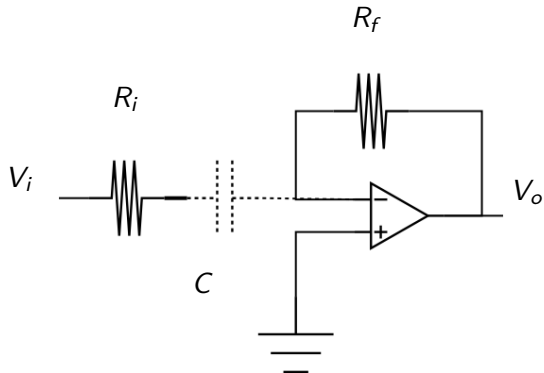High pass filter at *low* frequencies

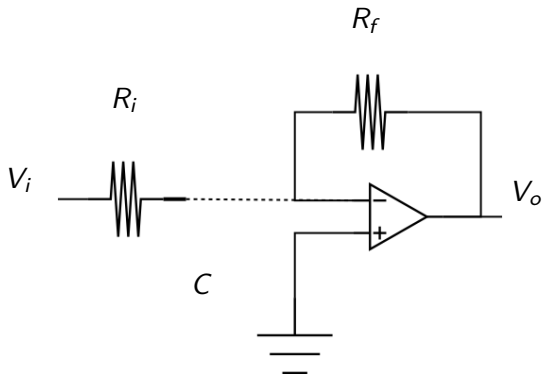


High pass filter at *high* frequencies


## High pass filter Bode plot

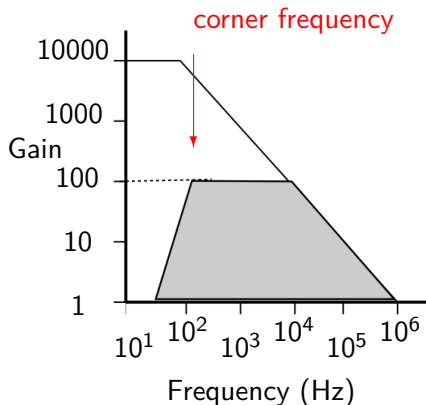

## High pass filter Bode plot

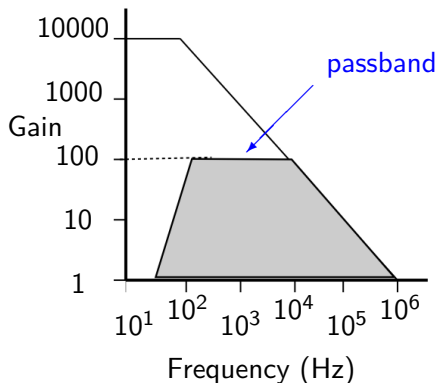

## High pass filter Bode plot

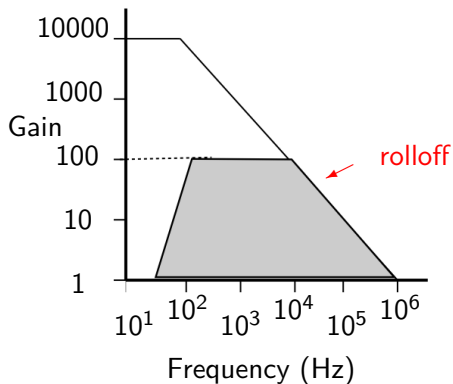

In the input part of the circuit, at high frequencies  $X_c \approx 0$  and so the gain is that of a normal inverting amplifier. As the frequency decreases, at a **corner frequency**  $X_c = R_i$ . Below this frequency,

$$Z \propto \frac{1}{f}$$

since  $X_c > R_i$ .

A **band pass filter** combines a low pass and a high pass filter to allow frequencies *between* two corner frequencies,  $f_{c1}$  and  $f_{c2}$  to pass, and attenuates those *outside* that range. The next figure shows the Bode plot for a band pass filter.

## Bandpass filter Bode plot

