

PC300 op amp quiz (Answer each question in a sentence or two.)

1. Given the following input/output graph, sketch the circuit that generated it. Show all component values. (If there is a choice of component values, explain the choice.) State any necessary restrictions on supply voltages.

