

PC/CP320 Diode Calculation Checklist (1.0)

1. Zener diode
resistance _____
2. Optoisolator
LED resistance
(5 V to 3.3V) _____
3. Optoisolator
photodiode/transistor
resistance
(5 V to 3.3V) _____
4. Optoisolator
LED resistance
(3.3V to 5 V) _____
5. Optoisolator
photodiode/transistor
resistance
(3.3V to 5 V) _____