

PC/CP320 Diode Calculation Checklist (2019)

1. Zener diode  
resistance \_\_\_\_\_
2. Optoisolator  
LED resistance  
(5 V to 3.3V) \_\_\_\_\_
3. Optoisolator  
photodiode/transistor  
resistance  
(5 V to 3.3V) \_\_\_\_\_
4. Optoisolator  
LED resistance  
(3.3V to 5 V) \_\_\_\_\_
5. Optoisolator  
photodiode/transistor  
resistance  
(3.3V to 5 V) \_\_\_\_\_