

# Electronics

## Controlling Power to Output Transducers

Terry Sturtevant

Wilfrid Laurier University

November 10, 2016

# Basic Rule of Control

## Basic Rule of Control

Control usually involves three things:

## Basic Rule of Control

Control usually involves three things:

- 1 a fixed power supply

## Basic Rule of Control

Control usually involves three things:

- 1 a fixed power supply
- 2 a **load** to which we want to control the power

## Basic Rule of Control

Control usually involves three things:

- 1 a fixed power supply
- 2 a **load** to which we want to control the power
- 3 a **control element** to which we will send signals to control the power to the load.

## Basic Rule of Control

Control usually involves three things:

- ① a fixed power supply
- ② a **load** to which we want to control the power
- ③ a **control element** to which we will send signals to control the power to the load.

These will be arranged in a voltage divider.


## Basic Rule of Control

Types of output transducers


Types of control

Devices for control


Other considerations

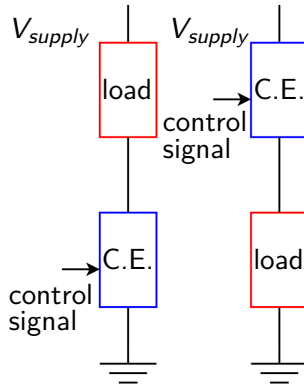



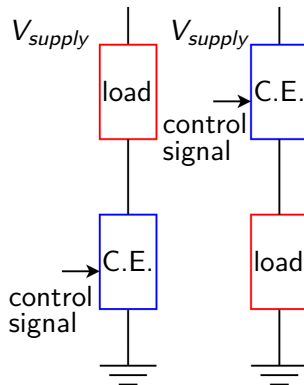

“C.E.” is the control element.

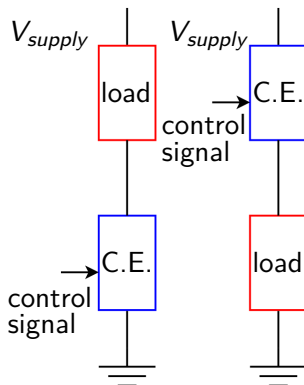

“C.E.” is the control element.

“Load” could be a motor, solenoid, relay coil, etc.

## Low power devices

## Low power devices

These devices require *low power*.

## Low power devices

These devices require *low power*. Low power is typically  $\lesssim 1W$ .

## Low power devices

These devices require *low power*. Low power is typically  $\lesssim 1W$ .

- meter

## Low power devices

These devices require *low power*. Low power is typically  $\lesssim 1W$ .

- meter
- oscilloscope

## Low power devices

These devices require *low power*. Low power is typically  $\lesssim 1W$ .

- meter
- oscilloscope

These devices produce **information**.



Basic Rule of Control  
Types of output transducers  
Types of control  
Devices for control  
Other considerations

Produce "information"  
Produce "action"

## High power devices

## High power devices

These devices require *high power*.

## High power devices

These devices require *high power*. High power is typically  $\gtrsim 1W$ .

## High power devices

These devices require *high power*. High power is typically  $\gtrsim 1W$ .

- lights

## High power devices

These devices require *high power*. High power is typically  $\gtrsim 1W$ .

- lights
- solenoids

## High power devices

These devices require *high power*. High power is typically  $\gtrsim 1W$ .

- lights
- solenoids

These devices produce **action**.

## High power devices

These devices require *high power*. High power is typically  $\gtrsim 1W$ .

- lights
- solenoids

These devices produce **action**.

An operational amplifier is a *voltage* device; it can't produce more than a few mW of power.

# Types of control



## Types of control

- on/off

## Types of control

- on/off  
like a switch

## Types of control

- on/off  
like a switch
- proportional

## Types of control

- on/off  
like a switch
- proportional  
like a rheostat or potentiometer

## Control trade-offs

## Control trade-offs

There are trade-offs involved in choosing a type of control.

## Control trade-offs

There are trade-offs involved in choosing a type of control.

- efficiency

## Control trade-offs

There are trade-offs involved in choosing a type of control.

- efficiency
  - on/off is 100% efficient



## Control trade-offs

There are trade-offs involved in choosing a type of control.

- efficiency
  - on/off is 100% efficient
  - proportional is less efficient

## Control trade-offs

There are trade-offs involved in choosing a type of control.

- efficiency
  - on/off is 100% efficient
  - proportional is less efficient
- noise

## Control trade-offs

There are trade-offs involved in choosing a type of control.

- efficiency
  - on/off is 100% efficient
  - proportional is less efficient
- noise
  - on/off produces more noise

## Control trade-offs

There are trade-offs involved in choosing a type of control.

- efficiency
  - on/off is 100% efficient
  - proportional is less efficient
- noise
  - on/off produces more noise
  - proportional produces less noise

## Control trade-offs

There are trade-offs involved in choosing a type of control.

- efficiency
  - on/off is 100% efficient
  - proportional is less efficient
- noise
  - on/off produces more noise
  - proportional produces less noise

**There is a trade-off between efficiency and noise.**

- As previously noted, any device used for control is basically used in a voltage divider using

- As previously noted, any device used for control is basically used in a voltage divider using
  - the supply voltage,

- As previously noted, any device used for control is basically used in a voltage divider using
  - the supply voltage,
  - the control device,



- As previously noted, any device used for control is basically used in a voltage divider using
  - the supply voltage,
  - the control device,
  - and the load.

- As previously noted, any device used for control is basically used in a voltage divider using
  - the supply voltage,
  - the control device,
  - and the load.
- The order of the control element and the load in the voltage divider has some effects on the circuit operation.

# Relay

# Relay

A relay is based on a solenoid, and has four types of pins:

# Relay

A relay is based on a solenoid, and has four types of pins:

- coil

# Relay

A relay is based on a solenoid, and has four types of pins:

- coil
- common

# Relay

A relay is based on a solenoid, and has four types of pins:

- coil
- common
- **NO**; normally open (possibly)


# Relay

A relay is based on a solenoid, and has four types of pins:


- coil
- common
- **NO**; normally open (possibly)
- **NC**; normally closed (possibly)



Relay **OFF**

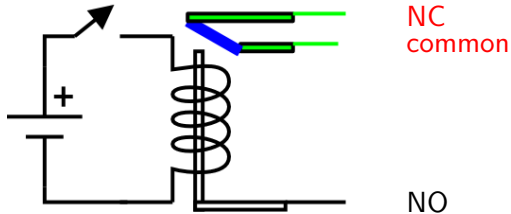


Relay ON

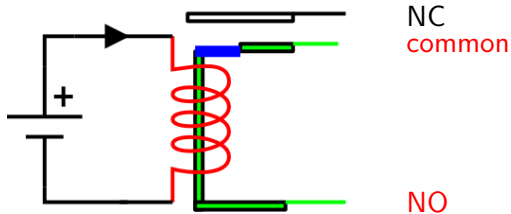

An internal spring returns the solenoid to its original position when power is removed from the coil.


Since a relay is inductive, all of the precautions for an inductive device must be taken.

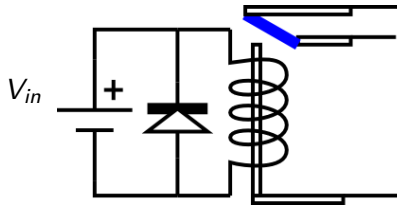Since a relay is inductive, all of the precautions for an inductive device must be taken.




The relay can be inserted on either side of the load in a voltage divider.

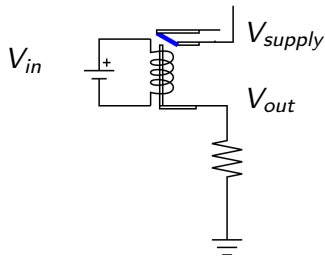The relay can be inserted on either side of the load in a voltage divider.



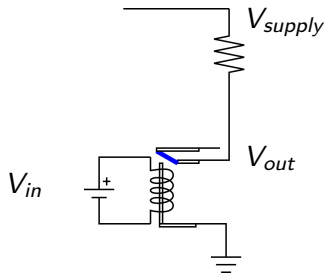The relay can be inserted on either side of the load in a voltage divider.





# Transistors

# Transistors

- There are several types of transistor; each is a three terminal device.

# Transistors

- There are several types of transistor; each is a three terminal device.
- The most common types of transistors are BJTs and FETs.

# Transistors

- There are several types of transistor; each is a three terminal device.
- The most common types of transistors are BJTs and FETs.
- Transistors are often used in voltage dividers to act as variable resistors.

# Metal Oxide Semiconductor Field Effect Transistors

# Metal Oxide Semiconductor Field Effect Transistors

A MOSFET (or Metal Oxide Semiconductor Field Effect Transistor) is a three terminal device.

# Metal Oxide Semiconductor Field Effect Transistors

A MOSFET (or Metal Oxide Semiconductor Field Effect Transistor) is a three terminal device.

- drain

# Metal Oxide Semiconductor Field Effect Transistors

A MOSFET (or Metal Oxide Semiconductor Field Effect Transistor) is a three terminal device.

- drain
- source



# Metal Oxide Semiconductor Field Effect Transistors


A MOSFET (or Metal Oxide Semiconductor Field Effect Transistor) is a three terminal device.

- drain
- source
- gate


## FET symbol




## FET symbol

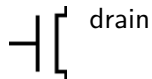

## FET symbol

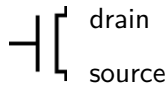

## FET symbol

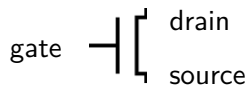

## FET operation

- FETS are *voltage* amplifiers; a small **gate voltage** controls a much larger **drain/source current**.

## FET operation

- FETS are *voltage* amplifiers; a small **gate voltage** controls a much larger **drain/source current**.

Actually it's the voltage between the gate and the source which matters.

## D and E MOSFETs



## D and E MOSFETs

There are two kinds of MOSFET

## D and E MOSFETs

There are two kinds of MOSFET

- enhancement mode (E type)

## D and E MOSFETs

There are two kinds of MOSFET

- enhancement mode (E type)

When  $V_{gs}$  is below  $V_{th}$ ,  $I_D = 0$

## D and E MOSFETs

There are two kinds of MOSFET

- enhancement mode (E type)

When  $V_{gs}$  is below  $V_{th}$ ,  $I_D = 0$

As  $V_{gs}$  increases above  $V_{th}$ ,

## D and E MOSFETs

There are two kinds of MOSFET

- enhancement mode (E type)

When  $V_{gs}$  is below  $V_{th}$ ,  $I_D = 0$

As  $V_{gs}$  increases above  $V_{th}$ ,

$I_D$  increases.

## D and E MOSFETs

There are two kinds of MOSFET

- enhancement mode (E type)

When  $V_{gs}$  is below  $V_{th}$ ,  $I_D = 0$

As  $V_{gs}$  increases above  $V_{th}$ ,  
 $I_D$  increases.

- depletion mode (D type)

## D and E MOSFETs

There are two kinds of MOSFET

- enhancement mode (E type)

When  $V_{gs}$  is below  $V_{th}$ ,  $I_D = 0$

As  $V_{gs}$  increases above  $V_{th}$ ,

$I_D$  increases.

- depletion mode (D type)

To get  $I_D$  to zero, a *negative*  $V_{gs_{off}}$  must be applied.

## D and E MOSFETs

There are two kinds of MOSFET

- enhancement mode (E type)

When  $V_{gs}$  is below  $V_{th}$ ,  $I_D = 0$

As  $V_{gs}$  increases above  $V_{th}$ ,  
 $I_D$  increases.

- depletion mode (D type)

To get  $I_D$  to zero, a *negative*  $V_{gs_{off}}$  must be applied.

Actually, all MOSFETs operate in *enhancement* mode. It's just that some *only* operate in that mode.



## D and E MOSFETs

There are two kinds of MOSFET

- enhancement mode (E type)


When  $V_{gs}$  is below  $V_{th}$ ,  $I_D = 0$

As  $V_{gs}$  increases above  $V_{th}$ ,  
 $I_D$  increases.


- depletion mode (D type)

To get  $I_D$  to zero, a *negative*  $V_{gs_{off}}$  must be applied.

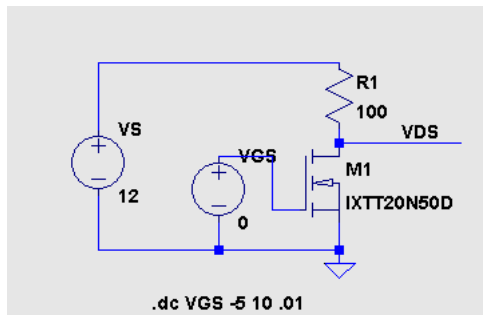
Actually, all MOSFETs operate in *enhancement* mode. It's just that some *only* operate in that mode. Which kind you want depends on whether or not you want *some* current to flow with no applied gate-source voltage.




D (depletion mode) MOSFET

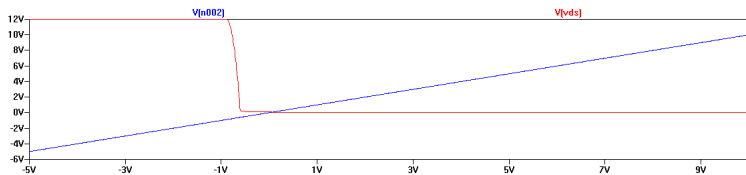


D (depletion mode) MOSFET output

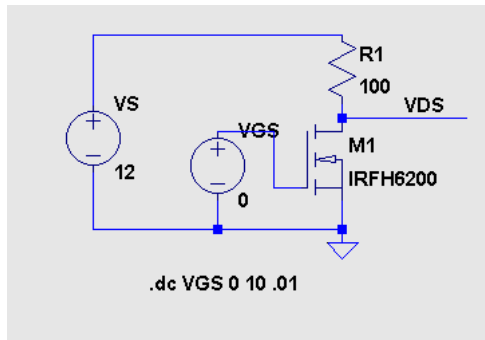


E (enhancement mode) MOSFET

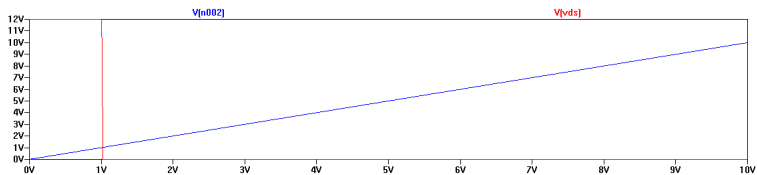


E (enhancement mode) MOSFET output

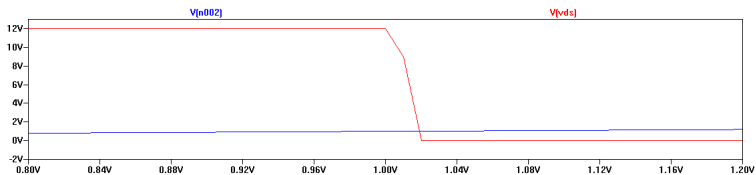

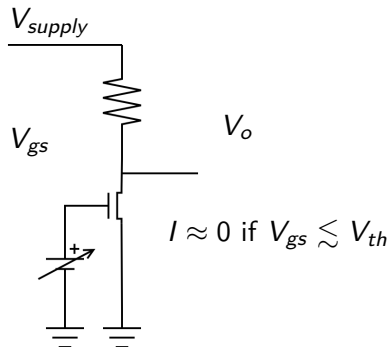E (enhancement mode) MOSFET output zoomed in




E (enhancement mode) FET

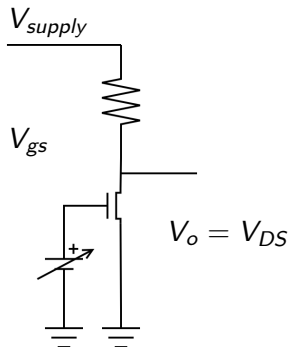


E (enhancement mode) FET




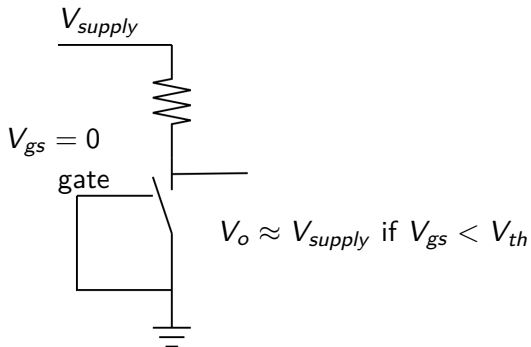

E (enhancement mode) FET

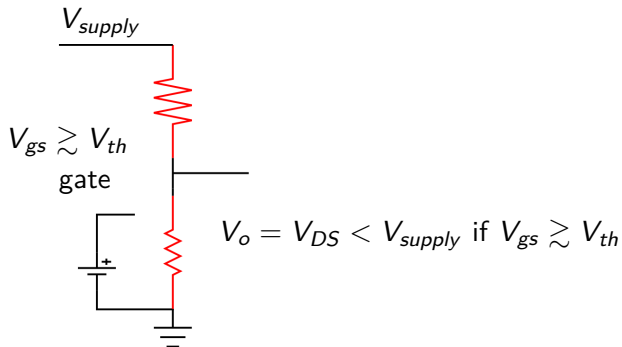

E (enhancement mode) FET

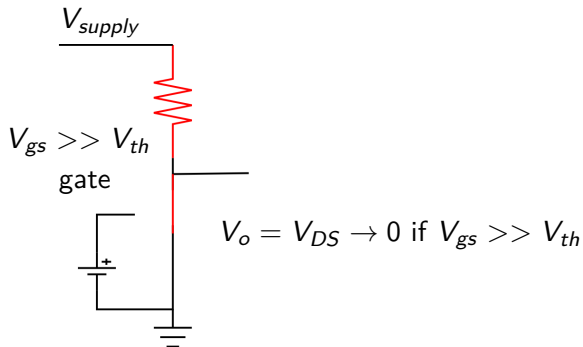


E (enhancement mode) FET


- FETS are *voltage* amplifiers; a small **gate-source** voltage controls a much larger **drain/source** current.

- FETS are *voltage* amplifiers; a small **gate-source** voltage controls a much larger **drain/source** current.
- *You do not use a gate resistor with an FET!*

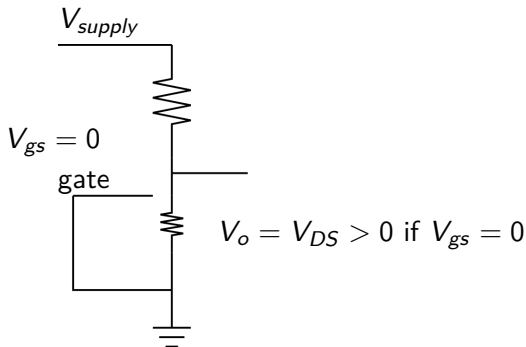- FETS are *voltage* amplifiers; a small **gate-source** voltage controls a much larger **drain/source** current.
- *You do not use a gate resistor with an FET!*
- All FETs work in *enhancement* mode; some also work in *depletion* mode.




D (depletion mode) FET

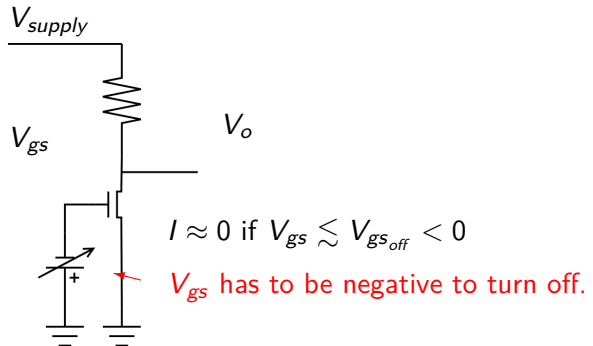


D (depletion mode) FET



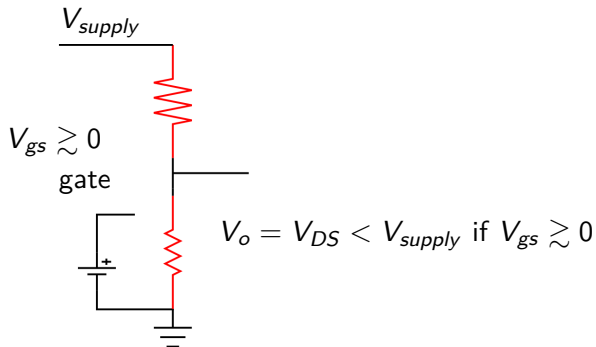

D (depletion mode) FET

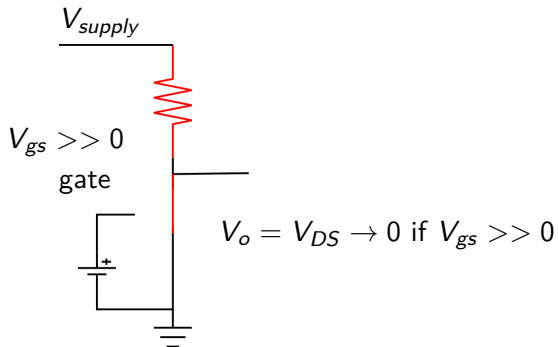


D (depletion mode) FET


The MOSFET, like the relay, can be placed in either position of a voltage divider.

The MOSFET, like the relay, can be placed in either position of a voltage divider. The effects are the same as for the relay.

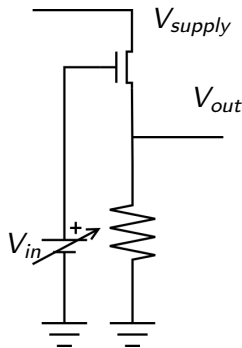The MOSFET, like the relay, can be placed in either position of a voltage divider. The effects are the same as for the relay.



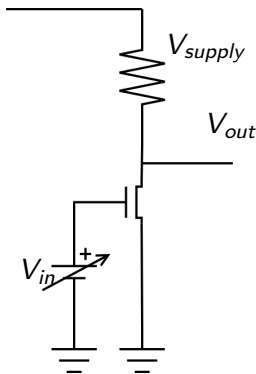The MOSFET, like the relay, can be placed in either position of a voltage divider. The effects are the same as for the relay.



# Bipolar Junction Transistors

## Bipolar Junction Transistors

A BJT (or Bipolar Junction Transistor) is a three terminal *current* device.



## Bipolar Junction Transistors

A BJT (or Bipolar Junction Transistor) is a three terminal *current* device. The terminals are

## Bipolar Junction Transistors

A BJT (or Bipolar Junction Transistor) is a three terminal *current* device. The terminals are

- collector

# Bipolar Junction Transistors

A BJT (or Bipolar Junction Transistor) is a three terminal *current* device. The terminals are

- collector
- emitter

## Bipolar Junction Transistors

A BJT (or Bipolar Junction Transistor) is a three terminal *current* device. The terminals are

- collector
- emitter
- base

## Bipolar Junction Transistors

A BJT (or Bipolar Junction Transistor) is a three terminal *current* device. The terminals are


- collector
- emitter
- base

The current from the collector to the emitter is controlled by the *current* into the base.






collector

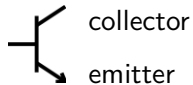



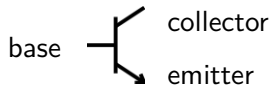

# BJT operation

## BJT operation


- BJTS are *current* amplifiers;

## BJT operation

- BJTS are *current* amplifiers; a small **base** current controls a much larger **collector/emitter** current.

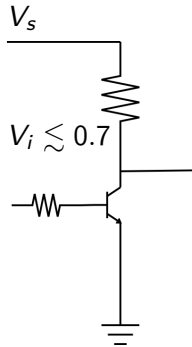
## BJT operation


- BJTS are *current* amplifiers; a small **base** current controls a much larger **collector/emitter** current.
- *You should always have a base resistor with a BJT!*



$$V_o \approx V_s \text{ if } V_i \approx 0.7$$
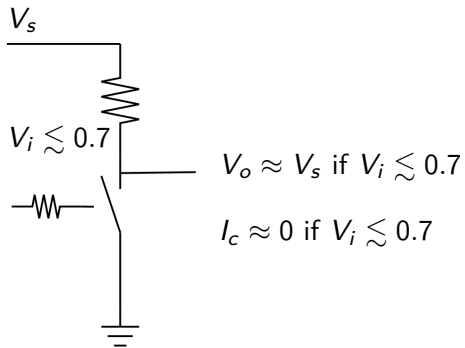
$$I_c \approx 0 \text{ if } V_i \approx 0.7$$



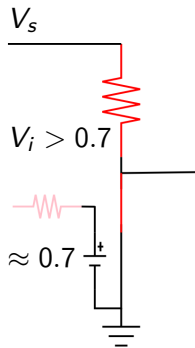


$$V_o = V_s - I_c R \text{ if } V_i > 0.7$$

$$I_c \propto I_b \text{ if } V_i > 0.7$$




Like the previous devices, either position in a voltage divider can be used.

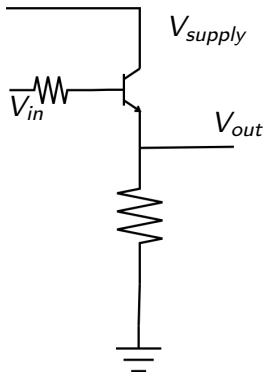Like the previous devices, either position in a voltage divider can be used.



Like the previous devices, either position in a voltage divider can be used.

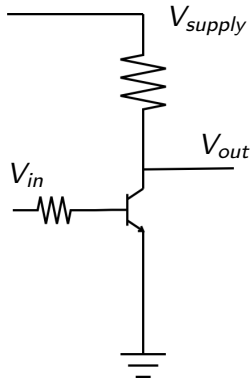Like the previous devices, either position in a voltage divider can be used.



# TRIAC

# TRIAC

A TRIAC is a three terminal *ac voltage* device.

# TRIAC

A TRIAC is a three terminal *ac voltage* device. The terminals are

# TRIAC

A TRIAC is a three terminal *ac voltage* device. The terminals are

- main terminal 1



# TRIAC

A TRIAC is a three terminal *ac voltage* device. The terminals are

- main terminal 1
- main terminal 2

# TRIAC

A TRIAC is a three terminal *ac voltage* device. The terminals are

- main terminal 1
- main terminal 2
- gate

# TRIAC

A TRIAC is a three terminal *ac voltage* device. The terminals are

- main terminal 1
- main terminal 2
- gate


A triac will begin to conduct when it receives a voltage pulse on the *gate*.


# TRIAC


A TRIAC is a three terminal *ac voltage* device. The terminals are

- main terminal 1
- main terminal 2
- gate

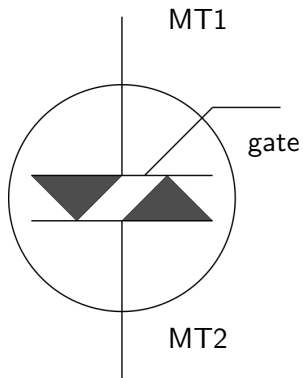A triac will begin to conduct when it receives a voltage pulse on the *gate*. It will continue to conduct until the *current* is zero.



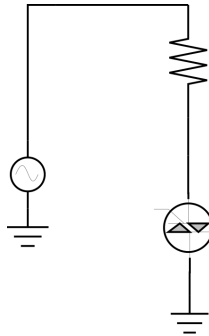

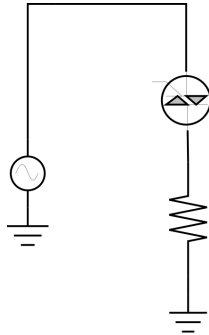

It can operate in two modes.





It can operate in two modes.

- burst


It can operate in two modes.


- burst
- delayed trigger

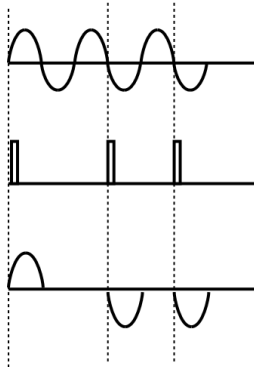

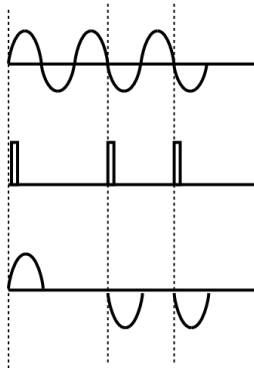


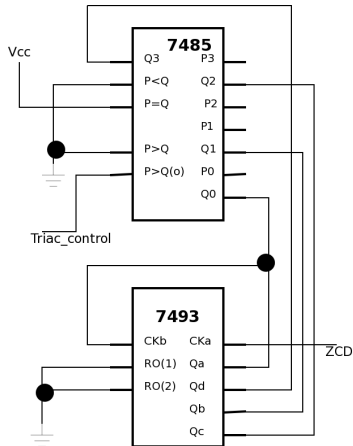
In *burst* mode, trigger pulses are only given at the beginning of half-cycles.



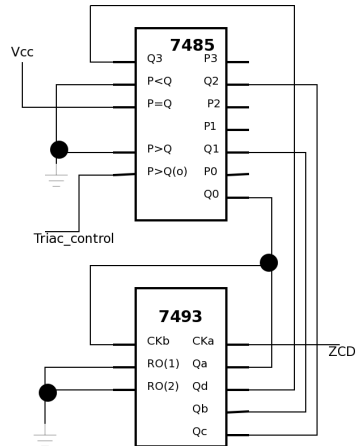

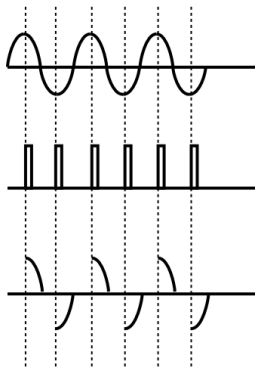
This is a typical circuit to control a triac in burst mode.




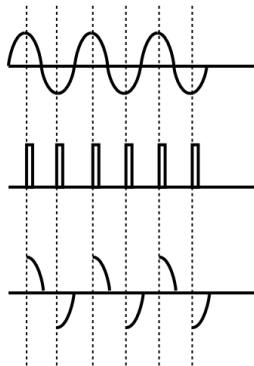

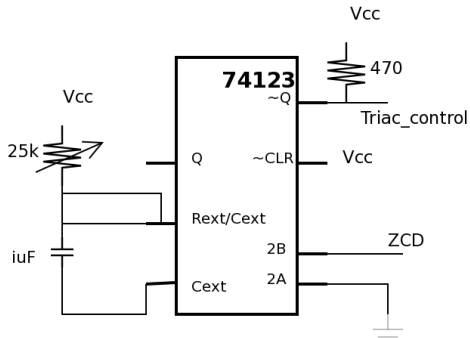In *delayed trigger* mode, trigger pulses are delayed after the beginning of half-cycles to produce power for only a part of each half cycle.





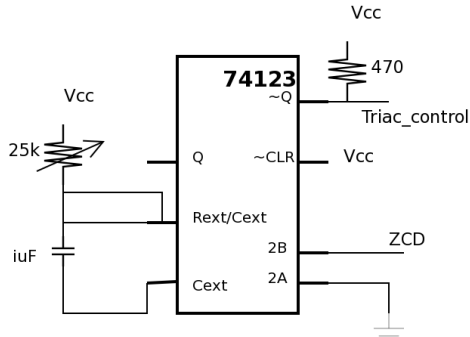

This is a typical circuit to control a triac in delayed trigger mode.

# Using TTL gates for control

## Using TTL gates for control

- “Extra” current from TTL

## Using TTL gates for control


- “Extra” current from TTL
- sink instead of source

## Using TTL gates for control

- “Extra” current from TTL
- sink instead of source
- 0.4mA vs. 8 mA (LS)


## Current sourcing

## Current sourcing

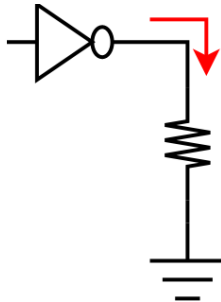




## Current sourcing

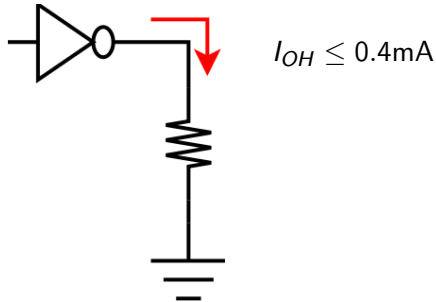


## Current sinking

## Current sinking

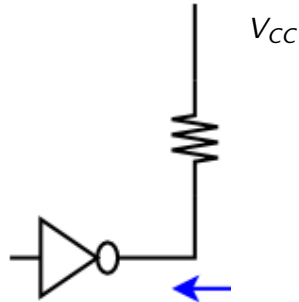

## Current sinking

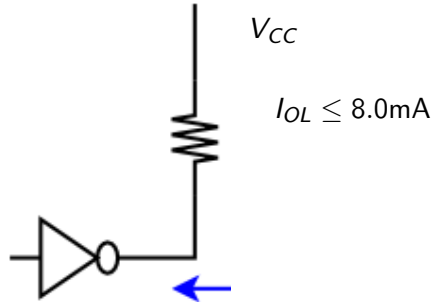

Using a TTL gate to sink instead of source allows 20x the current!