

Electronics Analog and Digital Grounds

Terry Sturtevant

Wilfrid Laurier University

May 31, 2017

Analog and Digital Grounds

Analog and Digital Grounds

- digital noise; fast, lots of current

Analog and Digital Grounds

- digital noise; fast, lots of current
- analog noise; slow, low current


Connection resistance

Connection resistance

Consider a trace on a circuit board.


Connection resistance

Consider a trace on a circuit board.

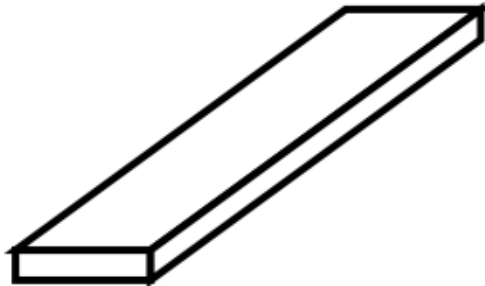


Connection resistance

Consider a trace on a circuit board.

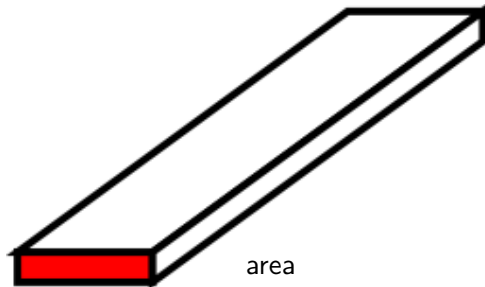

Connection resistance

Consider a trace on a circuit board.

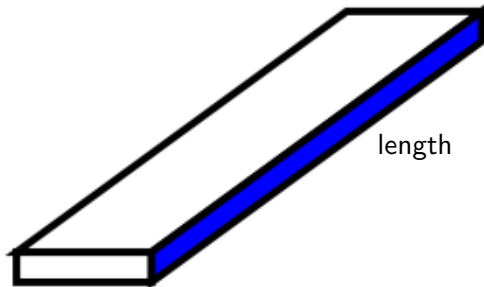

Connection resistance

Connection resistance

- Copper resistivity $\rho \approx 1.56 \times 10^{-8} \Omega - m$

Connection resistance

- Copper resistivity $\rho \approx 1.56 \times 10^{-8} \Omega - m$
- Trace dimensions $\approx mm \times mm / 100 \times length(cm)$

Connection resistance

- Copper resistivity $\rho \approx 1.56 \times 10^{-8} \Omega - m$
- Trace dimensions $\approx mm \times mm / 100 \times length(cm)$
- Resistance $R \approx 10^{-8} length / (10^{-3} \times 10^{-5}) \rightarrow 1 \Omega / m$

Connection resistance

- Copper resistivity $\rho \approx 1.56 \times 10^{-8} \Omega - m$
- Trace dimensions $\approx mm \times mm / 100 \times length(cm)$
- Resistance $R \approx 10^{-8} length / (10^{-3} \times 10^{-5}) \rightarrow 1 \Omega / m$
- Voltage fluctuation on lines $\Delta V = (\Delta I) R$;

Connection resistance

- Copper resistivity $\rho \approx 1.56 \times 10^{-8} \Omega - m$
- Trace dimensions $\approx mm \times mm/100 \times length(cm)$
- Resistance $R \approx 10^{-8} length / (10^{-3} \times 10^{-5}) \rightarrow 1 \Omega/m$
- Voltage fluctuation on lines $\Delta V = (\Delta I) R$;

Thus mA fluctuation \rightarrow mV/m fluctuation.

Connection resistance

- Copper resistivity $\rho \approx 1.56 \times 10^{-8} \Omega - m$
- Trace dimensions $\approx mm \times mm / 100 \times length(cm)$
- Resistance $R \approx 10^{-8} length / (10^{-3} \times 10^{-5}) \rightarrow 1 \Omega / m$
- Voltage fluctuation on lines $\Delta V = (\Delta I) R$;

Thus mA fluctuation \rightarrow mV/m fluctuation. *This includes fluctuations on power and ground lines.*

Connection resistance

- Copper resistivity $\rho \approx 1.56 \times 10^{-8} \Omega - m$
- Trace dimensions $\approx mm \times mm / 100 \times length(cm)$
- Resistance $R \approx 10^{-8} length / (10^{-3} \times 10^{-5}) \rightarrow 1 \Omega / m$
- Voltage fluctuation on lines $\Delta V = (\Delta I) R$;

Thus mA fluctuation \rightarrow mV/m fluctuation. *This includes fluctuations on power and ground lines.* The farther you get from power and ground connections, the more noise you get on power and ground lines.

Effect of noise on power and ground lines

Effect of noise on power and ground lines

Analog

Effect of noise on power and ground lines

Analog

Consider an op amp with a gain of 1000

Effect of noise on power and ground lines

Analog

Consider an op amp with a gain of 1000
(inverting amp),

Effect of noise on power and ground lines

Analog

Consider an op amp with a gain of 1000
(inverting amp),
assumes “ground” is zero;

Effect of noise on power and ground lines

Analog

Consider an op amp with a gain of 1000

(inverting amp),

assumes “ground” is zero;

if off by few mv with an input signal of mv, effect could be very large.

Effect of noise on power and ground lines

Analog

Consider an op amp with a gain of 1000

(inverting amp),

assumes “ground” is zero;

if off by few mv with an input signal of mv, effect could be very large.

Digital

Effect of noise on power and ground lines

Analog

Consider an op amp with a gain of 1000

(inverting amp),

assumes “ground” is zero;

if off by few mv with an input signal of mv, effect could be very large.

Digital

May produce glitches.

Solution to noise problems - analog

Solution to noise problems - analog

Digital and analog grounds should be separated to minimize problems with analog signals due to digital noise on power and ground lines.

Solution to noise problems - analog

Digital and analog grounds should be separated to minimize problems with analog signals due to digital noise on power and ground lines.


Keep separate power and grounds (so digital noise absent);

Solution to noise problems - analog


Digital and analog grounds should be separated to minimize problems with analog signals due to digital noise on power and ground lines.

Keep separate power and grounds (so digital noise absent); only join once near supply.


Separate grounds; MCP3008 (Microchip)

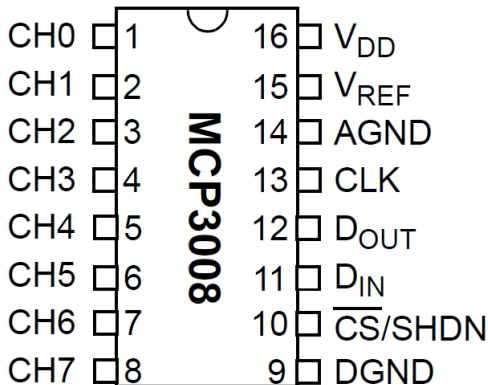

Separate grounds; MCP3008 (Microchip)

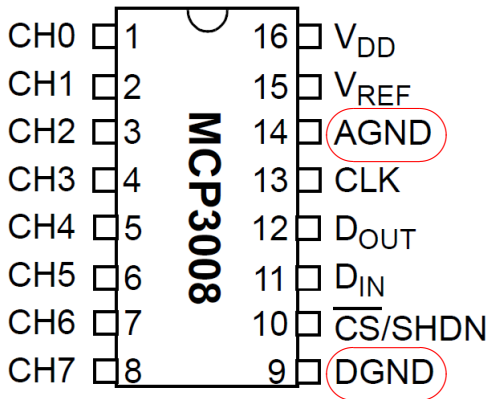

Separate grounds; MCP3008 (Microchip)

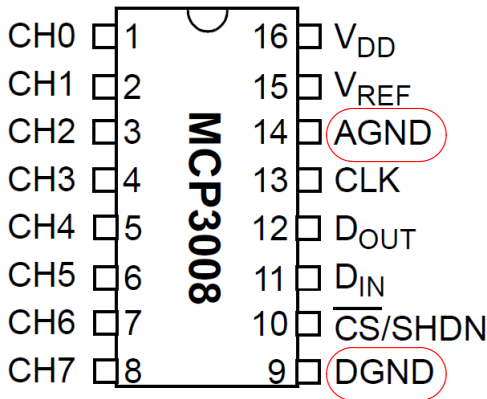

"If no ground plane is utilized, both grounds must be connected to V_{SS} on the board."

From MCP3008 datasheet (Microchip)

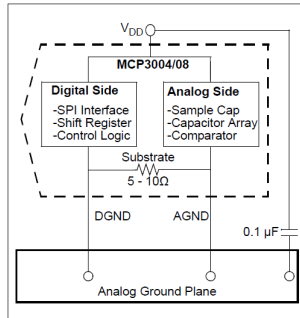


FIGURE 6-5: Separation of Analog and Digital Ground Pins.

From MCP3008 datasheet (Microchip)


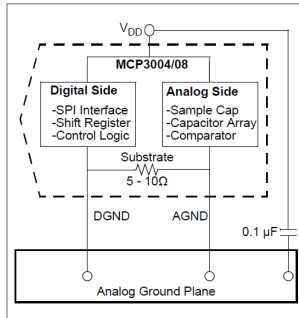



FIGURE 6-5: Separation of Analog and Digital Ground Pins.

“If a ground plane is available, both digital and analog ground pins should be connected to the analog ground plane.”

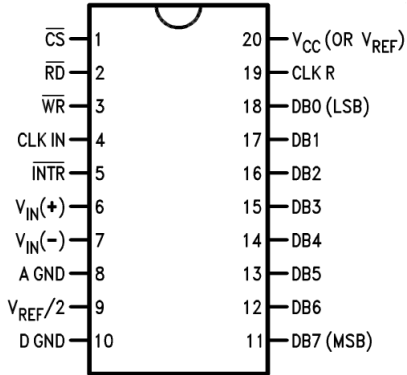
Separate grounds; ADC0804 (National Semiconductor)



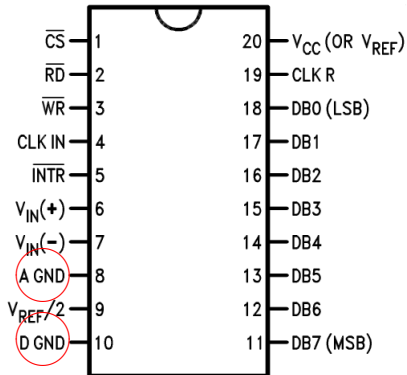Separate grounds; ADC0804 (National Semiconductor)




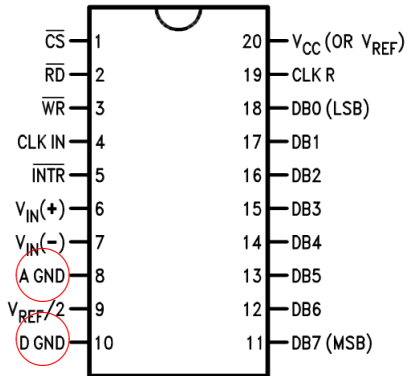Separate grounds; ADC0804 (National Semiconductor)




"Note: The separate A Gnd point should always be wired to the D Gnd."

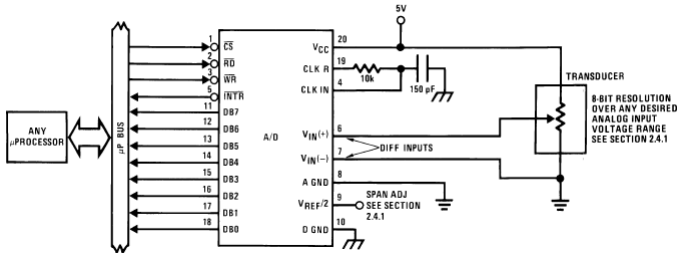From ADC0804 datasheet (National Semiconductor)



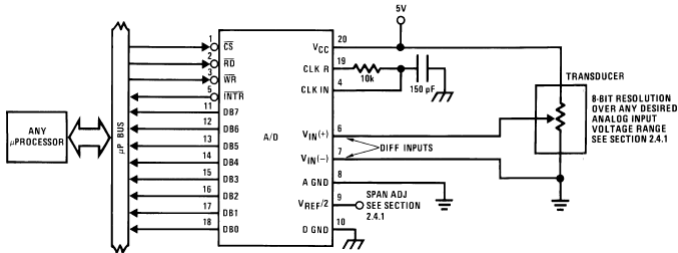From ADC0804 datasheet (National Semiconductor)



Can you identify which symbol is for each type of ground?

Solution to noise problems - digital


Solution to noise problems - digital

Use filter capacitors from V_{CC} to ground near IC to smooth the fluctuations as close to the device as possible;


Solution to noise problems - digital

Use filter capacitors from V_{CC} to ground near IC to smooth the fluctuations as close to the device as possible; The value is typically $0.01 \rightarrow 0.1\mu F$

Filter capacitors

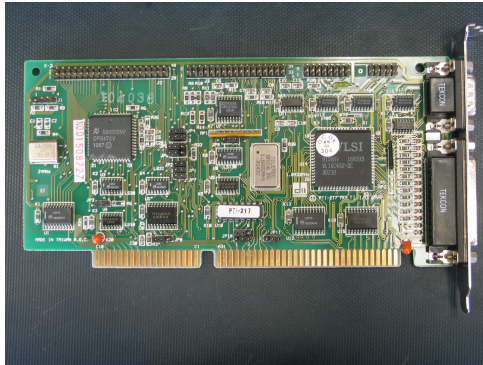

Filter capacitors

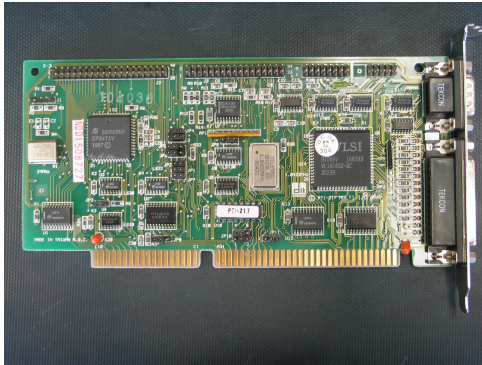

Here's an ordinary circuit board.

Filter capacitors



Filter capacitors



Notice the filter capacitors.

Filter capacitors




Notice the filter capacitors.

Filter capacitors




Notice the filter capacitors.

Filter capacitors

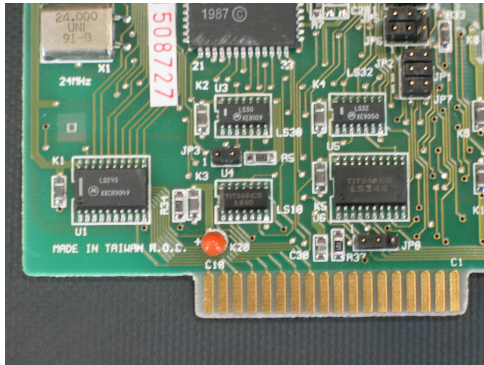


Here are more.

Filter capacitors

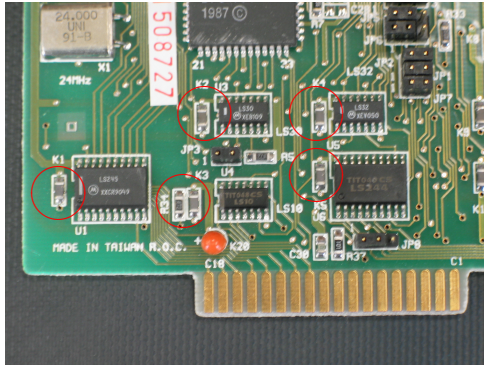


Here are more.

Filter capacitors

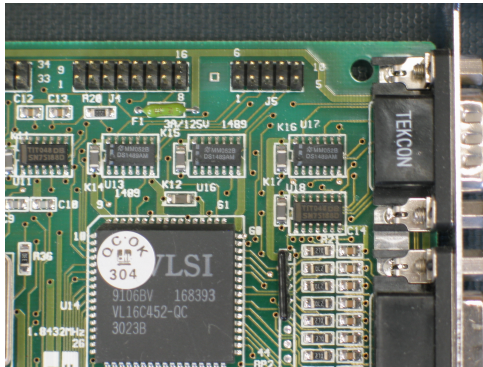

Find some more.

Filter capacitors

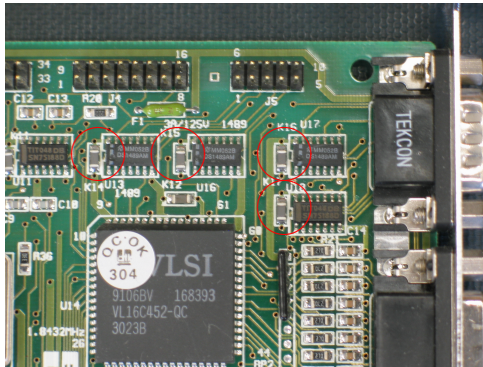

Find some more.