

Electronics

Uses of Differential Amplifier Circuits


Terry Sturtevant

Wilfrid Laurier University

October 18, 2017

Differential amplifier

Differential amplifier

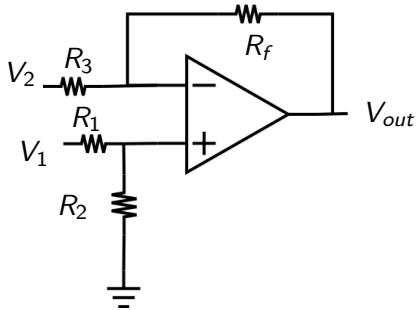

$$V_{out} = \frac{V_1 R_2}{R_1 + R_2} \left(1 + \frac{R_f}{R_3} \right) - V_2 \frac{R_f}{R_3}$$

$$V_{out} = \frac{V_1 R_2}{R_1 + R_2} \left(1 + \frac{R_f}{R_3} \right) - V_2 \frac{R_f}{R_3}$$

Simplified if $R_f = R_2$ and $R_1 = R_3$

$$V_{out} = \frac{V_1 R_2}{R_1 + R_2} \left(1 + \frac{R_f}{R_3} \right) - V_2 \frac{R_f}{R_3}$$

Simplified if $R_f = R_2$ and $R_1 = R_3$

$$\therefore V_{out} = \frac{R_f}{R_1} (V_1 - V_2)$$

$$V_{out} = \frac{V_1 R_2}{R_1 + R_2} \left(1 + \frac{R_f}{R_3} \right) - V_2 \frac{R_f}{R_3}$$

Simplified if $R_f = R_2$ and $R_1 = R_3$

$$\therefore V_{out} = \frac{R_f}{R_1} (V_1 - V_2)$$

If all resistors are equal, $V_{out} = V_1 - V_2$

Uses of Differential Amplifiers

Uses of Differential Amplifiers

- 1 differential signals

Uses of Differential Amplifiers

- 1 differential signals
e.g. Wheatstone bridge

Uses of Differential Amplifiers

- 1 differential signals
e.g. Wheatstone bridge
- 2 signals which never reach zero

Uses of Differential Amplifiers

- 1 differential signals
e.g. Wheatstone bridge
- 2 signals which never reach zero
e.g. voltage divider

Uses of Differential Amplifiers

- 1 differential signals
e.g. Wheatstone bridge
- 2 signals which never reach zero
e.g. voltage divider
- 3 signals which vary in the “wrong” *direction*

Uses of Differential Amplifiers

- 1 differential signals
e.g. Wheatstone bridge
- 2 signals which never reach zero
e.g. voltage divider
- 3 signals which vary in the “wrong” *direction*
similar to “inverting” a signal in a single supply configuration

Differential Signals

Differential Signals

- Some circuits produce *pairs* of outputs

Differential Signals

- Some circuits produce *pairs* of outputs
e.g. Wheatstone bridge

Differential Signals

- Some circuits produce *pairs* of outputs
e.g. Wheatstone bridge
- The *difference* between the outputs is the quantity of interest

Differential Signals

- Some circuits produce *pairs* of outputs
e.g. Wheatstone bridge
- The *difference* between the outputs is the quantity of interest
- A differential amplifier allows you to subtract *one signal from another signal*

Signals which never reach zero

Signals which never reach zero

- Some circuits produce signals which never reach zero

Signals which never reach zero

- Some circuits produce signals which never reach zero
e.g. voltage divider

Signals which never reach zero

- Some circuits produce signals which never reach zero
e.g. voltage divider
- It is often more useful if the minimum output is zero

Signals which never reach zero

- Some circuits produce signals which never reach zero
e.g. voltage divider
- It is often more useful if the minimum output is zero
- A differential amplifier allows you to subtract *a fixed voltage from the signal*

Signals which vary in the “wrong” direction

Signals which vary in the “wrong” direction

- Some circuits produce signals which vary opposite to the desired direction

Signals which vary in the “wrong” direction

- Some circuits produce signals which vary opposite to the desired direction
e.g. a light sensor which produces a higher voltage as the light gets dimmer

Signals which vary in the “wrong” direction

- Some circuits produce signals which vary opposite to the desired direction
e.g. a light sensor which produces a higher voltage as the light gets dimmer
- It is often more useful to have the variation in the other direction

Signals which vary in the “wrong” direction

- Some circuits produce signals which vary opposite to the desired direction
e.g. a light sensor which produces a higher voltage as the light gets dimmer
- It is often more useful to have the variation in the other direction
- A differential amplifier allows you to subtract *the signal from a fixed voltage*

Signals which vary in the “wrong” direction

- Some circuits produce signals which vary opposite to the desired direction
e.g. a light sensor which produces a higher voltage as the light gets dimmer
- It is often more useful to have the variation in the other direction
- A differential amplifier allows you to subtract *the signal from a fixed voltage*

In a dual supply configuration, an inverting amplifier could be used, but this works with a single supply as well.

Scaling fixed voltages

Scaling fixed voltages

$$V_{out} = \frac{V_1 R_2}{R_1 + R_2} \left(1 + \frac{R_f}{R_3} \right) - V_2 \frac{R_f}{R_3}$$

Scaling fixed voltages

$$V_{out} = \frac{V_1 R_2}{R_1 + R_2} \left(1 + \frac{R_f}{R_3} \right) - V_2 \frac{R_f}{R_3}$$

Simplified if $R_f = R_2$ and $R_1 = R_3$

Scaling fixed voltages

$$V_{out} = \frac{V_1 R_2}{R_1 + R_2} \left(1 + \frac{R_f}{R_3} \right) - V_2 \frac{R_f}{R_3}$$

Simplified if $R_f = R_2$ and $R_1 = R_3$

$$\therefore V_{out} = \frac{R_f}{R_1} (V_1 - V_2)$$

Scaling fixed voltages

$$V_{out} = \frac{V_1 R_2}{R_1 + R_2} \left(1 + \frac{R_f}{R_3} \right) - V_2 \frac{R_f}{R_3}$$

Simplified if $R_f = R_2$ and $R_1 = R_3$

$$\therefore V_{out} = \frac{R_f}{R_1} (V_1 - V_2)$$

If all resistors are equal, $V_{out} = V_1 - V_2$

Scaling fixed voltages

$$V_{out} = \frac{V_1 R_2}{R_1 + R_2} \left(1 + \frac{R_f}{R_3} \right) - V_2 \frac{R_f}{R_3}$$

Simplified if $R_f = R_2$ and $R_1 = R_3$

$$\therefore V_{out} = \frac{R_f}{R_1} (V_1 - V_2)$$

If all resistors are equal, $V_{out} = V_1 - V_2$

If the fixed voltages are not what you want, you can adjust the resistor values instead.