

Electronics H-Bridges and DC Motors

Terry Sturtevant

Wilfrid Laurier University

April 22, 2019

DC motor

DC motor

- PMDC (Permanent Magnet DC)

DC motor

- PMDC (Permanent Magnet DC)
- uses permanent fixed magnets

DC motor

- PMDC (Permanent Magnet DC)
- uses permanent fixed magnets
armature on shaft has electromagnet

DC motor

- PMDC (Permanent Magnet DC)
- uses permanent fixed magnets
armature on shaft has electromagnet
commutator on shaft reverses current direction every half rotation

DC motor

- PMDC (Permanent Magnet DC)
- uses permanent fixed magnets
armature on shaft has electromagnet
commutator on shaft reverses current direction every half rotation
- speed controlled by current


DC motor

- PMDC (Permanent Magnet DC)
- uses permanent fixed magnets
armature on shaft has electromagnet
commutator on shaft reverses current direction every half rotation
- speed controlled by current
- direction controlled by polarity


DC motor

- PMDC (Permanent Magnet DC)
- uses permanent fixed magnets
armature on shaft has electromagnet
commutator on shaft reverses current direction every half rotation
- speed controlled by current
- direction controlled by polarity
- continuous motion


Permanent magnet DC motor

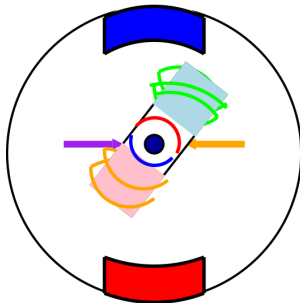


Permanent magnet DC motor

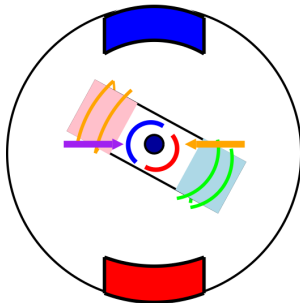


Permanent magnet DC motor

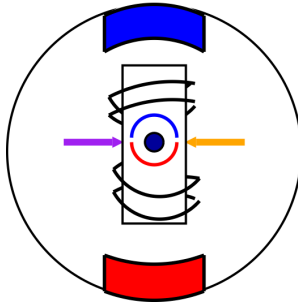


Permanent magnet DC motor

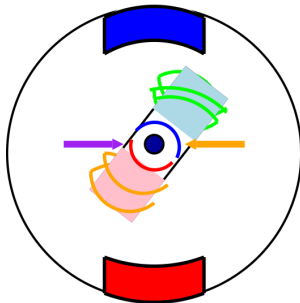

Permanent magnet DC motor

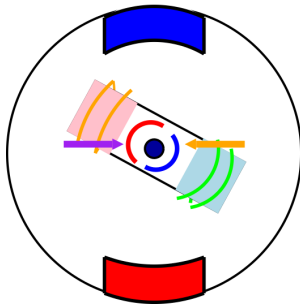

Permanent magnet DC motor

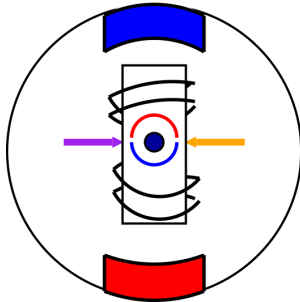

H-Bridge

H-Bridge

- Allows a DC motor to run in either direction with a single supply

H-Bridge

- Allows a DC motor to run in either direction with a single supply
- uses four transistors

H-Bridge

- Allows a DC motor to run in either direction with a single supply
- uses four transistors
either BJTs or FETs can be used

H-Bridge

- Allows a DC motor to run in either direction with a single supply
- uses four transistors
either BJTs or FETs can be used
- only two transistors are “on” at a time

Transistors

Transistors

- There are several types of transistor; each is a three terminal device.

Transistors

- There are several types of transistor; each is a three terminal device.
- The most common types of transistors are BJTs and FETs.

Transistors

- There are several types of transistor; each is a three terminal device.
- The most common types of transistors are BJTs and FETs.
- Transistors are often used in voltage dividers to act as variable resistors.

Metal Oxide Semiconductor Field Effect Transistors

Metal Oxide Semiconductor Field Effect Transistors

A MOSFET (or Metal Oxide Semiconductor Field Effect Transistor) is a three terminal device.

Metal Oxide Semiconductor Field Effect Transistors

A MOSFET (or Metal Oxide Semiconductor Field Effect Transistor) is a three terminal device.

- drain

Metal Oxide Semiconductor Field Effect Transistors

A MOSFET (or Metal Oxide Semiconductor Field Effect Transistor) is a three terminal device.

- drain
- source

Metal Oxide Semiconductor Field Effect Transistors


A MOSFET (or Metal Oxide Semiconductor Field Effect Transistor) is a three terminal device.

- drain
- source
- gate


FET symbol




FET symbol

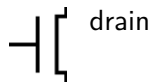

FET symbol

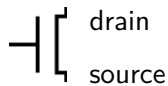

FET symbol

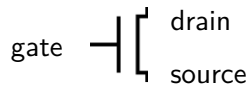

FET operation

- FETS are *voltage* amplifiers; a small **gate voltage** controls a much larger **drain/source current**.

FET operation

- FETS are *voltage* amplifiers; a small **gate voltage** controls a much larger **drain/source current**.

Actually it's the voltage between the gate and the source which matters.

D and E MOSFETs

D and E MOSFETs

There are two kinds of MOSFET

D and E MOSFETs

There are two kinds of MOSFET

- enhancement mode (E type)

D and E MOSFETs

There are two kinds of MOSFET

- enhancement mode (E type)

When V_{gs} is below V_{th} , $I_D = 0$

D and E MOSFETs

There are two kinds of MOSFET

- enhancement mode (E type)

When V_{gs} is below V_{th} , $I_D = 0$

As V_{gs} increases above V_{th} ,

D and E MOSFETs

There are two kinds of MOSFET

- enhancement mode (E type)

When V_{gs} is below V_{th} , $I_D = 0$

As V_{gs} increases above V_{th} ,

I_D increases.

D and E MOSFETs

There are two kinds of MOSFET

- enhancement mode (E type)

When V_{gs} is below V_{th} , $I_D = 0$

As V_{gs} increases above V_{th} ,
 I_D increases.

- depletion mode (D type)

D and E MOSFETs

There are two kinds of MOSFET

- enhancement mode (E type)

When V_{gs} is below V_{th} , $I_D = 0$

As V_{gs} increases above V_{th} ,
 I_D increases.

- depletion mode (D type)

To get I_D to zero, a *negative* $V_{gs_{off}}$ must be applied.

D and E MOSFETs

There are two kinds of MOSFET

- enhancement mode (E type)

When V_{gs} is below V_{th} , $I_D = 0$

As V_{gs} increases above V_{th} ,
 I_D increases.

- depletion mode (D type)

To get I_D to zero, a *negative* $V_{gs_{off}}$ must be applied.

In an H-bridge, you want E-MOSFETS so no current flows with no applied gate-source voltage.

Bipolar Junction Transistors

Bipolar Junction Transistors

A BJT (or Bipolar Junction Transistor) is a three terminal *current* device.

Bipolar Junction Transistors

A BJT (or Bipolar Junction Transistor) is a three terminal *current* device. The terminals are

Bipolar Junction Transistors

A BJT (or Bipolar Junction Transistor) is a three terminal *current* device. The terminals are

- collector

Bipolar Junction Transistors

A BJT (or Bipolar Junction Transistor) is a three terminal *current* device. The terminals are

- collector
- emitter

Bipolar Junction Transistors

A BJT (or Bipolar Junction Transistor) is a three terminal *current* device. The terminals are

- collector
- emitter
- base


Bipolar Junction Transistors


A BJT (or Bipolar Junction Transistor) is a three terminal *current* device. The terminals are


- collector
- emitter
- base

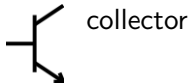The current from the collector to the emitter is controlled by the *current* into the base.





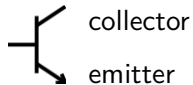

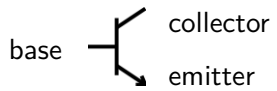

BJT operation

BJT operation

- BJTS are *current* amplifiers;


BJT operation

- BJTs are *current* amplifiers; a small **base** current controls a much larger **collector/emitter** current.


BJT operation

- BJTS are *current* amplifiers; a small **base** current controls a much larger **collector/emitter** current.
- *You should always have a base resistor with a BJT!*

H bridge (shown with BJTs)

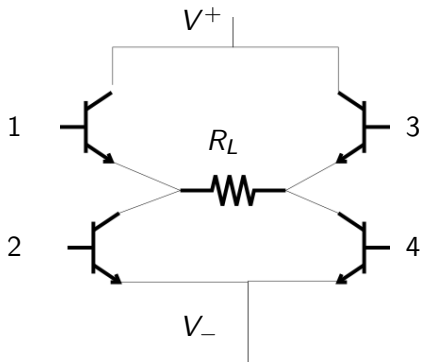


H bridge (shown with BJTs)

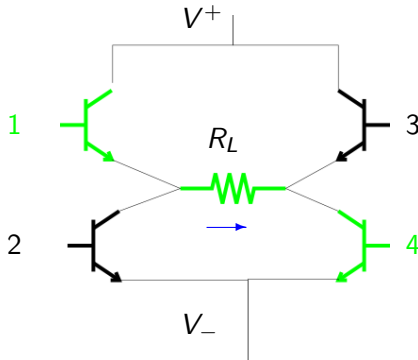

Current flows from left to right.

H bridge (shown with BJTs)

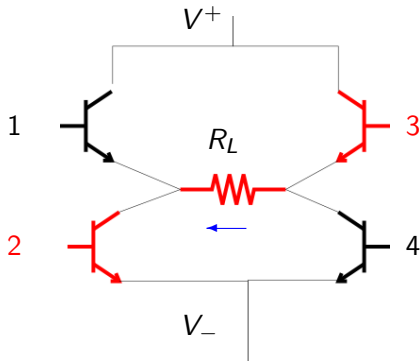

Current flows from right to left.

EMF considerations

EMF considerations

- inductive loads require a few special considerations

EMF considerations

- inductive loads require a few special considerations
- a motor is an inductive load

Induced EMF

Induced EMF

- Quickly changing voltage across inductor produces *induced EMF*

Induced EMF

- Quickly changing voltage across inductor produces *induced EMF*
induced voltage tries to counteract change in current

Induced EMF

- Quickly changing voltage across inductor produces *induced EMF*
induced voltage tries to counteract change in current
can produce big voltage spikes


Induced EMF

- Quickly changing voltage across inductor produces *induced EMF*
induced voltage tries to counteract change in current
can produce big voltage spikes
- A diode across a coil will limit voltages to $\approx 0.7V$.

Induced EMF


- Quickly changing voltage across inductor produces *induced EMF*
induced voltage tries to counteract change in current
can produce big voltage spikes
- A diode across a coil will limit voltages to $\approx 0.7V$.
A zener diode can limit voltages the other way to about the zener voltage.

No diode to reduce induced EMF

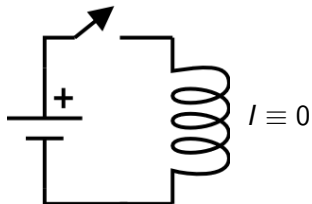


Initially $I = 0$.

No diode to reduce induced EMF

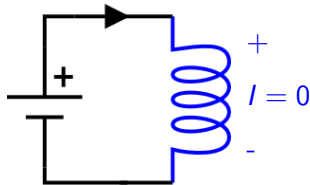


Induced voltage tries to maintain $I = 0$.

No diode to reduce induced EMF

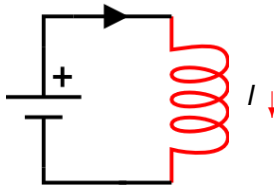


Eventually current is established determined by resistance in circuit.

No diode to reduce induced EMF

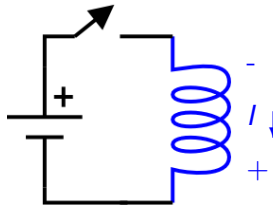


Induced voltage tries to maintain I at the previous value.

No diode to reduce induced EMF

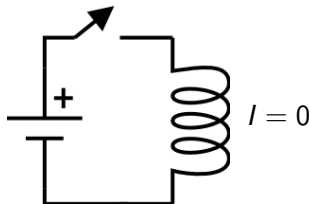


Eventually current is reduced to $I = 0$.

Diode to reduce induced EMF

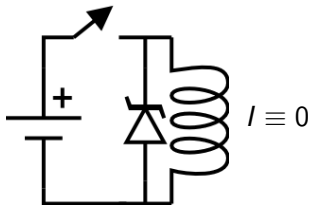


Initially $I = 0$.

Diode to reduce induced EMF

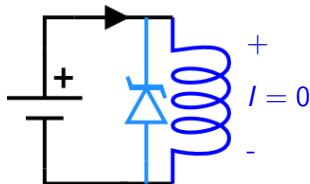


Induced voltage tries to maintain $I = 0$, *but cannot exceed V_Z .*

Diode to reduce induced EMF

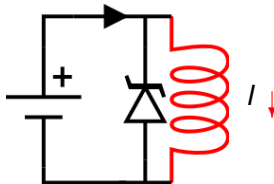


Eventually current is established determined by resistance in circuit.

Diode to reduce induced EMF

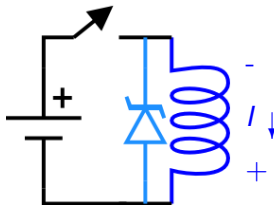


Induced voltage tries to maintain I but cannot exceed $\approx 0.7V$.

Diode to reduce induced EMF

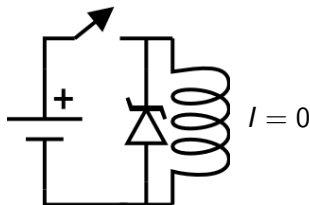

Eventually current is reduced to $I = 0$.

H bridge with diodes included

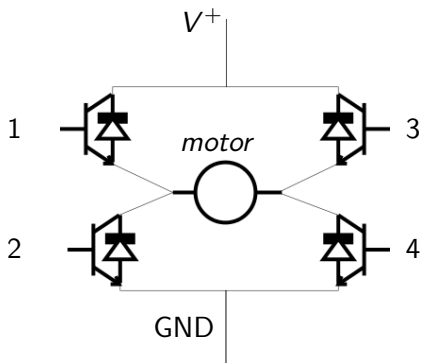

Diodes across the transistors

Diodes across the transistors

- Putting a diode across each transistor keeps the voltage from spiking at the terminals.

Diodes across the transistors

- Putting a diode across each transistor keeps the voltage from spiking at the terminals.
- This includes the base or gate.

Diodes across the transistors

- Putting a diode across each transistor keeps the voltage from spiking at the terminals.
- This includes the base or gate.
- This will prevent spike getting to *whatever is controlling it*.

L9110 H-bridge

L9110 H-bridge


- There are several H-bridge chips available.

L9110 H-bridge


- There are several H-bridge chips available.
- The L9110 is one example.

L9110 H-bridge

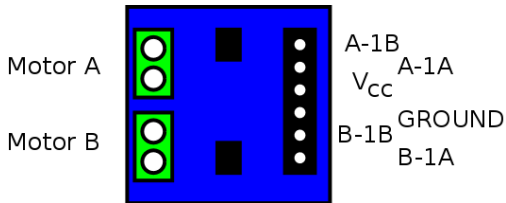
- There are several H-bridge chips available.
- The L9110 is one example.
- There are boards with two allowing independent control of two motors.



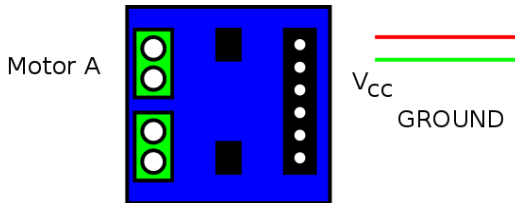All the two motors have in common are the supply voltages.



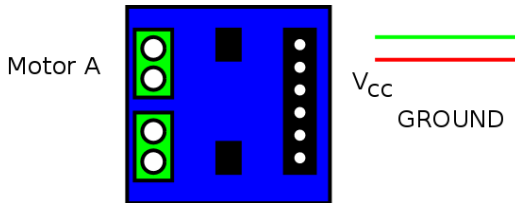If the 1A input is HIGH and the 1B input is LOW, the motor will run in one direction.



If the 1A input is LOW and the 1B input is HIGH, the motor will run in the other direction.

Controlling Speed

Controlling Speed

- Controlling the base current or gate voltage may be difficult.

Controlling Speed

- Controlling the base current or gate voltage may be difficult.
- However, pulse-width-modulation allows you to control the *average* power.

Controlling Speed


- Controlling the base current or gate voltage may be difficult.
- However, pulse-width-modulation allows you to control the *average* power.
- This is the easy way to control speed.

Controlling Speed

- Controlling the base current or gate voltage may be difficult.
- However, pulse-width-modulation allows you to control the *average* power.
- This is the easy way to control speed.


As long as the frequency is high enough, mechanical inertia will make the motion smooth.

Pulse width modulation to limit current

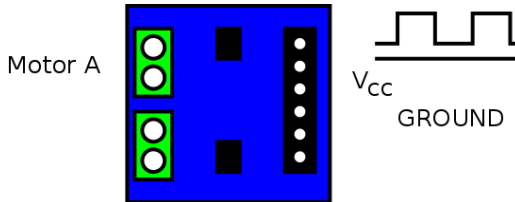


PWM can be used on one input..

Pulse width modulation to limit current

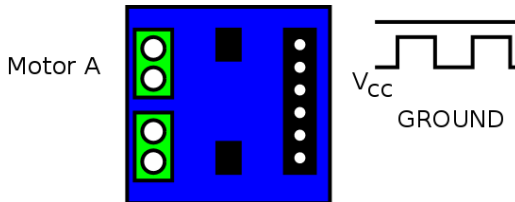


or the other.

Pulse width modulation to limit current

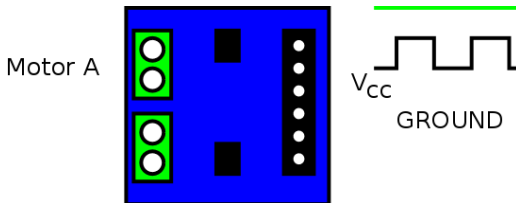


Alternatively, you can use PWM on one input..

Pulse width modulation to limit current

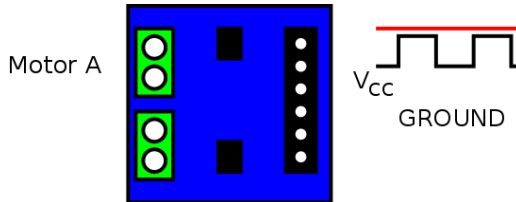

and control direction with the other.

Pulse width modulation to limit current

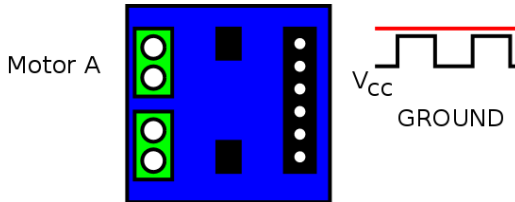

In this case *decreasing* the duty cycle will *increase* power in one direction.