

Electronics Kirchhoff's Law Example

Terry Sturtevant

Wilfrid Laurier University

May 31, 2017

Analyzing the behaviour of DC circuits involving *only* DC (i.e. unchanging in time) voltage sources and **ohmic** devices can be done using **Kirchhoff's Laws**.

*All of these calculations assume that the current through a device is **proportional** to the voltage across the device.*

*All of these calculations assume that the current through a device is **proportional** to the voltage across the device. A device for which this is true is considered “ohmic”.*

*All of these calculations assume that the current through a device is **proportional** to the voltage across the device.*

A device for which this is true is considered “ohmic”.

For many devices the relationship may be far more complex, and so the equations relating voltages and currents in the circuit become non-linear and are much harder to solve.

Kirchhoff's **C**urrent Law

Kirchhoff's **Current** Law

At any point in a circuit, the sum of the currents flowing toward the point is equal to the sum of the currents flowing away from the point;

Kirchhoff's **Current** Law

At any point in a circuit, the sum of the currents flowing toward the point is equal to the sum of the currents flowing away from the point; or, the algebraic sum of all the currents flowing toward a node is equal to zero.

Kirchhoff's **C**urrent Law

At any point in a circuit, the sum of the currents flowing toward the point is equal to the sum of the currents flowing away from the point; or, the algebraic sum of all the currents flowing toward a node is equal to zero.

$$\sum I = 0$$

Kirchhoff's **Voltage** Law

Kirchhoff's **Voltage** Law

In any closed circuit, the algebraic sum of all the voltages around the loop is equal to zero;

Kirchhoff's **Voltage** Law

In any closed circuit, the algebraic sum of all the voltages around the loop is equal to zero; or, the sum of all voltage sources is equal to the sum of all IR drops.

Kirchhoff's **Voltage** Law

In any closed circuit, the algebraic sum of all the voltages around the loop is equal to zero; or, the sum of all voltage sources is equal to the sum of all IR drops. (In this case “voltage sources” can be positive or negative.)

Kirchhoff's **Voltage** Law

In any closed circuit, the algebraic sum of all the voltages around the loop is equal to zero; or, the sum of all voltage sources is equal to the sum of all IR drops. (In this case “voltage sources” can be positive or negative.)

$$\sum V = \sum IR$$

The path around a loop is a series of voltage “steps”, in which, at the end of the loop, you must return to the same voltage you started with.

The path around a loop is a series of voltage “steps”, in which, at the end of the loop, you must return to the same voltage you started with. There are only two kinds of voltages in the circuit:

The path around a loop is a series of voltage “steps”, in which, at the end of the loop, you must return to the same voltage you started with. There are only two kinds of voltages in the circuit:

- those due to **sources**, such as batteries,

The path around a loop is a series of voltage “steps”, in which, at the end of the loop, you must return to the same voltage you started with. There are only two kinds of voltages in the circuit:

- those due to **sources**, such as batteries,
- those due to **sinks**, which are resistors.

The path around a loop is a series of voltage “steps”, in which, at the end of the loop, you must return to the same voltage you started with. There are only two kinds of voltages in the circuit:

- those due to **sources**, such as batteries,
- those due to **sinks**, which are resistors.

By Ohm's law, the voltage across a resistor is IR .

The way that these laws are applied to analyze a circuit involves choosing **nodes** in the circuit for the first law and using **loops** in the circuit for the second and producing equations from each node and loop.

After the equations are created, determining the currents in the circuit is accomplished by solving the equations simultaneously.

After the equations are created, determining the currents in the circuit is accomplished by solving the equations simultaneously. In this case, the system we must solve is of the form

After the equations are created, determining the currents in the circuit is accomplished by solving the equations simultaneously. In this case, the system we must solve is of the form

$$AX = B$$

After the equations are created, determining the currents in the circuit is accomplished by solving the equations simultaneously. In this case, the system we must solve is of the form

$$AX = B$$

where A is the coefficient matrix and X is the vector of the currents.

After the equations are created, determining the currents in the circuit is accomplished by solving the equations simultaneously. In this case, the system we must solve is of the form

$$AX = B$$

where A is the coefficient matrix and X is the vector of the currents. (Because of the two types of equations used, B is a vector of voltages and zeros.)

If a solution exists, it may be found by

If a solution exists, it may be found by

$$X = A^{-1}B$$

If a solution exists, it may be found by

$$X = A^{-1}B$$

where A^{-1} is the inverse of the coefficient matrix.

If a solution exists, it may be found by

$$X = A^{-1}B$$


where A^{-1} is the inverse of the coefficient matrix. (A solution will not exist if you have, for instance, erroneously connected two different voltage sources in parallel.)

So far no mention has been made of the *dimension* of the coefficient matrix.


So far no mention has been made of the *dimension* of the coefficient matrix. Clearly, to be invertible A must be square, however you will probably have many more equations than currents.

So far no mention has been made of the *dimension* of the coefficient matrix. Clearly, to be invertible A must be square, however you will probably have many more equations than currents. This is because the equations are *not* all **linearly independent**.

 
So far no mention has been made of the *dimension* of the coefficient matrix. Clearly, to be invertible A must be square, however you will probably have many more equations than currents. This is because the equations are *not* all **linearly independent**. In other words, some of the equations are redundant, and will have to be eliminated for the system to be solvable.




Label all V's and R's.

 


Label all V's and R's.

 


Label all V's and R's.

 


Label all V's and R's.

 


Label all V's and R's.

 


Label all V's and R's.

 

 
Label all I 's to go with R 's and pick directions for I 's.



 
Label all I 's to go with R 's and pick directions for I 's.



 
Label all I 's to go with R 's and pick directions for I 's.




Label loops.

 


Label loops.

 

Label loops.

 

Label nodes.

 

Label nodes.

Making loop equations

Making loop equations

For each loop:

Making loop equations

For each loop:

- 1 Start at node, go around to first component.

Making loop equations

For each loop:

- 1 Start at node, go around to first component.
- 2 If component is a battery, count the voltage as *positive* if you come to the '-' terminal first.

Making loop equations

For each loop:

- 1 Start at node, go around to first component.
- 2 If component is a battery, count the voltage as *positive* if you come to the '-' terminal first.
- 3 If component is a resistor, count the IR as *positive* if you come to the resistor going *against* the current.

Making loop equations

For each loop:


- 1 Start at node, go around to first component.
- 2 If component is a battery, count the voltage as *positive* if you come to the '-' terminal first.
- 3 If component is a resistor, count the IR as *positive* if you come to the resistor going *against* the current.
- 4 Repeat for all components until you are back at the node.

Making loop equations


For each loop:

- 1 Start at node, go around to first component.
- 2 If component is a battery, count the voltage as *positive* if you come to the '-' terminal first.
- 3 If component is a resistor, count the IR as *positive* if you come to the resistor going *against* the current.
- 4 Repeat for all components until you are back at the node.
- 5 Set the sum of all of the contributions from 2 and 3 to zero.

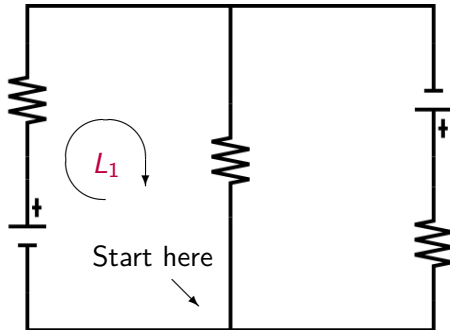
Here's how the equation for Loop 1 is created.



 
Start at the lower right corner of this loop.




V_1 is the first thing we encounter.

 

 
V_1 is *positive* since we hit the negative terminal first.




R_1 is the next thing we encounter.

 

 
$I_1 R_1$ is *negative* since the loop direction *matches* the current direction.




R_3 is next.

 


 $I_3 R_3$ is *positive* since the loop direction *opposes* the current direction.




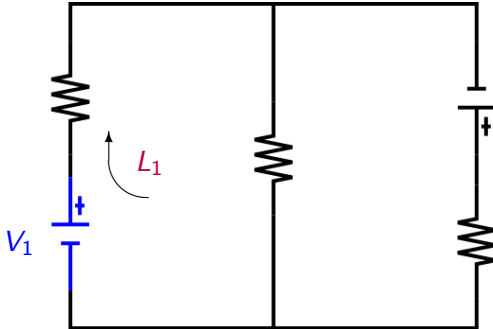


$$+V_1$$

 

$$+V_1 - I_1 R_1$$

 

$$+V_1 - I_1 R_1 + I_3 R_3$$

 

$$+V_1 - I_1 R_1 + I_3 R_3 = 0$$

Thus for the example above:

Thus for the example above:
Loop 1 (starting at Node 1)

Thus for the example above:
Loop 1 (starting at Node 1)

$$V_1 - I_1 R_1 + I_3 R_3 = 0$$

Thus for the example above:

Loop 1 (starting at Node 1)

$$V_1 - I_1 R_1 + I_3 R_3 = 0$$

Loop 2 (starting at Node 2)

$$V_2 - I_2 R_2 - I_3 R_3 = 0$$

Thus for the example above:

Loop 1 (starting at Node 1)

$$V_1 - I_1 R_1 + I_3 R_3 = 0$$

Loop 2 (starting at Node 2)

$$V_2 - I_2 R_2 - I_3 R_3 = 0$$

Loop 3 (starting at Node 1)

$$V_1 - I_1 R_1 + V_2 - I_2 R_2 = 0$$

Making node equations

Making node equations

For each node:

Making node equations

For each node:


- 1 Currents coming *into* node are *positive*, others are *negative*.

Making node equations


For each node:

- 1 Currents coming *into* node are *positive*, others are *negative*.
- 2 Set the sum of all of the contributions from 1 to zero.

 
Here's how the equation for Node 1 is created.




Here is Node 1.

 


I_1 and I_3 go into Node 1.

 

I_2 comes out of Node 1.

 

$$I_1 + I_3 = I_2$$

 

$$I_1 + I_3 - I_2 = 0$$

Thus for the example above:

Thus for the example above:
Node 1

$$I_2 - I_3 - I_1 = 0$$

Thus for the example above:

Node 1

$$I_2 - I_3 - I_1 = 0$$

Node 2

$$I_1 + I_3 - I_2 = 0$$

Set up a system of equations.

Set up a system of equations. Thus for the example above:

Set up a system of equations. Thus for the example above:

$$\begin{array}{l} \text{Loop 1 :} \\ \text{Loop 2 :} \\ \text{Loop 3 :} \\ \text{Node 1 :} \\ \text{Node 2 :} \end{array} \begin{array}{r} -I_1 R_1 \\ \\ -I_1 R_1 \\ -I_1 \\ +I_1 \end{array} \begin{array}{r} \\ -I_2 R_2 \\ -I_2 R_2 \\ +I_2 \\ -I_2 \end{array} \begin{array}{r} +I_3 R_3 \\ -I_3 R_3 \\ \\ -I_3 \\ +I_3 \end{array} = \begin{array}{r} -V_1 \\ -V_2 \\ -V_1 - V_2 \\ 0 \\ 0 \end{array}$$

Create matrices.

Create matrices.
Thus for the example above:

Create matrices.

Thus for the example above:

We can rewrite the above system in matrix form as

Create matrices.

Thus for the example above:

We can rewrite the above system in matrix form as

$$\begin{pmatrix} -R_1 & 0 & +R_3 \\ 0 & -R_2 & -R_3 \\ -R_1 & -R_2 & 0 \\ -1 & +1 & -1 \\ +1 & -1 & +1 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} -V_1 \\ -V_2 \\ -V_1 - V_2 \\ 0 \\ 0 \end{pmatrix}$$

So clearly if we let

So clearly if we let

$$A = \begin{pmatrix} -R_1 & 0 & +R_3 \\ 0 & -R_2 & -R_3 \\ -R_1 & -R_2 & 0 \\ -1 & +1 & -1 \\ +1 & -1 & +1 \end{pmatrix}$$

So clearly if we let

$$A = \begin{pmatrix} -R_1 & 0 & +R_3 \\ 0 & -R_2 & -R_3 \\ -R_1 & -R_2 & 0 \\ -1 & +1 & -1 \\ +1 & -1 & +1 \end{pmatrix}$$

$$X = \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix}$$

So clearly if we let

$$A = \begin{pmatrix} -R_1 & 0 & +R_3 \\ 0 & -R_2 & -R_3 \\ -R_1 & -R_2 & 0 \\ -1 & +1 & -1 \\ +1 & -1 & +1 \end{pmatrix}$$

$$X = \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix}$$

$$B = \begin{pmatrix} -V_1 \\ -V_2 \\ -V_1 - V_2 \\ 0 \\ 0 \end{pmatrix}$$

Then

Then

$$AX = B$$

Reduce coefficient matrix to square, since it will not be invertible otherwise.

Reduce coefficient matrix to square, since it will not be invertible otherwise. Be sure to adjust the solution vector accordingly.

$$A = \begin{pmatrix} -R_1 & 0 & +R_3 \\ 0 & -R_2 & -R_3 \\ -R_1 & -R_2 & 0 \\ -1 & +1 & -1 \\ +1 & -1 & +1 \end{pmatrix}$$

Here's the matrix

$$A = \begin{pmatrix} -R_1 & 0 & +R_3 \\ 0 & -R_2 & -R_3 \\ -R_1 & -R_2 & 0 \\ -1 & +1 & -1 \\ +1 & -1 & +1 \end{pmatrix}$$

Notice row 1

$$A = \begin{pmatrix} -R_1 & 0 & +R_3 \\ 0 & -R_2 & -R_3 \\ -R_1 & -R_2 & 0 \\ -1 & +1 & -1 \\ +1 & -1 & +1 \end{pmatrix}$$

Notice row 1 + row 2

$$A = \begin{pmatrix} -R_1 & 0 & +R_3 \\ 0 & -R_2 & -R_3 \\ -R_1 & -R_2 & 0 \\ -1 & +1 & -1 \\ +1 & -1 & +1 \end{pmatrix}$$

Notice row 1 + row 2 equal row 3, so we can get rid of row 3

$$A = \begin{pmatrix} -R_1 & 0 & +R_3 \\ 0 & -R_2 & -R_3 \\ -R_1 & -R_2 & 0 \\ -1 & +1 & -1 \\ +1 & -1 & +1 \end{pmatrix}$$

Also, row 4

$$A = \begin{pmatrix} -R_1 & 0 & +R_3 \\ 0 & -R_2 & -R_3 \\ -R_1 & -R_2 & 0 \\ -1 & +1 & -1 \\ +1 & -1 & +1 \end{pmatrix}$$

Also, row 4 = -row 5, so get rid of row 5

So we are left with

$$\mathcal{A} = \begin{pmatrix} -R_1 & 0 & +R_3 \\ 0 & -R_2 & -R_3 \\ -1 & +1 & -1 \end{pmatrix}$$

So we are left with

$$\mathcal{A} = \begin{pmatrix} -R_1 & 0 & +R_3 \\ 0 & -R_2 & -R_3 \\ -1 & +1 & -1 \end{pmatrix}$$

and

$$\mathcal{B} = \begin{pmatrix} -V_1 \\ -V_2 \\ 0 \end{pmatrix}$$

after adjustment

Now

$$X = \mathcal{A}^{-1}\mathcal{B}$$

Now

$$X = \mathcal{A}^{-1}\mathcal{B}$$

which gives

Now

$$X = \mathcal{A}^{-1}\mathcal{B}$$

which gives

$$X = \frac{1}{R_2 R_1 + R_2 R_3 + R_1 R_3} \begin{pmatrix} R_3 V_1 + R_3 V_2 + R_2 V_1 \\ R_3 V_1 + R_1 V_2 + R_3 V_2 \\ R_1 V_2 - R_2 V_1 \end{pmatrix}$$

Now

$$X = \mathcal{A}^{-1}\mathcal{B}$$

which gives

$$X = \frac{1}{R_2R_1 + R_2R_3 + R_1R_3} \begin{pmatrix} R_3V_1 + R_3V_2 + R_2V_1 \\ R_3V_1 + R_1V_2 + R_3V_2 \\ R_1V_2 - R_2V_1 \end{pmatrix}$$

Notice that, depending on the voltages involved, some of the currents could be negative.

Now

$$X = \mathcal{A}^{-1}\mathcal{B}$$

which gives

$$X = \frac{1}{R_2R_1 + R_2R_3 + R_1R_3} \begin{pmatrix} R_3V_1 + R_3V_2 + R_2V_1 \\ R_3V_1 + R_1V_2 + R_3V_2 \\ R_1V_2 - R_2V_1 \end{pmatrix}$$

Notice that, depending on the voltages involved, some of the currents could be negative. In this case, it simply means that the actual current goes in the opposite direction from what you had chosen.