

# Electronics

## Logic Gates: Tri-State Output

Terry Sturtevant

Wilfrid Laurier University

May 20, 2011

# Types of logic gate outputs

- Totem pole

# Types of logic gate outputs

- Totem pole

Output is **HIGH** or **LOW**.

# Types of logic gate outputs

- Totem pole  
Output is **HIGH** or **LOW**.
- Open collector

# Types of logic gate outputs

- Totem pole  
Output is HIGH or LOW.
- Open collector  
Output is floating or LOW.

# Types of logic gate outputs

- Totem pole  
Output is **HIGH** or **LOW**.
- Open collector  
Output is **floating** or **LOW**.
- **Tri-state** outputs combine these

# Types of logic gate outputs

- Totem pole  
Output is **HIGH** or **LOW**.
- Open collector  
Output is **floating** or **LOW**.
- **Tri-state** outputs combine these  
Output can be

# Types of logic gate outputs

- Totem pole  
Output is **HIGH** or **LOW**.
- Open collector  
Output is **floating** or **LOW**.
- **Tri-state** outputs combine these  
Output can be
  - **HIGH**,



# Types of logic gate outputs

- Totem pole  
Output is **HIGH** or **LOW**.
- Open collector  
Output is **floating** or **LOW**.
- **Tri-state** outputs combine these  
Output can be
  - **HIGH**,
  - **LOW**, or

# Types of logic gate outputs

- Totem pole  
Output is **HIGH** or **LOW**.
- Open collector  
Output is **floating** or **LOW**.
- **Tri-state** outputs combine these  
Output can be
  - **HIGH**,
  - **LOW**, or
  - **floating**

# Types of logic gate outputs

- Totem pole  
Output is **HIGH** or **LOW**.
- Open collector  
Output is **floating** or **LOW**.
- **Tri-state** outputs combine these  
Output can be
  - **HIGH**,
  - **LOW**, or
  - **floating**
- This requires two inputs;


# Types of logic gate outputs

- Totem pole  
Output is **HIGH** or **LOW**.
- Open collector  
Output is **floating** or **LOW**.
- **Tri-state** outputs combine these  
Output can be
  - **HIGH**,
  - **LOW**, or
  - **floating**
- This requires two inputs;  
**input** and


# Types of logic gate outputs

- Totem pole  
Output is **HIGH** or **LOW**.
- Open collector  
Output is **floating** or **LOW**.
- **Tri-state** outputs combine these  
Output can be
  - **HIGH**,
  - **LOW**, or
  - **floating**
- This requires two inputs;  
**input** and  
**select**.

# Tri-state outputs

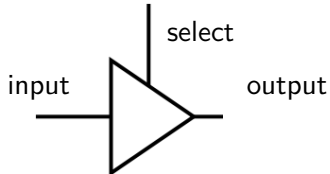


# Tri-state outputs

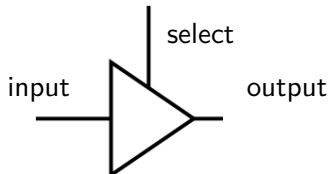

- **input** is to make output LOW or HIGH,


# Tri-state outputs

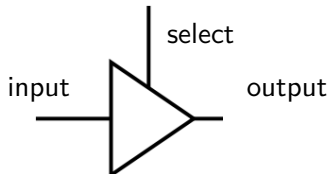


- **input** is to make output LOW or HIGH,
- **select** is to make output float or follow input




# Tri-state output equivalent circuit

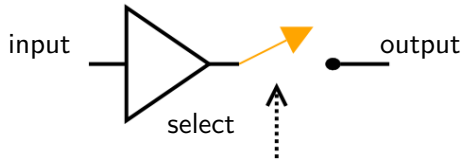


# Tri-state output equivalent circuit

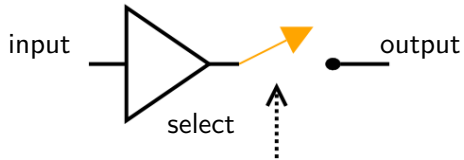


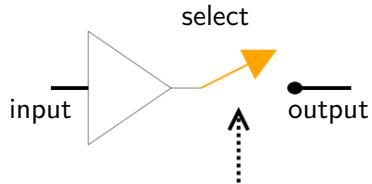- The **select** determines whether the output is floating or not.




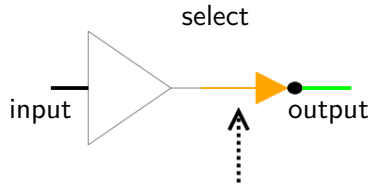

## Tri-state output (inverting)

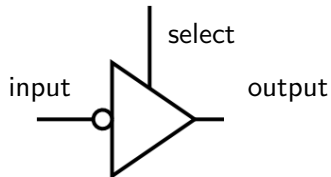


## Tri-state output (inverting)

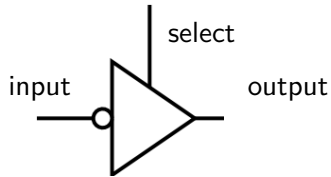


- Gates can be inverting, like other gates.

# Microprocessor buses

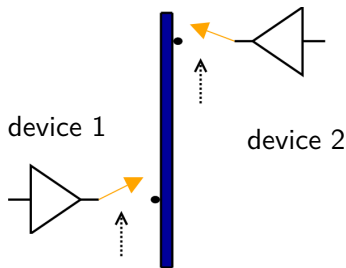

- A **bus** is created if several tristate devices are connected together.
- As long as only one is selected at a time, there is no problem.


# Microprocessor buses

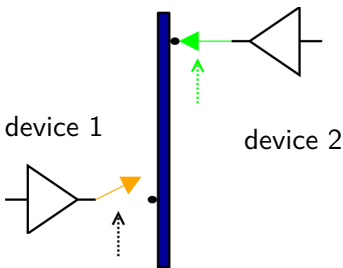

- A **bus** is created if several tristate devices are connected together.
- As long as only one is selected at a time, there is no problem.




# Microprocessor buses

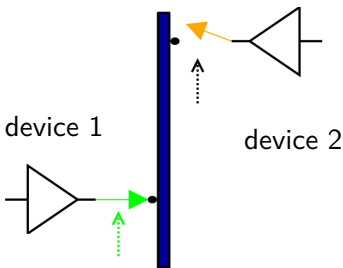


- A **bus** is created if several tristate devices are connected together.
- As long as only one is selected at a time, there is no problem.

# Microprocessor buses

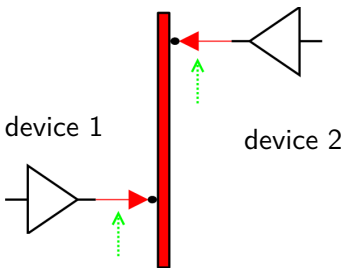


- A **bus** is created if several tristate devices are connected together.
- As long as only one is selected at a time, there is no problem.

## Tri-state (I/O) pins

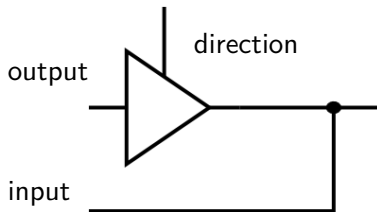


## Tri-state (I/O) pins

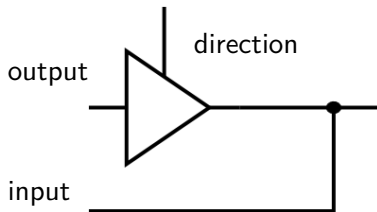


- Tri-state pins allow input and output on the same pin.

## Tri-state (I/O) pins

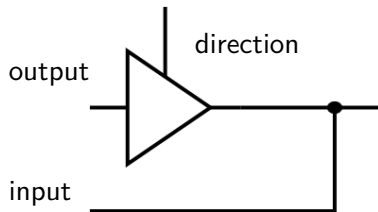


- Tri-state pins allow input and output on the same pin.
- The **direction** input indicates output or input (i.e. floating).

# Tri-state busses

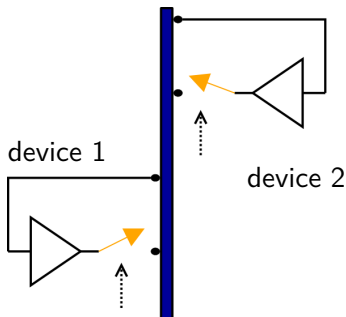


- Tri-state busses allow several devices to input and output on the same lines.
- Uses I/O signal and address decoding

# Tri-state busses

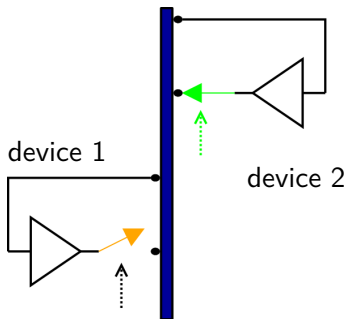

- Tri-state busses allow several devices to input and output on the same lines.
- Uses I/O signal and address decoding


# Tri-state busses

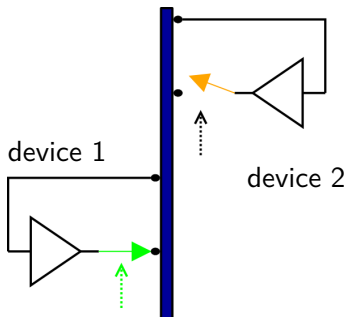

- Tri-state busses allow several devices to input and output on the same lines.
- Uses I/O signal and address decoding




# Tri-state busses

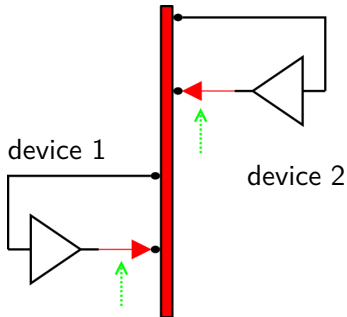

- Tri-state busses allow several devices to input and output on the same lines.
- Uses I/O signal and address decoding


## Internal view (CMOS)

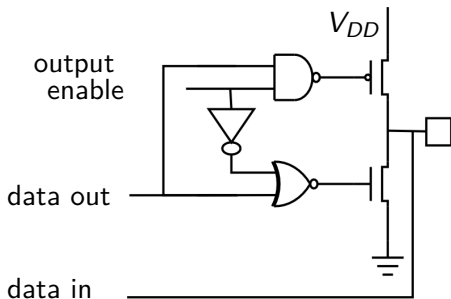

Here's what a CMOS tri-state output looks like inside.


(Note the top transistor is turned on by a low, but the bottom transistor is turned on by a high.)

# Internal view (CMOS)

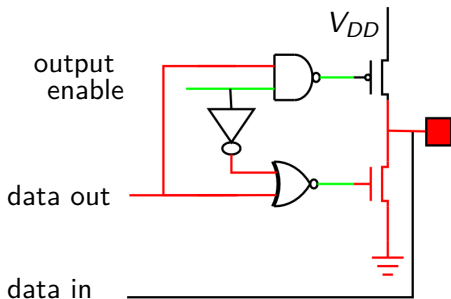


When output is enabled, and data out is low, the output will be low. (Only bottom transistor on.)

# Internal view (CMOS)

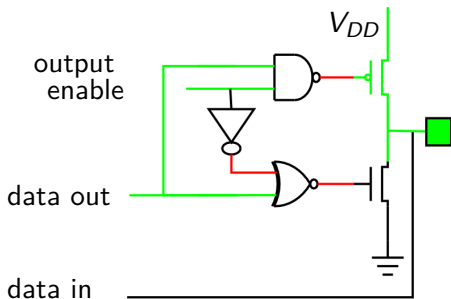

When output is enabled, and data out is high, the output will be high. (Only top transistor on.)

# Internal view (CMOS)

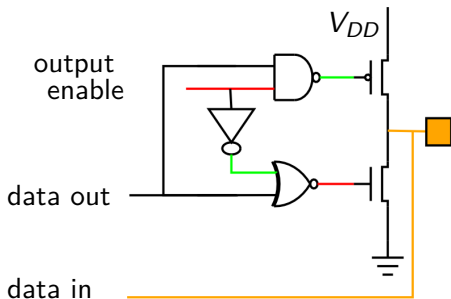

When output is not enabled,  
the output will float (to become an input). (Both transistors off.)