

Electronics

Sketching Op Amp Circuit Inputs and Outputs

Terry Sturtevant

Wilfrid Laurier University

September 17, 2013

- 1 Sketch V_{in} . (Show a couple of cycles.)

- 1 Sketch V_{in} . (Show a couple of cycles.)
- 2 Sketch output lightly with correct sign, based on sign of gain.

- 1 Sketch V_{in} . (Show a couple of cycles.)
- 2 Sketch output lightly with correct sign, based on sign of gain.
- 3 Scale vertical axis based on magnitude of gain.

- 1 Sketch V_{in} . (Show a couple of cycles.)
- 2 Sketch output lightly with correct sign, based on sign of gain.
- 3 Scale vertical axis based on magnitude of gain.
- 4 Clip signal (if necessary) based on rails.

Example:

Example:

- 5V, 1kHz sine wave is fed into an inverting amplifier.

Example:

- 5V, 1kHz sine wave is fed into an inverting amplifier.

$$R_f = 8k\Omega,$$

Example:

- 5V, 1kHz sine wave is fed into an inverting amplifier.

$$R_f = 8k\Omega,$$

$$R_i = 2k\Omega,$$

Example:

- 5V, 1kHz sine wave is fed into an inverting amplifier.

$$R_f = 8k\Omega,$$

$$R_i = 2k\Omega,$$

Positive supply is at 10V,

Example:

- 5V, 1kHz sine wave is fed into an inverting amplifier.

$$R_f = 8k\Omega,$$

$$R_i = 2k\Omega,$$

Positive supply is at 10V,

Negative supply is at $-5V$,

Example:

- 5V, 1kHz sine wave is fed into an inverting amplifier.

$$R_f = 8k\Omega,$$

$$R_i = 2k\Omega,$$

Positive supply is at 10V,

Negative supply is at $-5V$,

First: Determine gain:

First: Determine gain:

- For an inverting amplifier,

First: Determine gain:

- For an inverting amplifier,

$$V_o/V_i = -R_f/R_i$$

First: Determine gain:

- For an inverting amplifier,

$$V_o/V_i = -R_f/R_i$$

- So, for our circuit,

First: Determine gain:

- For an inverting amplifier,

$$V_o/V_i = -R_f/R_i$$

- So, for our circuit,

$$V_o/V_i = -8k\Omega/2k\Omega$$

First: Determine gain:

- For an inverting amplifier,

$$V_o/V_i = -R_f/R_i$$

- So, for our circuit,

$$V_o/V_i = -8k\Omega/2k\Omega$$

$$= -4$$

First: Determine gain:

- For an inverting amplifier,


$$V_o/V_i = -R_f/R_i$$

- So, for our circuit,


$$V_o/V_i = -8k\Omega/2k\Omega$$

$$= -4$$


- The gain is -4 .

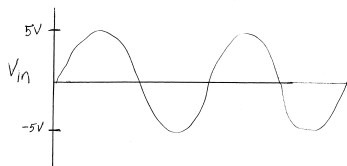


Sketch V_{in} .

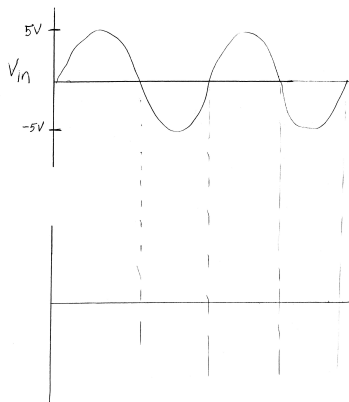

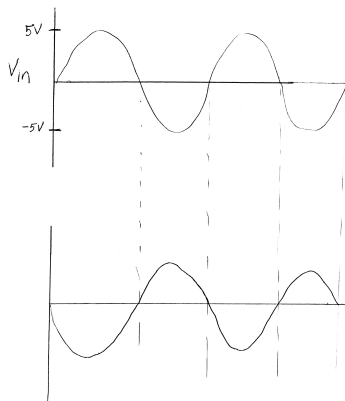
Create axes for V_{out} . (Use critical points for alignment.)



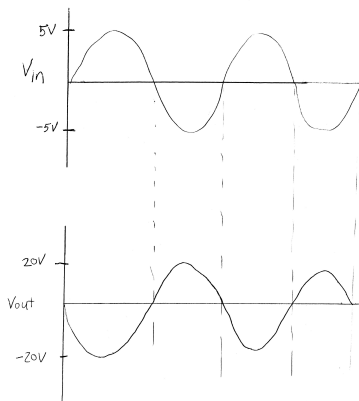
Sketch shape of V_{out} with *sign* of the gain. (inverted in this case.)



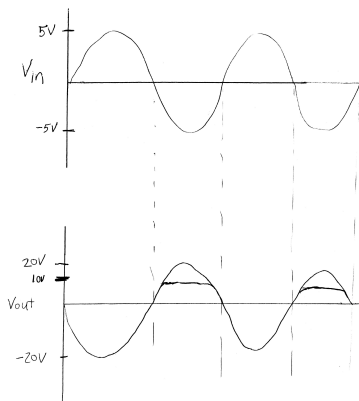
Use *magnitude* of gain to make scale for V_{out} . (magnitude of 4.)



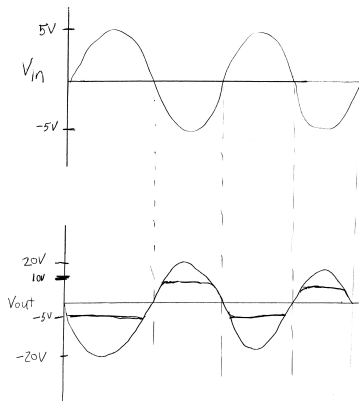Adjust top of waveform for *positive* rail. (+10V)



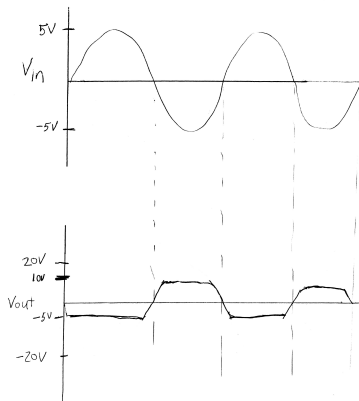Adjust bottom of waveform for *negative* rail. (-5V)



Clean up by removing obsolete lines.

Review

Review

- 1 Sketch V_{in} . (Show a couple of cycles.)

Review

- 1 Sketch V_{in} . (Show a couple of cycles.)
- 2 Sketch output lightly with correct sign, based on sign of gain.

Review

- 1 Sketch V_{in} . (Show a couple of cycles.)
- 2 Sketch output lightly with correct sign, based on sign of gain.
- 3 Scale vertical axis based on magnitude of gain.

Review

- 1 Sketch V_{in} . (Show a couple of cycles.)
- 2 Sketch output lightly with correct sign, based on sign of gain.
- 3 Scale vertical axis based on magnitude of gain.
- 4 Clip signal (if necessary) based on rails.