

Electronics Voltage Dividers

Terry Sturtevant


Wilfrid Laurier University


May 31, 2017

Applications of Kirchhoff's Voltage Law


Applications of Kirchhoff's Voltage Law

Voltage dividers

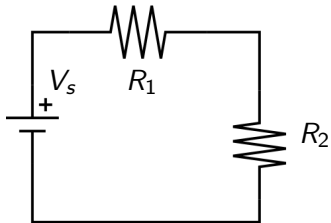


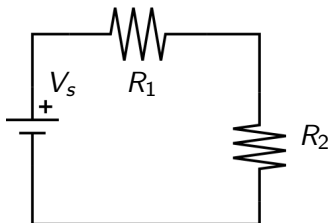


$$V_s = V_{R_1} + V_{R_2}$$

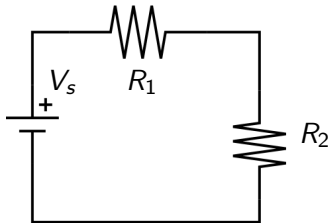

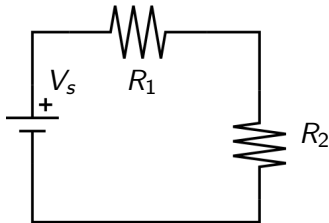
- A **voltage divider** “divides” the supply voltage



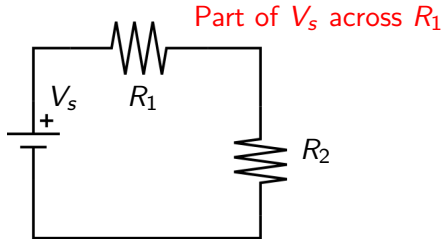- A **voltage divider** “divides” the supply voltage
- It’s useful when you need a different voltage than the supply



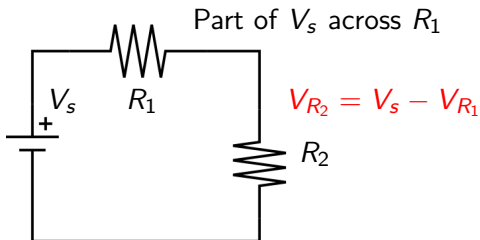- A **voltage divider** “divides” the supply voltage
- It’s useful when you need a different voltage than the supply



- A **voltage divider** “divides” the supply voltage
- It’s useful when you need a different voltage than the supply


Since the current is the same in both resistors, the voltage is *divided* between the two; thus it is a **voltage divider**.


Since the current is the same in both resistors, the voltage is *divided* between the two; thus it is a **voltage divider**.

Voltage divider circuits are very common, even when one or both circuit elements aren't resistors.


Since the current is the same in both resistors, the voltage is *divided* between the two; thus it is a **voltage divider**.

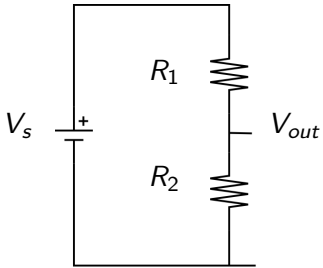Voltage divider circuits are very common, even when one or both circuit elements aren't resistors.



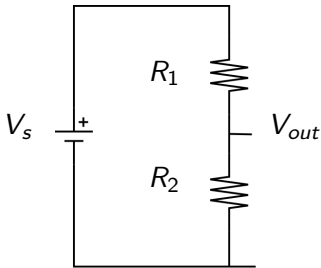


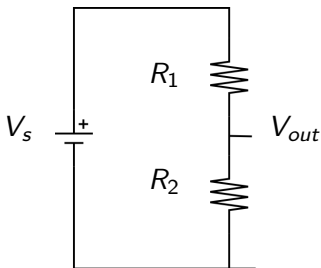Usually a voltage divider is drawn like this so it looks like a ladder.




Usually a voltage divider is drawn like this so it looks like a ladder.

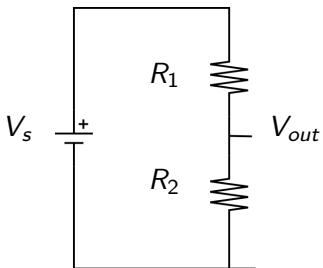
As you climb the ladder, the voltage increases.




Since $I_1 = I_2$,

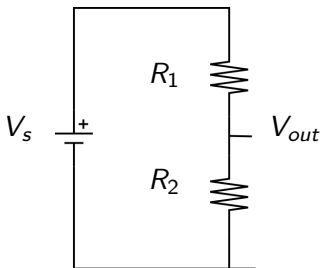

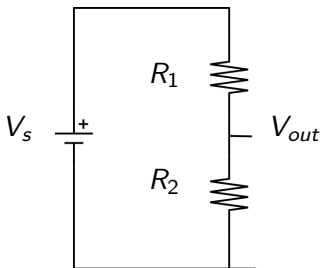
Since $I_1 = I_2$, (by Kirchhoff's current law,)



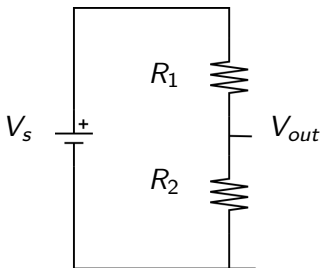
Since $I_1 = I_2$, (by Kirchhoff's current law),
and $V_s = V_{R_1} + V_{R_2}$,



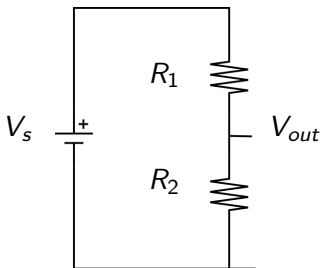
Since $I_1 = I_2$, (by Kirchhoff's current law),
and $V_s = V_{R_1} + V_{R_2}$, (by Kirchhoff's voltage law),



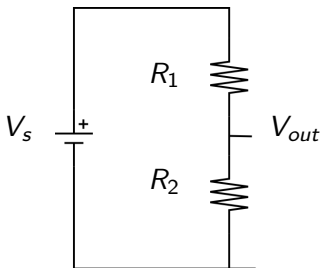
Since $I_1 = I_2$, (by Kirchhoff's current law),
and $V_s = V_{R_1} + V_{R_2}$, (by Kirchhoff's voltage law),
so $V_s = I_1 R_1 + I_1 R_2$



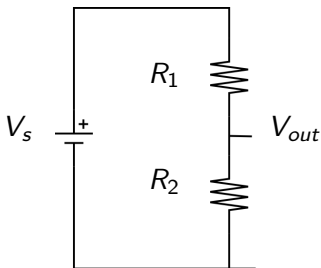
Since $I_1 = I_2$, (by Kirchhoff's current law),
and $V_s = V_{R_1} + V_{R_2}$, (by Kirchhoff's voltage law),
so $V_s = I_1 R_1 + I_1 R_2 = I(R_1 + R_2)$



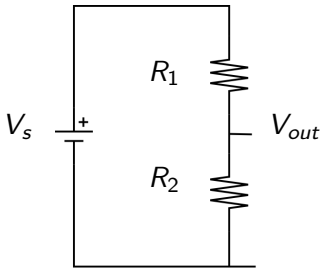
Since $I_1 = I_2$, (by Kirchhoff's current law),
and $V_s = V_{R_1} + V_{R_2}$, (by Kirchhoff's voltage law),
so $V_s = I_1 R_1 + I_1 R_2 = I(R_1 + R_2)$
$$I = \frac{V_s}{R_1 + R_2}$$




$$\text{So } V_{out} = V_2 = IR_2$$

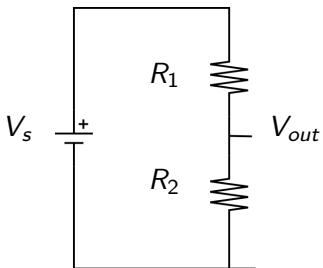
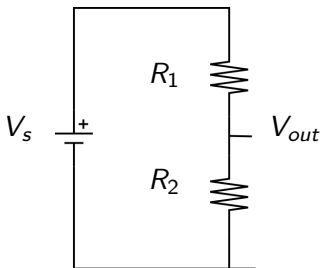
$$\text{So } V_{out} = V_2 = IR_2 = \frac{V_s}{R_1 + R_2} R_2$$



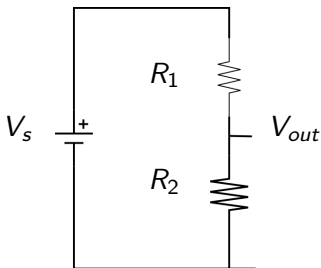
$$\begin{aligned} \text{So } V_{out} &= V_2 = IR_2 = \frac{V_s}{R_1 + R_2} R_2 \\ &= V_s \left(\frac{R_2}{R_1 + R_2} \right) \end{aligned}$$




If R_1 gets *smaller*, then

$$V_{out} = V_s \left(\frac{R_2}{R_1 + R_2} \right)$$

gets *bigger*.

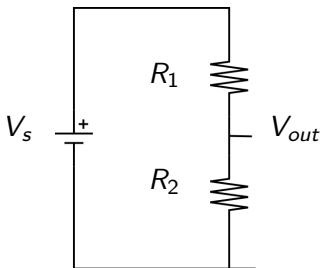
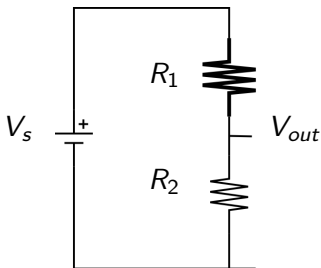
$$V_{out} = V_s \left(\frac{R_2}{R_1 + R_2} \right)$$



If R_1 gets *bigger*, then

$$V_{out} = V_s \left(\frac{R_2}{R_1 + R_2} \right)$$

gets *smaller*.

Voltage divider (no load)

Voltage divider (no load)

If $R_1 = 5\Omega$, $R_2 = 10\Omega$, $V_s = 5V$

Voltage divider (no load)

If $R_1 = 5\Omega$, $R_2 = 10\Omega$, $V_s = 5V$

V_{out}

Voltage divider (no load)

If $R_1 = 5\Omega$, $R_2 = 10\Omega$, $V_s = 5V$


$$V_{out} = V_s \left(\frac{R_2}{R_1 + R_2} \right) = 5 \left(\frac{10}{5 + 10} \right)$$

Voltage divider (no load)

If $R_1 = 5\Omega$, $R_2 = 10\Omega$, $V_s = 5V$


$$\begin{aligned} V_{out} &= V_s \left(\frac{R_2}{R_1 + R_2} \right) = 5 \left(\frac{10}{5 + 10} \right) \\ &= 3.3V \end{aligned}$$

Voltage divider (with load R_L)

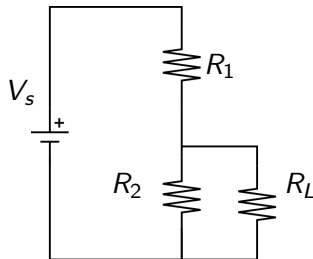


Load will reduce the output voltage

Voltage divider (with load R_L)

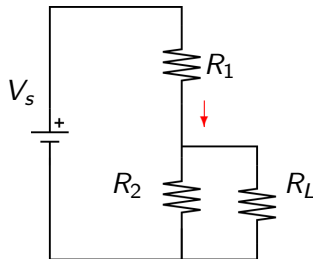

Voltage divider (with load R_L)

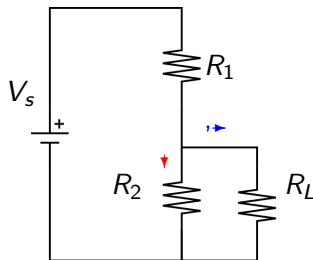

Some current goes through R_2 , but some goes through R_L so the *effective* value of R_2 is reduced.

If $R_1 = 5\Omega$, $R_2 = 10\Omega$, $V_s = 5V$ and $R_L = 10\Omega$

If $R_1 = 5\Omega$, $R_2 = 10\Omega$, $V_s = 5V$ and $R_L = 10\Omega$

Parallel resistance of R_2 and $R_L = \frac{R_2 R_L}{R_2 + R_L}$

If $R_1 = 5\Omega$, $R_2 = 10\Omega$, $V_s = 5V$ and $R_L = 10\Omega$

Parallel resistance of R_2 and $R_L = \frac{R_2 R_L}{R_2 + R_L}$

$$= \frac{10 \times 10}{10 + 10} = 5\Omega$$

If $R_1 = 5\Omega$, $R_2 = 10\Omega$, $V_s = 5V$ and $R_L = 10\Omega$

Parallel resistance of R_2 and $R_L = \frac{R_2 R_L}{R_2 + R_L}$

$$= \frac{10 \times 10}{10 + 10} = 5\Omega$$

Thus V_{out}

If $R_1 = 5\Omega$, $R_2 = 10\Omega$, $V_s = 5V$ and $R_L = 10\Omega$

Parallel resistance of R_2 and $R_L = \frac{R_2 R_L}{R_2 + R_L}$

$$= \frac{10 \times 10}{10 + 10} = 5\Omega$$

Thus V_{out}

$$= V_s \frac{R_p}{R_1 + R_p} = 5 \left(\frac{5}{5 + 5} \right)$$

If $R_1 = 5\Omega$, $R_2 = 10\Omega$, $V_s = 5V$ and $R_L = 10\Omega$

Parallel resistance of R_2 and $R_L = \frac{R_2 R_L}{R_2 + R_L}$

$$= \frac{10 \times 10}{10 + 10} = 5\Omega$$

Thus V_{out}

$$= V_s \frac{R_p}{R_1 + R_p} = 5 \left(\frac{5}{5 + 5} \right)$$

$$= 2.5V$$


Variable resistors


Variable resistors


Often it is useful to have *variable* resistors in a circuit.

Variable resistors

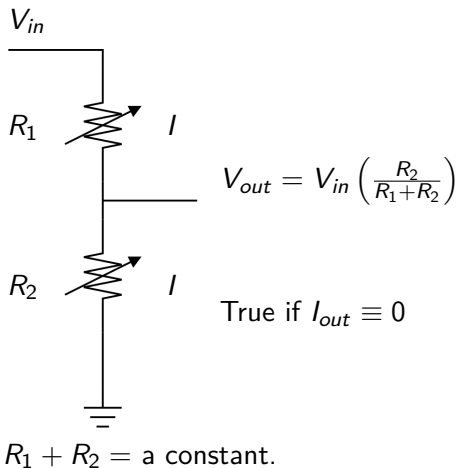Often it is useful to have *variable* resistors in a circuit.
These are sometimes called **potentiometers** or **trimmers**.



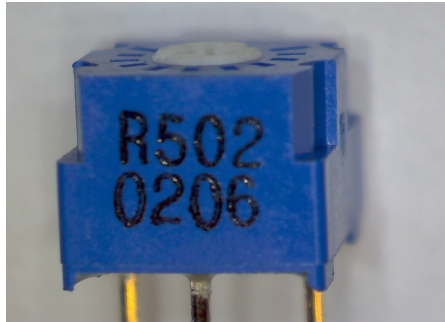

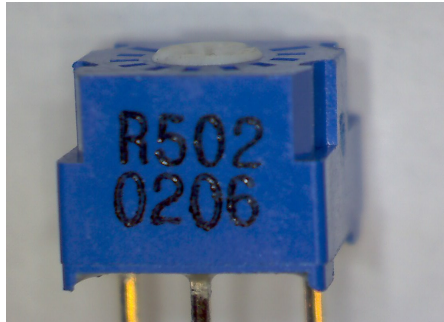

Here is a trimmer.



Here is a trimmer. The top line should look familiar.

The potentiometer has three pins.

The potentiometer has three pins.

The resistance given is between the two end pins.

The potentiometer has three pins.
The resistance given is between the two end pins.
The third pin is called the **wiper**.

The potentiometer has three pins.

The resistance given is between the two end pins.

The third pin is called the **wiper**.

A small screwdriver can be used to move the wiper from one end to the other, or anywhere in between.

The potentiometer has three pins.

The resistance given is between the two end pins.

The third pin is called the **wiper**.

A small screwdriver can be used to move the wiper from one end to the other, or anywhere in between.

The resistance between the two end pins will be constant.

The potentiometer has three pins.


The resistance given is between the two end pins.


The third pin is called the **wiper**.

A small screwdriver can be used to move the wiper from one end to the other, or anywhere in between.


The resistance between the two end pins will be constant.

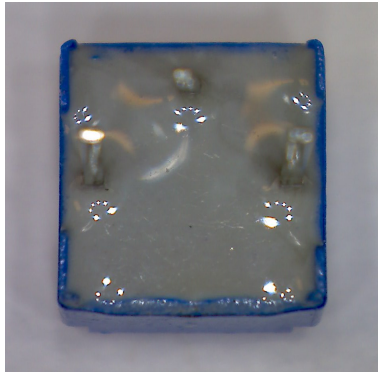If you want a resistance which varies, just use the wiper and one end pin.




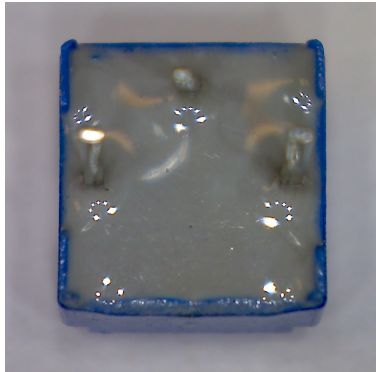


Here's a different view.

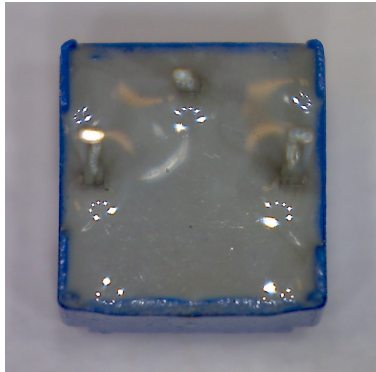


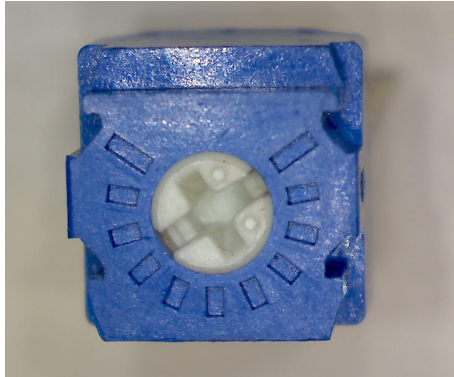
Here's a different view. The wiper is in the middle.



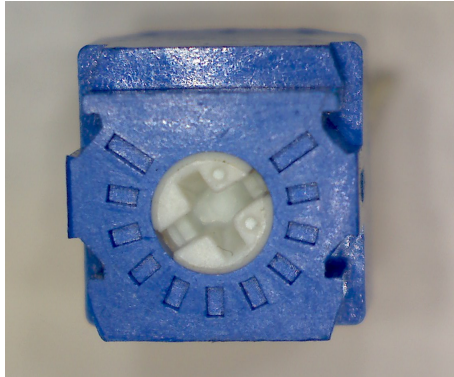


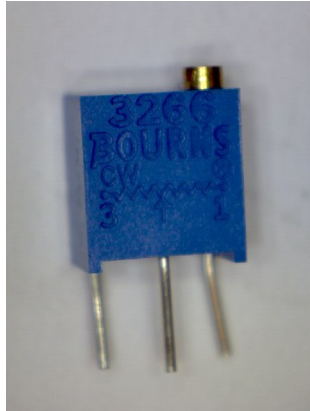From the top, this one has 10 dashes to represent intervals of roughly $R/10$.



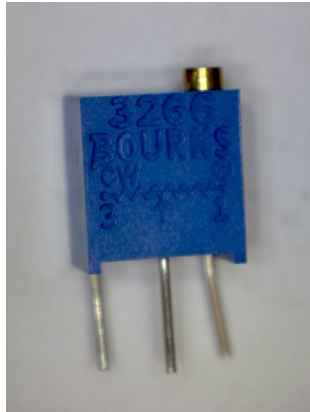

This is a slightly different style.

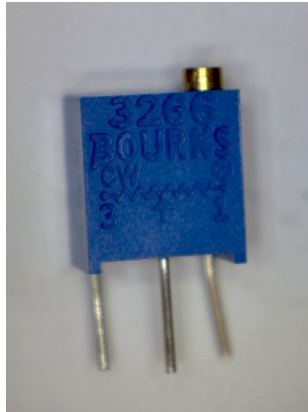

This is a slightly different style. Note the graphical indication of the wiper.

The potentiometer can be used for a variable voltage divider.

The potentiometer can be used for a variable voltage divider.
Connect the two ends of your supply to the two end pins.

The potentiometer can be used for a variable voltage divider.
Connect the two ends of your supply to the two end pins.
Measure the output voltage on the wiper.

The potentiometer can be used for a variable voltage divider.
Connect the two ends of your supply to the two end pins.
Measure the output voltage on the wiper.
Adjusting the wiper will change the output voltage from one end of the supply to the other, or to anywhere in between.

Switches in voltage dividers

Switches in voltage dividers


- One of the simplest forms of voltage divider is where one of the elements is a *switch*.

Switches in voltage dividers

- One of the simplest forms of voltage divider is where one of the elements is a *switch*.
- A switch can be thought of as a resistor which can have a value of either zero or infinity.


Switches in voltage dividers

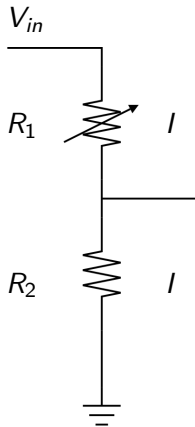- One of the simplest forms of voltage divider is where one of the elements is a *switch*.
- A switch can be thought of as a resistor which can have a value of either zero or infinity.
- Following is an illustration of a voltage divider where one element is a switch.




$$V_{out} = V_{in} \left(\frac{R_2}{R_1 + R_2} \right)$$


True if $I_{out} \equiv 0$

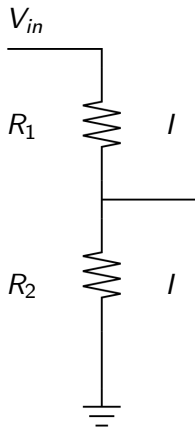



$$V_{out} = V_{in} \left(\frac{R_2}{R_1 + R_2} \right)$$

True if $I_{out} \equiv 0$

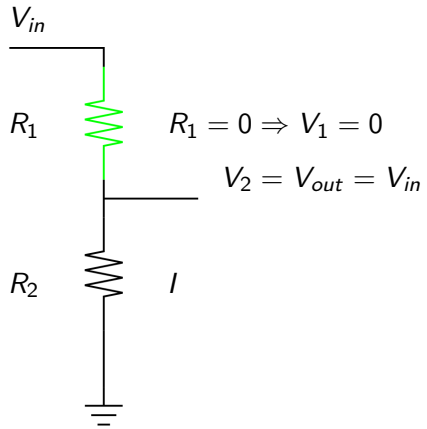

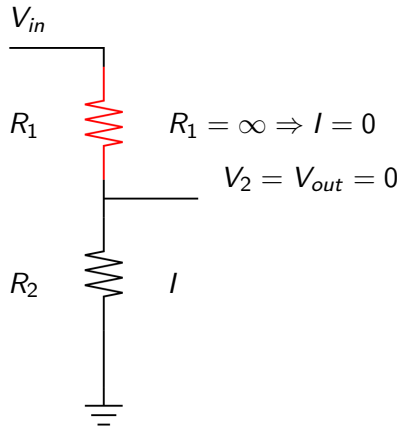

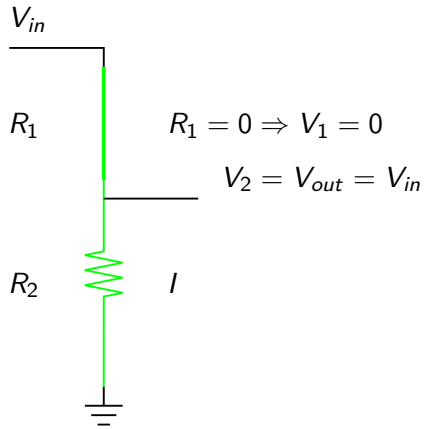


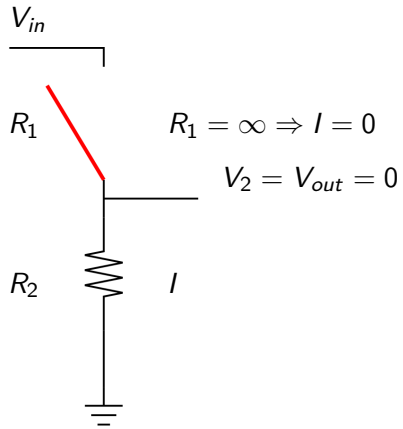

- So if one of the elements is a *switch*, the output varies between 0 and V_{in} .

- So if one of the elements is a *switch*, the output varies between 0 and V_{in} .
- If either resistor in a voltage divider is *variable*, then a range of output voltages is possible.

Resistive sensors in voltage dividers

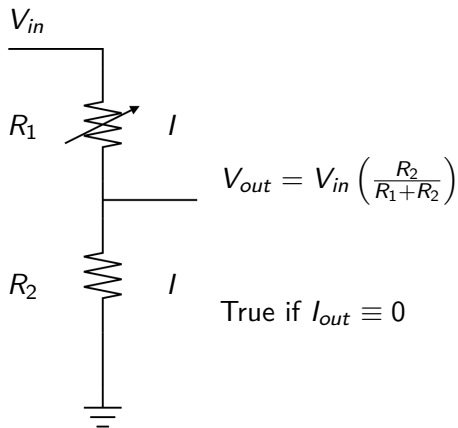

- If we want to put a variable resistor in a voltage divider, then we need to *choose* the other resistor.

- If we want to put a variable resistor in a voltage divider, then we need to *choose* the other resistor.
- To make the output vary *over as large a range as possible* as the variable resistor goes from R_{min} to R_{max} , it turns out we want to choose the other resistor, R so that

- If we want to put a variable resistor in a voltage divider, then we need to *choose* the other resistor.
- To make the output vary *over as large a range as possible* as the variable resistor goes from R_{min} to R_{max} , it turns out we want to choose the other resistor, R so that

$$R = \sqrt{R_{min} \times R_{max}}$$