

Electronics

Wheatstone Bridge Circuits

Terry Sturtevant

Wilfrid Laurier University

October 18, 2016

Wheatstone bridges

Wheatstone bridges


- A common type of circuit is a **Wheatstone bridge**.


Wheatstone bridges


- A common type of circuit is a **Wheatstone bridge**.
- It is really a pair of voltage dividers using a common voltage source.


Wheatstone bridges

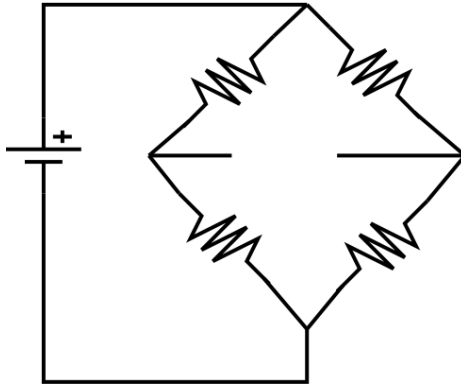
- A common type of circuit is a **Wheatstone bridge**.
- It is really a pair of voltage dividers using a common voltage source.
- It's usually operated with the output voltage at or close to zero.



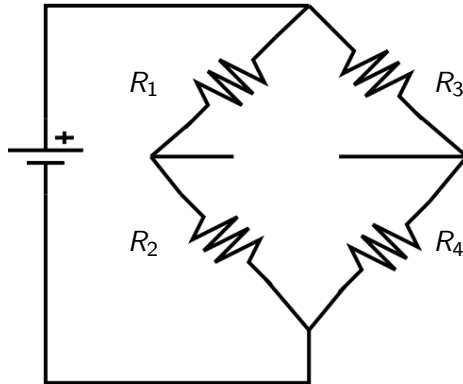


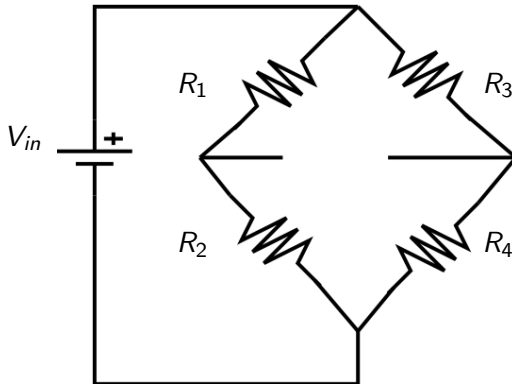

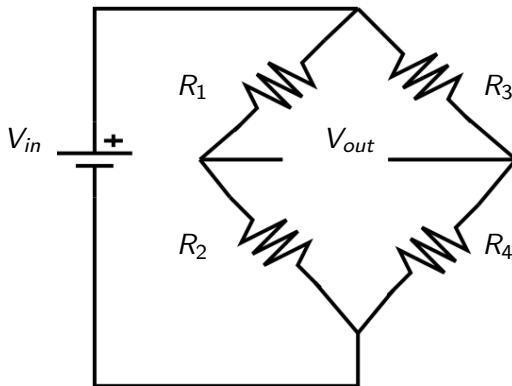


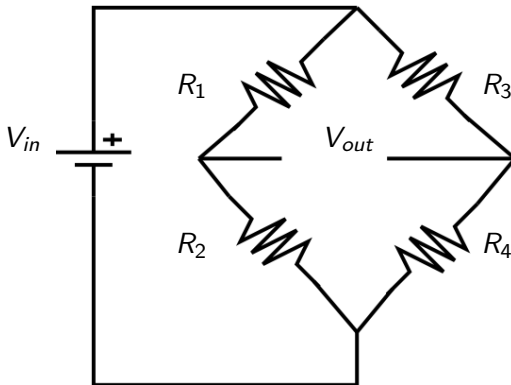


This is a Wheatstone bridge.

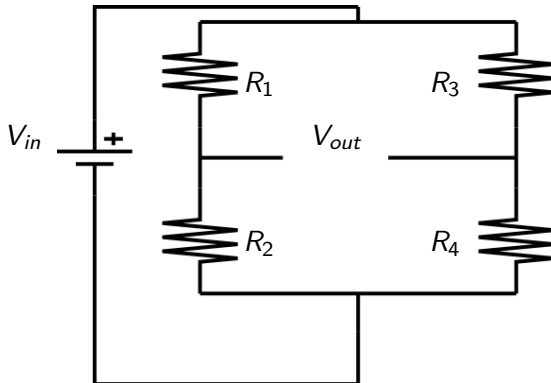

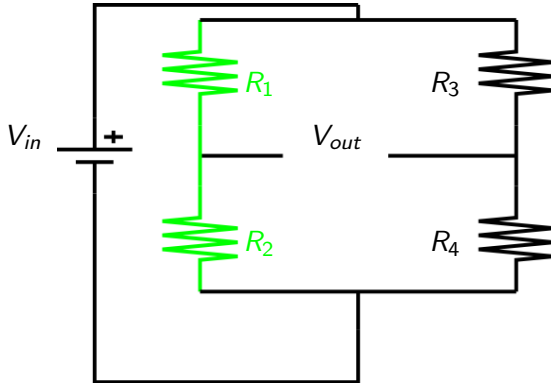Here it's redrawn to show the two voltage dividers.



Here's one voltage divider.

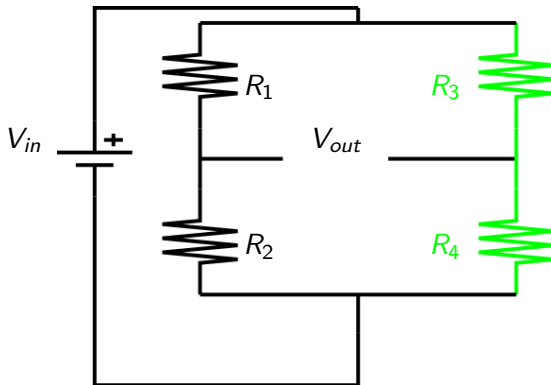


Here's the other voltage divider.

- Often a Wheatstone bridge is used with one resistor variable, such as a resistive sensor.

- Often a Wheatstone bridge is used with one resistor variable, such as a resistive sensor.
- Knowing the other resistors allows the variable one to be easily determined.

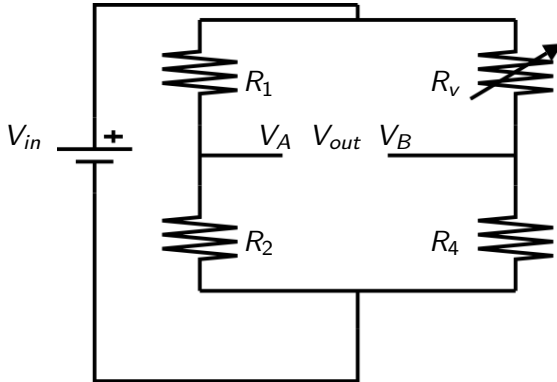- Often a Wheatstone bridge is used with one resistor variable, such as a resistive sensor.
- Knowing the other resistors allows the variable one to be easily determined.
- The circuit is very sensitive to small changes in the variable resistor.



The variable resistor could be in any of the four positions; this is one example.

Balancing a Wheatstone Bridge

Balancing a Wheatstone Bridge

- When the bridge is “balanced”, $V_o = 0$ or $V_A = V_B$.

Balancing a Wheatstone Bridge

- When the bridge is “balanced”, $V_o = 0$ or $V_A = V_B$.
- (This will happen when $\frac{R_1}{R_2} = \frac{R_3}{R_4}$.)

Balancing a Wheatstone Bridge

- When the bridge is “balanced”, $V_o = 0$ or $V_A = V_B$.
- (This will happen when $\frac{R_1}{R_2} = \frac{R_v}{R_4}$.)
- For our diagram $R_1 \rightarrow R_2$ is the *reference* branch, and $R_v \rightarrow R_4$ is the *evaluation* branch.

Balancing a Wheatstone Bridge


- When the bridge is “balanced”, $V_o = 0$ or $V_A = V_B$.
- (This will happen when $\frac{R_1}{R_2} = \frac{R_V}{R_4}$.)
- For our diagram $R_1 \rightarrow R_2$ is the *reference* branch, and $R_V \rightarrow R_4$ is the *evaluation* branch.
- If R_V increases, V_B will decrease, and vice versa.

Balancing a Wheatstone Bridge

- When the bridge is “balanced”, $V_o = 0$ or $V_A = V_B$.
- (This will happen when $\frac{R_1}{R_2} = \frac{R_V}{R_4}$.)
- For our diagram $R_1 \rightarrow R_2$ is the *reference* branch, and $R_V \rightarrow R_4$ is the *evaluation* branch.
- If R_V increases, V_B will decrease, and vice versa.
- For optimum performance, all resistors should be of the same order of magnitude.

Balancing a Wheatstone Bridge

- When the bridge is “balanced”, $V_o = 0$ or $V_A = V_B$.
- (This will happen when $\frac{R_1}{R_2} = \frac{R_V}{R_4}$.)
- For our diagram $R_1 \rightarrow R_2$ is the *reference* branch, and $R_V \rightarrow R_4$ is the *evaluation* branch.
- If R_V increases, V_B will decrease, and vice versa.
- For optimum performance, all resistors should be of the same order of magnitude.
- If using a resistive sensor, use a meter to measure resistance of sensor to get a correct order of magnitude.

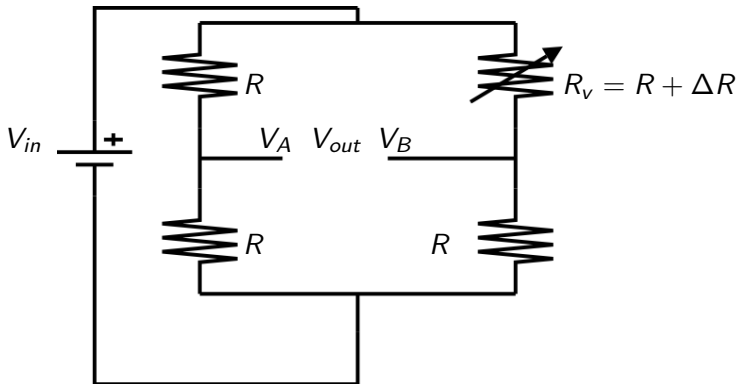

If resistors are chosen to be equal, except for R_v , then the output voltage will vary with changes in R_v .

Specifically,

Specifically,

$$V_A = V \frac{R}{2R} = V/2$$

Specifically,

$$V_A = V \frac{R}{2R} = V/2$$

$$V_B = V \frac{R}{2R+\Delta R} = V \frac{R+\Delta R/2-\Delta R/2}{2R+\Delta R} = V/2 - V \frac{\Delta R/2}{2R+\Delta R} \approx$$

$$V/2 - V \frac{\Delta R/2}{2R}$$

Specifically,

$$V_A = V \frac{R}{2R} = V/2$$

$$V_B = V \frac{R}{2R+\Delta R} = V \frac{R+\Delta R/2-\Delta R/2}{2R+\Delta R} = V/2 - V \frac{\Delta R/2}{2R+\Delta R} \approx$$
$$V/2 - V \frac{\Delta R/2}{2R}$$

If no current flows between A and B then

Specifically,

$$V_A = V \frac{R}{2R} = V/2$$

$$V_B = V \frac{R}{2R+\Delta R} = V \frac{R+\Delta R/2-\Delta R/2}{2R+\Delta R} = V/2 - V \frac{\Delta R/2}{2R+\Delta R} \approx$$
$$V/2 - V \frac{\Delta R/2}{2R}$$

If no current flows between A and B then

$$V_A - V_B \approx V \frac{\Delta R}{4R}$$

Specifically,

$$V_A = V \frac{R}{2R} = V/2$$

$$V_B = V \frac{R}{2R+\Delta R} = V \frac{R+\Delta R/2-\Delta R/2}{2R+\Delta R} = V/2 - V \frac{\Delta R/2}{2R+\Delta R} \approx V/2 - V \frac{\Delta R/2}{2R}$$

If no current flows between A and B then

$$V_A - V_B \approx V \frac{\Delta R}{4R}$$

which can be rearranged to give

Specifically,

$$V_A = V \frac{R}{2R} = V/2$$

$$V_B = V \frac{R}{2R + \Delta R} = V \frac{R + \Delta R/2 - \Delta R/2}{2R + \Delta R} = V/2 - V \frac{\Delta R/2}{2R + \Delta R} \approx V/2 - V \frac{\Delta R/2}{2R}$$

If no current flows between A and B then

$$V_A - V_B \approx V \frac{\Delta R}{4R}$$

which can be rearranged to give

$$\Delta R \approx \frac{(V_A - V_B)}{V} 4R$$

Specifically,

$$V_A = V \frac{R}{2R} = V/2$$

$$V_B = V \frac{R}{2R + \Delta R} = V \frac{R + \Delta R/2 - \Delta R/2}{2R + \Delta R} = V/2 - V \frac{\Delta R/2}{2R + \Delta R} \approx V/2 - V \frac{\Delta R/2}{2R}$$

If no current flows between A and B then

$$V_A - V_B \approx V \frac{\Delta R}{4R}$$

which can be rearranged to give

$$\Delta R \approx \frac{(V_A - V_B)}{V} 4R$$

So we can determine ΔR .

Specifically,

$$V_A = V \frac{R}{2R} = V/2$$

$$V_B = V \frac{R}{2R+\Delta R} = V \frac{R+\Delta R/2-\Delta R/2}{2R+\Delta R} = V/2 - V \frac{\Delta R/2}{2R+\Delta R} \approx V/2 - V \frac{\Delta R/2}{2R}$$

If no current flows between A and B then

$$V_A - V_B \approx V \frac{\Delta R}{4R}$$

which can be rearranged to give

$$\Delta R \approx \frac{(V_A - V_B)}{V} 4R$$

So we can determine ΔR .

(This approximation is true as long as $\Delta R \ll R$)

Wheatstone bridge options

- Lead wire compensation

Wheatstone bridge options

- Lead wire compensation
- Temperature compensation

Wheatstone bridge options


- Lead wire compensation
- Temperature compensation
- Instrumentation amplifiers

Wheatstone bridge options

- Lead wire compensation
- Temperature compensation
- Instrumentation amplifiers


differential op amp circuit with voltage followers on the inputs

Lead wire compensation

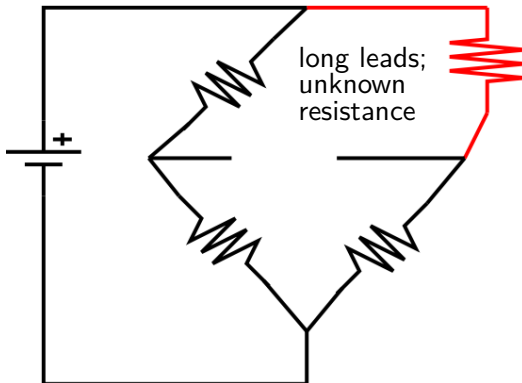

Uncompensated


Lead wire compensation

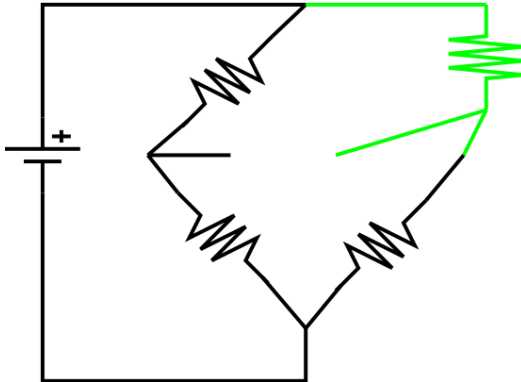


No current flows in measurement lead; similar resistance in both other leads

Temperature compensation


Temperature compensation

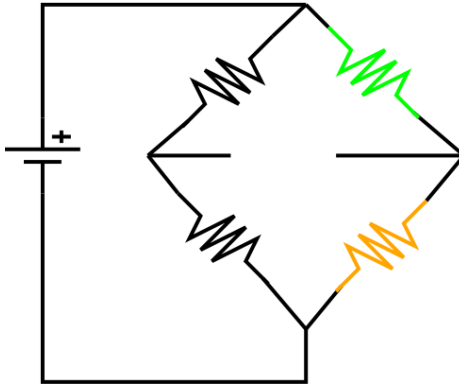


Temperature compensation

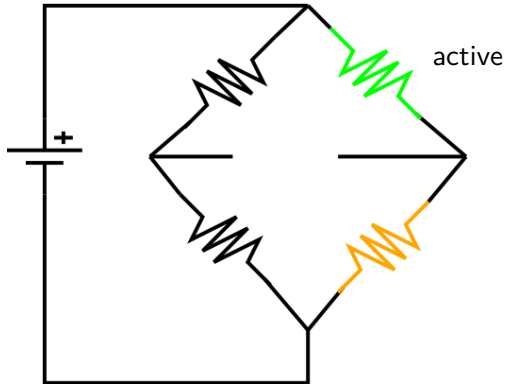

Temperature compensation

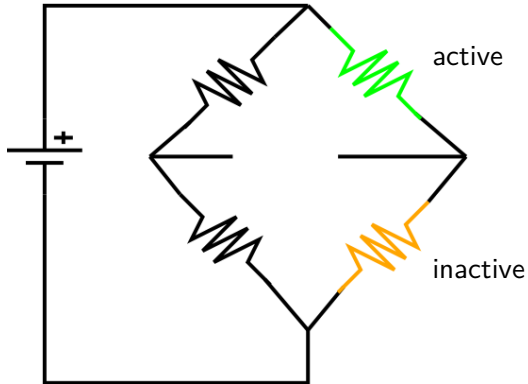


Temperature compensation

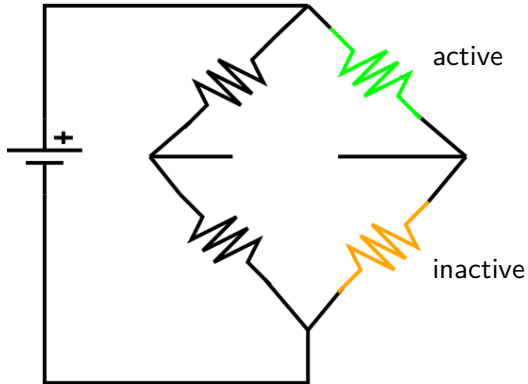


Temperature response of non-active sensor similar to active sensor

Doubling sensitivity

Doubling sensitivity

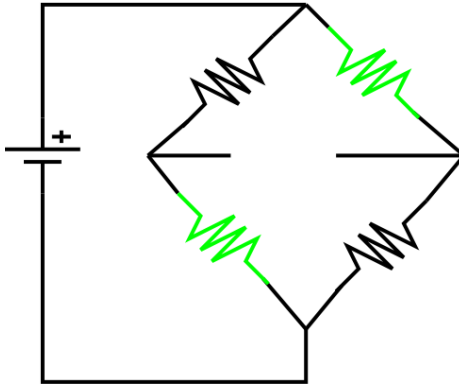

Doubling sensitivity

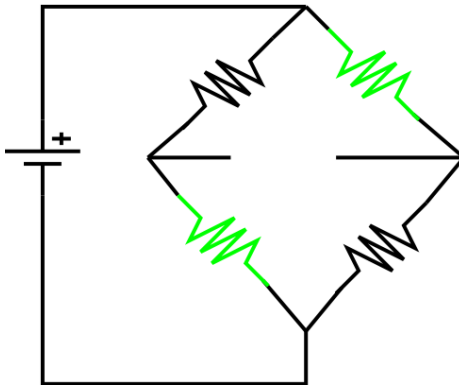

Sensors in diagonal positions produce opposite responses.

Wheatstone bridge current limit

- Put resistor in series with bridge

Wheatstone bridge current limit

- Put resistor in series with bridge
- Choose $R_s \gg R_t$


Wheatstone bridge current limit

- Put resistor in series with bridge
- Choose $R_s \gg R_t$


thus current controlled by R_s (fixed) rather than R_t (variable).

Reducing current

Reducing current

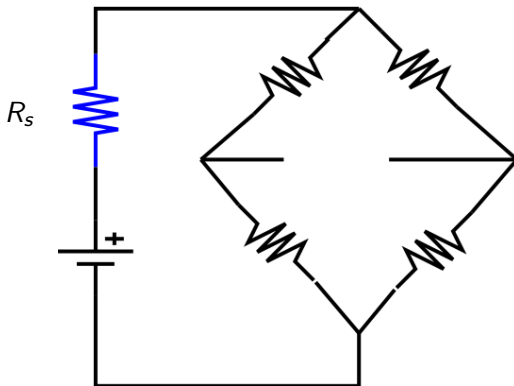

Reducing current

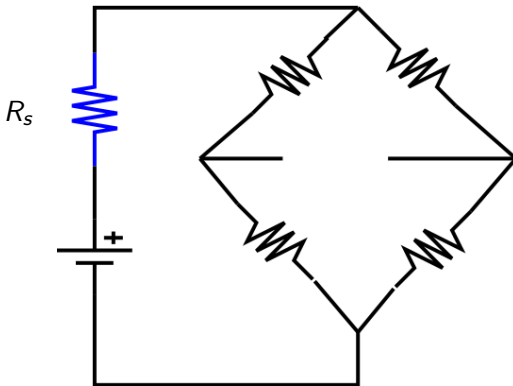

This is useful if the voltage supply is fixed.