

# Electronics Inductive Output Transducers

Terry Sturtevant

Wilfrid Laurier University

June 9, 2014

# Output transducers

# Output transducers

- also called “actuators”

# Output transducers

- also called “actuators”
- basically of two types

# Output transducers

- also called “actuators”
- basically of two types  
resistive

# Output transducers

- also called “actuators”
- basically of two types
  - resistive
  - inductive

# Output transducers

- also called “actuators”
- basically of two types
  - resistive
  - inductive
- inductive loads require a few special considerations

# Solenoid



# Solenoid

- consists of a coil and plunger

# Solenoid

- consists of a coil and plunger
- can be of either “push” or “pull” type


# Solenoid

- consists of a coil and plunger
- can be of either “push” or “pull” type  
“pull” type are much more common

# Solenoid


- consists of a coil and plunger
- can be of either “push” or “pull” type  
“pull” type are much more common

## Solenoid

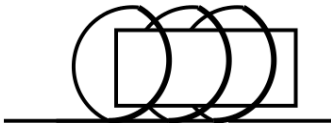

- plunger in

## Solenoid

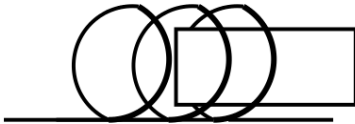

## Solenoid



- plunger out

# Induced EMF



# Induced EMF

- Quickly changing voltage across inductor produces *induced EMF*

# Induced EMF

- Quickly changing voltage across inductor produces *induced EMF*  
induced voltage tries to counteract change in current

# Induced EMF

- Quickly changing voltage across inductor produces *induced EMF*  
induced voltage tries to counteract change in current  
can produce big voltage spikes


# Induced EMF

- Quickly changing voltage across inductor produces *induced EMF*  
induced voltage tries to counteract change in current  
can produce big voltage spikes
- A diode across a coil will limit voltages to  $\approx 0.7V$ .

# Induced EMF


- Quickly changing voltage across inductor produces *induced EMF*  
induced voltage tries to counteract change in current  
can produce big voltage spikes
- A diode across a coil will limit voltages to  $\approx 0.7V$ .  
A zener diode can limit voltages the other way to about the zener voltage.

No diode to reduce induced EMF

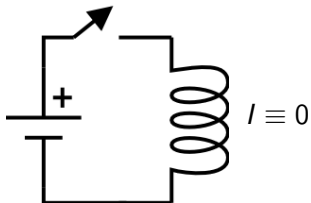


Initially  $I = 0$ .

No diode to reduce induced EMF

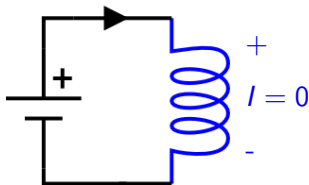

Induced voltage tries to maintain  $I = 0$ .


No diode to reduce induced EMF

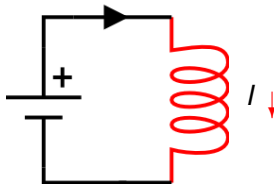

Eventually current is established determined by resistance in circuit.




No diode to reduce induced EMF

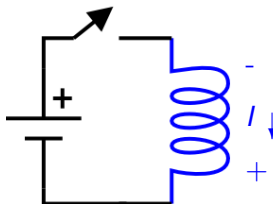


Induced voltage tries to maintain  $I$  at the previous value.

No diode to reduce induced EMF

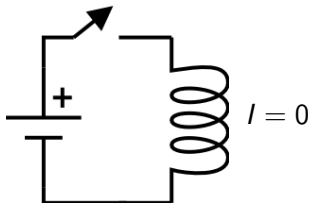


Eventually current is reduced to  $I = 0$ .

Diode to reduce induced EMF

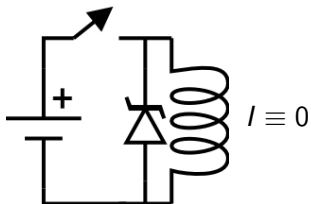


Initially  $I = 0$ .

Diode to reduce induced EMF

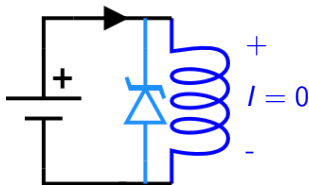


Induced voltage tries to maintain  $I = 0$ , *but cannot exceed  $V_Z$ .*

Diode to reduce induced EMF

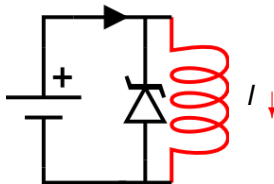


Eventually current is established determined by resistance in circuit.

Diode to reduce induced EMF

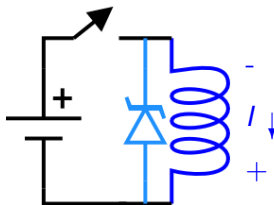

Induced voltage tries to maintain  $I$  but cannot exceed  $\approx 0.7V$ .

Diode to reduce induced EMF

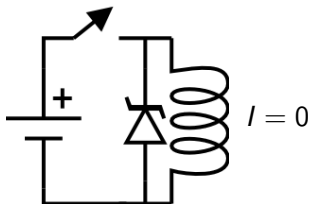

Eventually current is reduced to  $I = 0$ .

# Current requirements



# Current requirements

- A solenoid requires more current to move plunger than to hold it.

# Current requirements

- A solenoid requires more current to move plunger than to hold it.

Maintaining current larger than necessary wastes power and produces heat.

# Current requirements


- A solenoid requires more current to move plunger than to hold it.

Maintaining current larger than necessary wastes power and produces heat.


- Several options exist for adjusting current between moving the plunger and holding it.

## Series resistor


## Series resistor

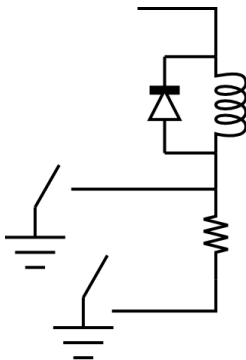


## Series resistor

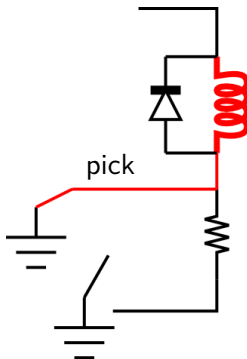

## Series resistor

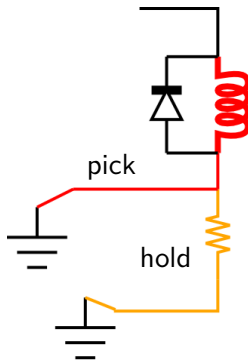


## Series resistor

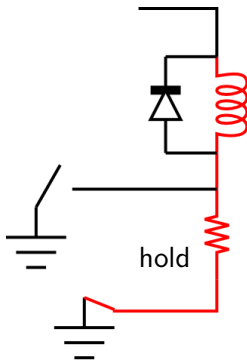




## Multiple supplies


## Multiple supplies

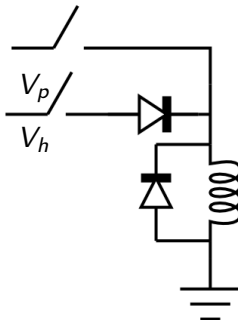


## Multiple supplies

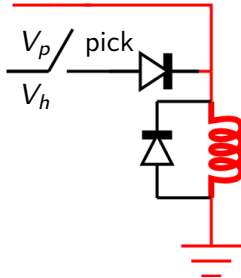


## Multiple supplies

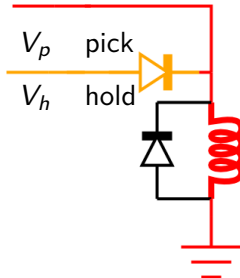

## Multiple supplies

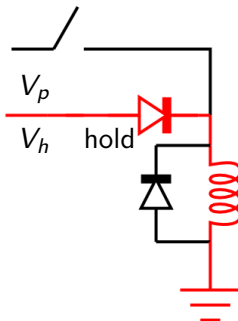


## Multiple supplies

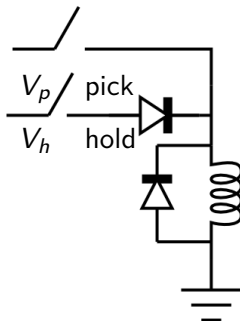

$$V_p > V_h$$
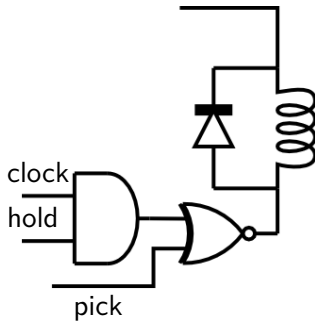
## Pulse width modulation to limit current



# Solenoids in action: Relays



# Solenoids in action: Relays

A relay is a device for switching, which is based on a solenoid.


## Solenoids in action: Relays

A relay is a device for switching, which is based on a solenoid.  
The solenoid is used to open and close a switch.


## Solenoids in action: Relays

A relay is a device for switching, which is based on a solenoid.  
The solenoid is used to open and close a switch.  
An internal spring returns the solenoid to its original position.

Relay **OFF**

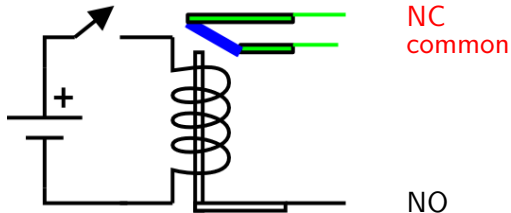

Relay **ON**

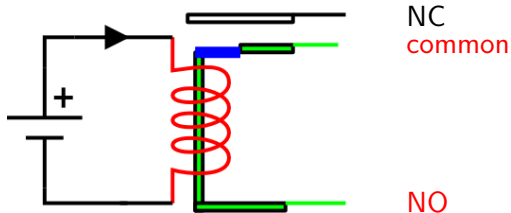

# DC motor types

# DC motor types

- Four main types of DC motors

# DC motor types

- Four main types of DC motors  
Permanent Magnet



# DC motor types

- Four main types of DC motors
  - Permanent Magnet
  - Brushless

# DC motor types

- Four main types of DC motors

Permanent Magnet

Brushless

Stepper

# DC motor types

- Four main types of DC motors

Permanent Magnet

Brushless

Stepper

Servo

# DC motor

# DC motor

- PMDC (Permanent Magnet DC)

# DC motor

- PMDC (Permanent Magnet DC)
- uses permanent fixed magnets

# DC motor

- PMDC (Permanent Magnet DC)
- uses permanent fixed magnets  
armature on shaft has electromagnet

# DC motor

- PMDC (Permanent Magnet DC)
- uses permanent fixed magnets  
armature on shaft has electromagnet  
commutator on shaft reverses current direction every half rotation




# DC motor

- PMDC (Permanent Magnet DC)
- uses permanent fixed magnets  
armature on shaft has electromagnet  
commutator on shaft reverses current direction every half rotation
- speed controlled by current


# DC motor

- PMDC (Permanent Magnet DC)
- uses permanent fixed magnets  
armature on shaft has electromagnet  
commutator on shaft reverses current direction every half rotation
- speed controlled by current
- continuous motion


## Permanent magnet DC motor

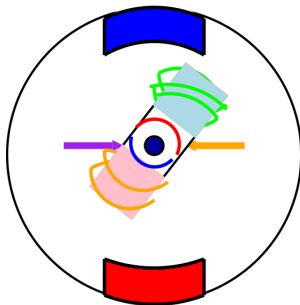


## Permanent magnet DC motor

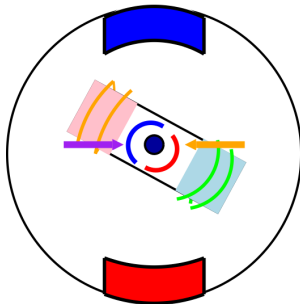


## Permanent magnet DC motor

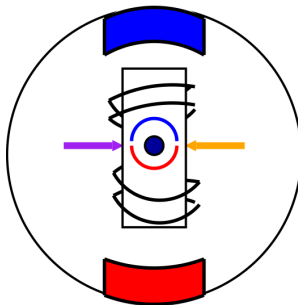


## Permanent magnet DC motor

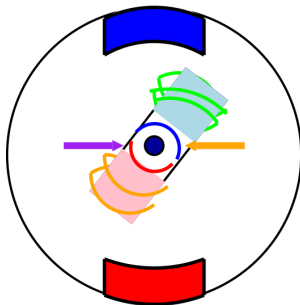

## Permanent magnet DC motor

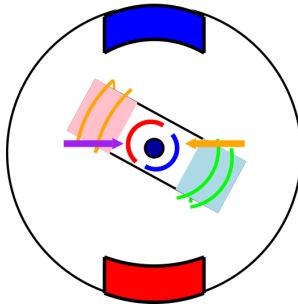

## Permanent magnet DC motor

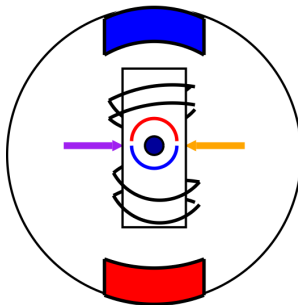



# Brushless DC motor

# Brushless DC motor

- uses fixed electromagnets

# Brushless DC motor

- uses fixed electromagnets  
armature on shaft has permanent magnets

# Brushless DC motor

- uses fixed electromagnets  
armature on shaft has permanent magnets
- continuous motion

# Brushless DC motor

- uses fixed electromagnets  
armature on shaft has permanent magnets
- continuous motion  
capable of holding one position


# Brushless DC motor

- uses fixed electromagnets  
armature on shaft has permanent magnets
- continuous motion  
capable of holding one position
- need to sense position

# Brushless DC motor


- uses fixed electromagnets  
armature on shaft has permanent magnets
- continuous motion  
capable of holding one position
- need to sense position  
can use a hall effect sensor or sense induced voltage in unused coils

## Brushless DC motor

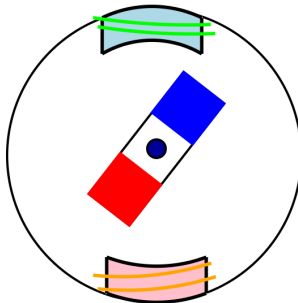





## Brushless DC motor

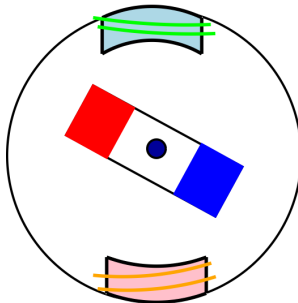


## Brushless DC motor

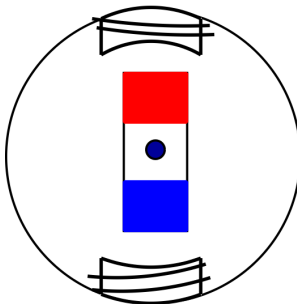


## Brushless DC motor

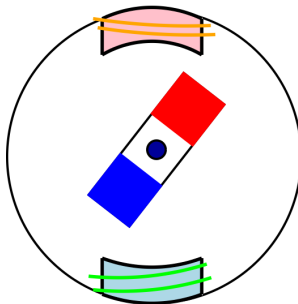

## Brushless DC motor

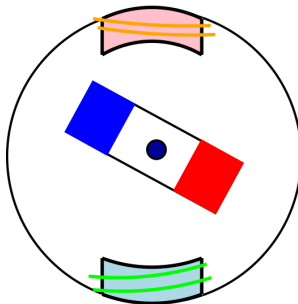

## Brushless DC motor

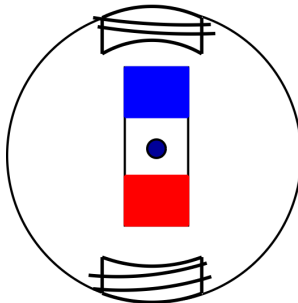

# Stepper motor

# Stepper motor

- uses fixed electromagnets

# Stepper motor

- uses fixed electromagnets  
armature on shaft has soft iron core



# Stepper motor

- uses fixed electromagnets  
armature on shaft has soft iron core  
i.e. no permanent magnets

# Stepper motor

- uses fixed electromagnets  
armature on shaft has soft iron core  
i.e. no permanent magnets
- similar operation to brushless motors

# Stepper motor

- uses fixed electromagnets  
armature on shaft has soft iron core  
i.e. no permanent magnets
- similar operation to brushless motors
- discrete steps

# Stepper motor


- uses fixed electromagnets  
armature on shaft has soft iron core  
i.e. no permanent magnets
- similar operation to brushless motors
- discrete steps
- drive electronics controls speed and direction

# Stepper motor


- uses fixed electromagnets  
armature on shaft has soft iron core  
i.e. no permanent magnets
- similar operation to brushless motors
- discrete steps
- drive electronics controls speed and direction
- half-stepping is possible
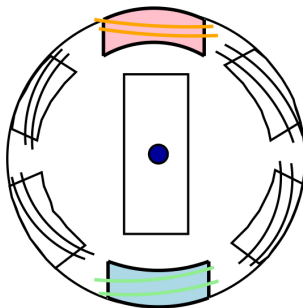
# Stepper motor

- uses fixed electromagnets  
armature on shaft has soft iron core  
i.e. no permanent magnets
- similar operation to brushless motors
- discrete steps
- drive electronics controls speed and direction
- half-stepping is possible
- can hold in position




Single stepping

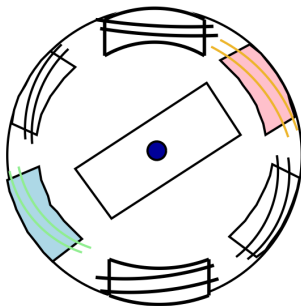


Single stepping




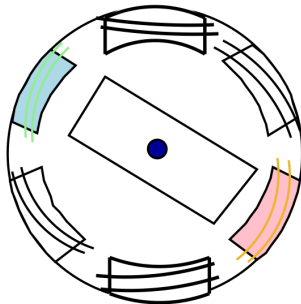


Single stepping

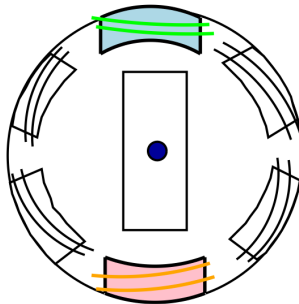


Single stepping

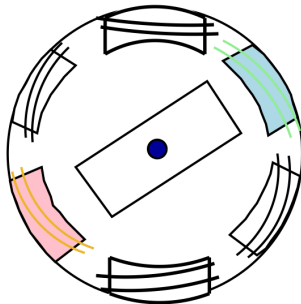


Single stepping

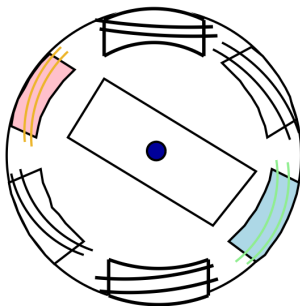


Single stepping

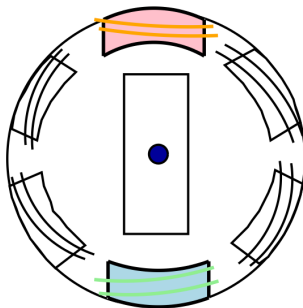


Half stepping

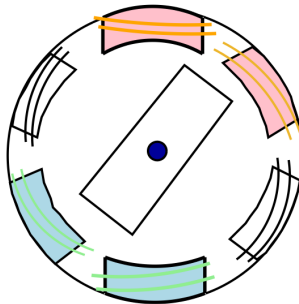

Half stepping

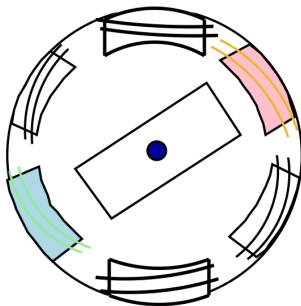


Half stepping

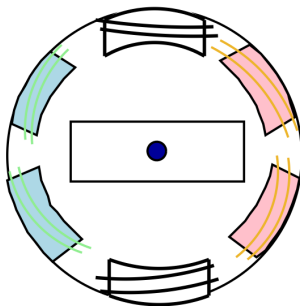


Half stepping




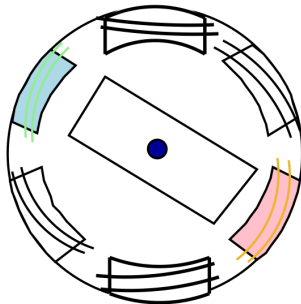


Half stepping

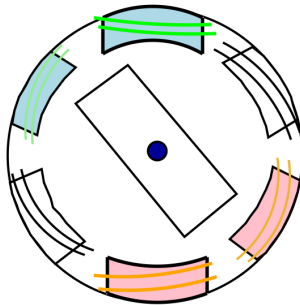


Half stepping

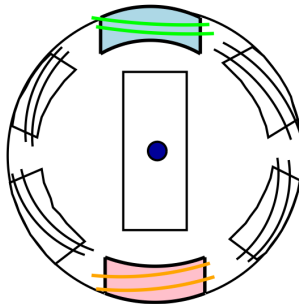


Half stepping

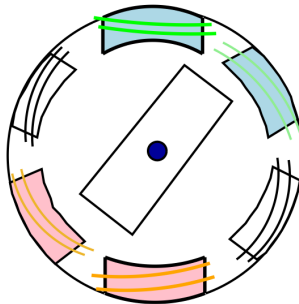


Half stepping

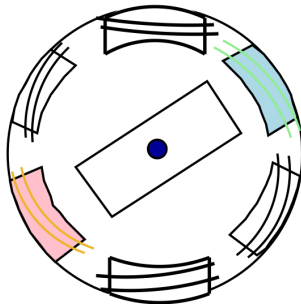


Half stepping

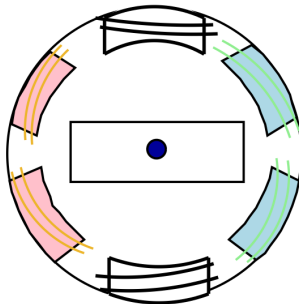

Half stepping

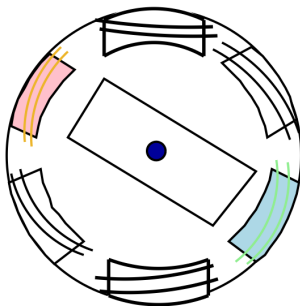

Half stepping

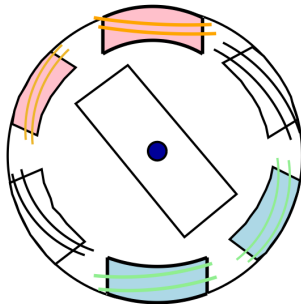

Half stepping



# Servo motor

# Servo motor

- PMDC motor with position sensing and feedback

# Servo motor

- PMDC motor with position sensing and feedback
- internal electronics

# Servo motor

- PMDC motor with position sensing and feedback
- internal electronics
- uses a digital pulse to control

# Servo motor

- PMDC motor with position sensing and feedback
- internal electronics
- uses a digital pulse to control  
default width keeps motor stationary (e.g. 1.5 ms)

# Servo motor

- PMDC motor with position sensing and feedback
- internal electronics
- uses a digital pulse to control
  - default width keeps motor stationary (e.g. 1.5 ms)
  - longer pulse makes motor rotate in one direction

# Servo motor

- PMDC motor with position sensing and feedback
- internal electronics
- uses a digital pulse to control
  - default width keeps motor stationary (e.g. 1.5 ms)
  - longer pulse makes motor rotate in one direction
  - shorter pulse makes motor rotate in the other direction

# Servo motor

- PMDC motor with position sensing and feedback
- internal electronics
- uses a digital pulse to control
  - default width keeps motor stationary (e.g. 1.5 ms)
  - longer pulse makes motor rotate in one direction
  - shorter pulse makes motor rotate in the other direction
  - pulse must be repeated periodically (e.g. every 20 ms)



## Servo motor

- PMDC motor with position sensing and feedback
- internal electronics
- uses a digital pulse to control
  - default width keeps motor stationary (e.g. 1.5 ms)
  - longer pulse makes motor rotate in one direction
  - shorter pulse makes motor rotate in the other direction
  - pulse must be repeated periodically (e.g. every 20 ms)
- often limited to less than 360 degree travel

## Servo motor

- PMDC motor with position sensing and feedback
- internal electronics
- uses a digital pulse to control
  - default width keeps motor stationary (e.g. 1.5 ms)
  - longer pulse makes motor rotate in one direction
  - shorter pulse makes motor rotate in the other direction
  - pulse must be repeated periodically (e.g. every 20 ms)
- often limited to less than 360 degree travel
- digital input does not have induced EMF problems

## Servo motor

- PMDC motor with position sensing and feedback
- internal electronics
- uses a digital pulse to control
  - default width keeps motor stationary (e.g. 1.5 ms)
  - longer pulse makes motor rotate in one direction
  - shorter pulse makes motor rotate in the other direction
  - pulse must be repeated periodically (e.g. every 20 ms)
- often limited to less than 360 degree travel
- digital input does not have induced EMF problems
  - internal electronics handles that

# Induced EMFs and motors

# Induced EMFs and motors

- Same problem as with solenoids

## Induced EMFs and motors

- Same problem as with solenoids  
can produce big voltage spikes

## Induced EMFs and motors

- Same problem as with solenoids  
can produce big voltage spikes
- Diodes across the coils can be used the same way

# Methods to reverse current to PM DC motor



# Methods to reverse current to PM DC motor

- dpdt switch


# Methods to reverse current to PM DC motor

- dpdt switch
- bipolar supply


# Methods to reverse current to PM DC motor

- dpdt switch
- bipolar supply
- H bridge


## DPDT switch

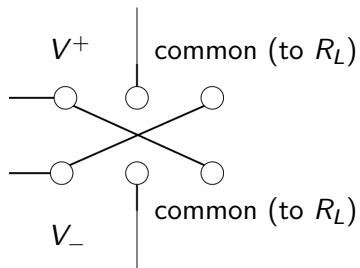


## DPDT switch

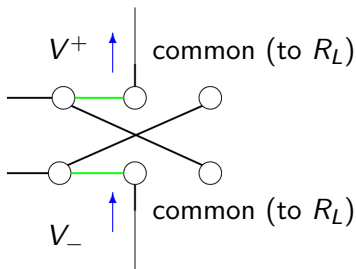


## DPDT switch

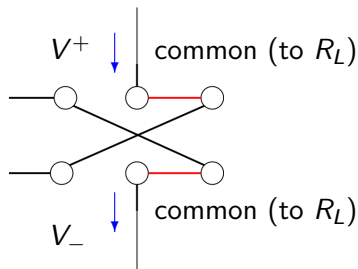

## Bipolar supply

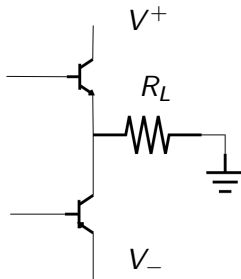


## Bipolar supply

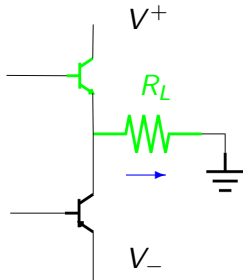





## Bipolar supply

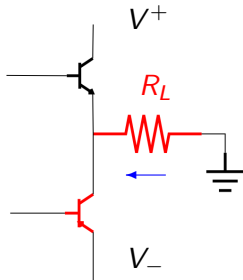

## H bridge

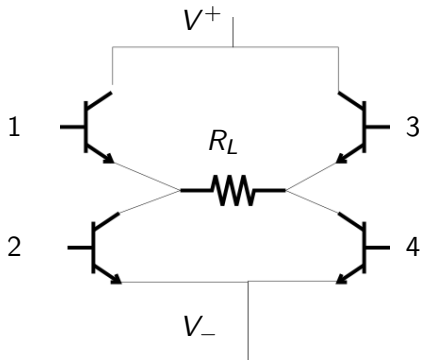

## H bridge

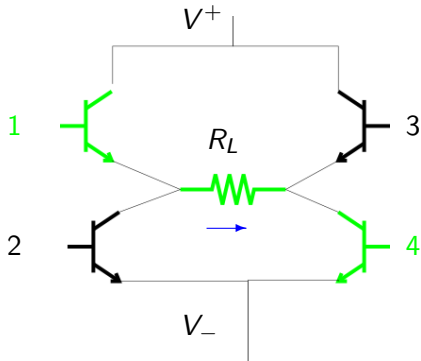

## H bridge

